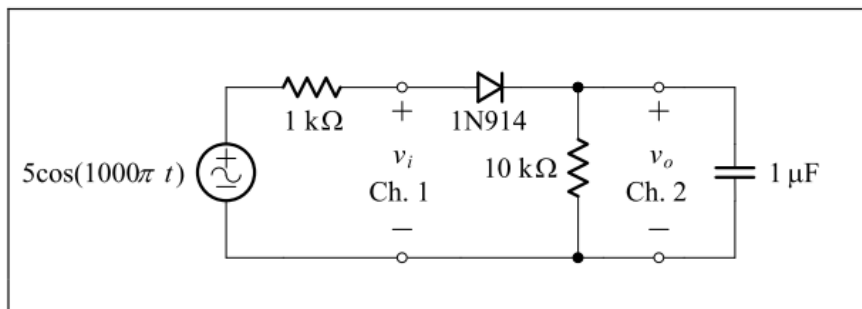



Analog Circuit

Lab 3


Perform the following practicles in LTspice as well as hardware. Sketch its V_i and V_o waveforms



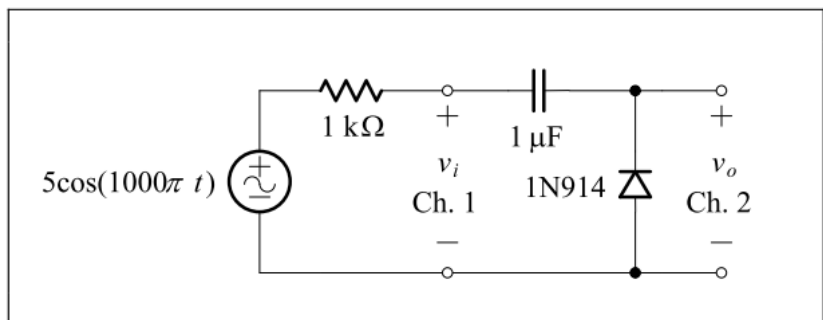Filtered half wave rectifier peak detector



Clamp circuit

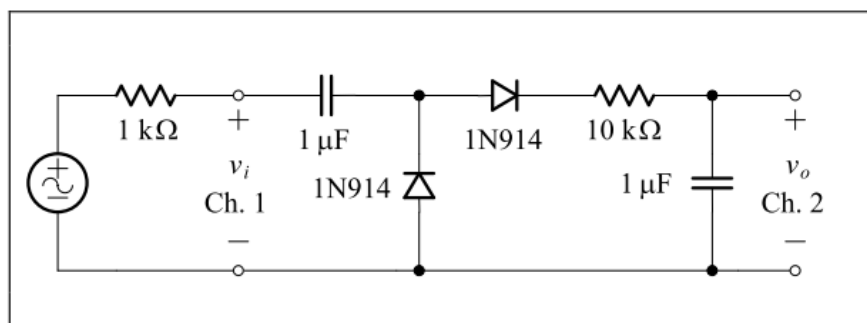

Voltage doubler