

Chapter 1 Solutions

1.1

A	B	C	$A \oplus B$	$B' \oplus C$	$(A \oplus B) \cdot C$	$A' \cdot (B' \oplus C)$	F
0	0	0	0	1	0	1	1
0	0	1	0	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	0	0	0
1	0	1	1	0	1	0	1
1	1	0	0	0	0	0	0
1	1	1	0	1	0	0	0

1.2

X	Y	B_{in}	$Diff$	B_{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Sum of Products: $Diff = XY'B_{in}' + X'Y'B_{in} + XYB_{in} + X'YB_{in}'$

$$B_{out} = X'B_{in} + X'Y + YB_{in}$$

Product of Sums: $Diff = (X + Y + B_{in})(X + Y' + B_{in}')(X' + Y + B_{in}')(X' + Y' + B_{in})$

$$B_{out} = (Y + B_{in})(X' + B_{in})(X' + Y)$$

1.3


CD \ AB	AB				
	00	01	11	10	
00	0	X	S	0	$S = G + H'$
01	X	E	E	X	
11	1	0	F'	1	
10	0	0	F'	0	

Set all map-entered variables to 0 to get $MS_0 = B'D$. Set E, F', G, and H, to 1 one at a time and all 1's to X's to get $MS_1 = C'D(E)$, $MS_2 = ABC(F')$, $MS_3 = BC'D'(G + H)$


$$Z = B'D + C'DE + ABCF' + BC'D'G + BC'D'H'$$

- 1.4 (a) $F = A'D' + AC'D + BCD' + A'B'C'E + BD'E$
 (b) $Z = A'CD' + C'D + BC'E + B'DE + CD'F + A'C'G$
 (c) $H = A'CD + A'B'CE + BCDF'$
 (d) $G = C'E'F + DEF + AD'F'$


1.5

 

 A static 1-hazard occurs when $A = 0$, $D = 0$, and C changes. When C changes from 1 to 0; $A'C$ also goes from 1 to 0. The hazard occurs because C' hasn't become 1 yet since it has to go through the inverter; therefore, F goes to 0 momentarily before going to 1. Gate delays are assumed to be 10ns in the timing diagram below.




1.6

 


$$F = bc' + b'd' + a'cd'$$

3 hazards: $A=0, C=0, D=0$, B changes
 $A=1, C=0, D=0$, B changes
 $A=0, B=1, D=0$, C changes

 To eliminate the hazards, add the term $c'd'$ (combining the four 1's in the top row) and replace $a'cd'$ with $a'd'$ (combining two 1's from the bottom left with two 1's from the top left.)



1.7 (a)

 

$$\begin{aligned}
 F &= ((ab)' \cdot (a+c)' + (a'+d)')' \\
 &= ab + ((a+c)' + (a'+d)')' \\
 &= ab + (a+c)(a'+d) \\
 &= ab + aa' + ad + a'c + cd;
 \end{aligned}$$

Circle all these terms on the K-map; arc shows nearby 1's not in the same product term, indicating a 1 hazard.


1-hazard $bcd = 110$, a changing $1 \Rightarrow 0$ gates 1,5,3,4,5,
 $0 \Rightarrow 1$ gates 3,4,5,1,5

$$\begin{aligned}
 F &= ab + aa' + ad + a'c + cd \\
 &= ab + a(a' + d) + c(a' + d) \\
 &= ab + (a+c)(a' + d) \\
 &= (ab + a+c)(ab + a' + d) \quad \text{--see Table 1-1 for Boolean laws} \\
 &= (a+c)(a+a'+d)(a'+b+d) \quad \text{-- } a+ab=a; a'+d+ab=(a'+d+a)(a'+d+b)
 \end{aligned}$$


Circle all these terms of 0's in the K-map; arc shows 0's not in same term.

0-hazard $bcd = 000$, a changing $0 \Rightarrow 1$ gates 3,4,5,3,5,
 $1 \Rightarrow 0$ gates 3,4,5,2,5

 - (b) We will design a 2-level sum of products circuit because a 2-level sum-of-products circuit has no 0-hazard as long as an input and its complement are not connected to the same AND gate. Avoid 1-hazard by adding product term bc . Use NAND gates as asked in the question.



1.8 (a)

 

$$\begin{aligned}
 H' &= ((A'+C)(C+D')(B+C'))' \\
 &= (A'+C)' + (C'+D')' + (B+C')' \\
 &= AC' + C'D + B'C
 \end{aligned}$$

$$H = (A'+C)(C+D')(B+C')$$

The circuit is in the Product-of-Sums form, and thus we only need to consider the static 0-hazards.

Circle all these terms of 0's in the K-map; arc shows 0's not in same term.

3 hazards:


ABCD = 0001, C changes to 1

ABCD = 1001, C changes to 1


ABCD = 1000, C changes to 1

Adding the terms: $(A'+B)(B+D')$ will eliminate the hazards.

(b)

 

1.9 (a)

 

$$f = AC' + A'B'D$$

Circle all these terms on the K-map; arc shows nearby 1's not in the same product term, indicating a 1 hazard.

Static 1-hazard:

$ABCD = 0001$, A changes to 1

$$f' = A'B + AC + A'D'$$


$$f = (A+B')(A'+C')(A+D)$$

Circle all these terms of 0's in the K-map; arc shows 0's not in same term.

Static 0-hazard:

$ABCD = 0010$, A changes to 1

(b)

 

1.10 (a) Any two of the three solutions will suffice.

AB \ CD	00	01	11	10
00	1	0	1	1
01	0	1	1	1
11	0	1	1	0
10	1	1	0	0

$$F = AC' + BD + A'CD' + B'C'D'$$

Static 1-hazard:
Between ABCD = 0000 and 0010
Between 0110 and 0111

AB \ CD	00	01	11	10
00	1	0	1	1
01	0	1	1	1
11	0	1	1	0
10	1	1	0	0

$$F = AC' + BD + A'BC + A'B'D'$$

Static 1-hazard:
Between ABCD = 0000 and 1000
Between 0010 and 0110

AB \ CD	00	01	11	10
00	1	0	1	1
01	0	1	1	1
11	0	1	1	0
10	1	1	0	0

$$F = AC' + BD + A'B'D' + A'CD'$$

Static 1-hazard:
Between ABCD = 0000 and 1000
Between 0110 and 0111

Hazard free circuit:
 $F = AC' + BD + A'BC + A'B'D' + A'CD' + B'C'D'$

(b)

AB \ CD	00	01	11	10
00	1	0	1	1
01	0	1	1	1
11	0	1	1	0
10	1	1	0	0

AB \ CD	00	01	11	10
00	1	0	1	1
01	0	1	1	1
11	0	1	1	0
10	1	1	0	0


$$F = (A+B'+C+D)(A+B+D')(A'+B+C')(A'+C'+D) \quad F = (A+B'+C+D)(A+B+D')(B+C'+D')(A'+C'+D)$$

Static 0-hazard:
Between ABCD = 0011 and 1011

Static 0-hazard:
Between ABCD = 1010 and 1011

Hazard free circuit:
 $F = (A+B'+C+D)(A+B+D')(A'+B+C')(A'+C'+D) (B+C'+D')$

1.11

 

(a) $Z = A'D' + (A + B)(B' + C')$
 $= A'D' + AB' + AC' + BB' + BC'$

Static 1 hazard (see the arcs between nearby 1's not in the same product term.)

ABCD = 0000 to 1000

ABCD = 0010 to 1010

$$Z = (A'D' + A + B)(A'D' + B' + C')$$

$$= (A' + A + B)(D' + A + B)(A' + B' + C')(D' + B' + C')$$

Static 0 hazard (see the arcs between nearby 0's not in the same term)

ABCD = 0111 to 0011

- (b) One can design a hazard-free sum of products circuit as in the previous question. Or, one can design a product of sums (POS) circuit with no hazards. A properly designed 2-level POS circuit has no 1-hazards. Static 0-hazards can be avoided by including loops for all 0's that are adjacent. 4 terms here including the arc:

$$Z = (A + B + D')(A' + B' + C')(D' + B' + C')(C' + D' + A)$$


$$= (D' + A + BC')(A' + B' + C')(D' + B' + C')$$

combining 1st and 4th terms


$$= (D' + A + BC')(B' + C' + A'D')$$

combining 2nd and 3rd terms


1.12 (a)

 

 
- (b) From the characteristic equation for a J-K flip-flop ($Q^+ = JQ' + K'Q$):



1.13

 

1.14 (a)

 

Present State		Next State		Output	
		X = 0	1	X = 0	1
Reset	S0	S1	S0	0	0
0	S1	S1	S2	0	0
01	S2	S3	S4	0	0
010	S3	S1	S5	0	1
011	S4	S5	S0	1	0
0101 or 0110	S5	S0	S0	1	1

(b) Guidelines:

- I. (0,1,3),(0,4,5)
- II. (0,1),(1,2),(3,4),(1,5),(0,5)
- III. (0,1,2,3),(4,5),(3,5)

For state assignment:

S0 = 000 S1 = 001 S2 = 010 S3 = 011 S4 = 100 S5 = 101


Equations for NAND gate network:

$$\begin{aligned} J_1 &= XQ_2 & K_1 &= X + Q_3 \\ J_2 &= XQ_1'Q_3 & K_2 &= X + Q_3 \\ J_3 &= X' & K_3 &= XQ_2' + Q_1 \\ Z &= XQ_2Q_3 + X'Q_1 + Q_1Q_3 \end{aligned}$$

For NOR gate network, use product of sums form:

$$\begin{aligned} K_3 &= (X + Q_1)(Q_2') \\ Z &= (Q_1 + Q_2)(X' + Q_3)(X + Q_2') \end{aligned}$$

1.15 (a)

 

Present State	Next State		Output	
	X = 0	1	X = 0	1
S0	S1	S3	00	00
S1	S1	S2	00	00
S2	S4	S3	10	00
S3	S4	S3	00	00
S4	S5	S2	01	00
S5	S5	S6	00	00
S6	S7	S6	00	00
S7	S5	S6	01	00

(b) Guidelines:

- I. (0,1),(2,3),(4,5,7),(0,2,3),(1,4),(5,6,7)
- II. (1,3),(1,2),2x(3,4),(2,5),2x(5,6),(6,7)
- III. (0,1,3,5,6),(4,7)

For state assignment:

S0 = 000 S1 = 100 S2 = 001 S3 = 101
S4 = 111 S5 = 011 S6 = 010 S7 = 110

Equations for NAND gate network:

$$\begin{aligned} J_1 &= Q_2' + X'Q_3' & K_1 &= XQ_3' + Q_2 \\ J_2 &= X'Q_3 & K_2 &= XQ_1Q_3 \\ J_3 &= XQ_2' + X'Q_1Q_2 & K_3 &= XQ_1'Q_2 \end{aligned}$$

$$Z_1 = X'Q_1'Q_2'Q_3$$

$$Z_2 = X'Q_1Q_2$$


For NOR gate network, use product of sums form:

$$J_1 = (Q_2' + Q_3')(X' + Q_2')$$

$$K_1 = (X + Q_2)(Q_2 + Q_3')$$

$$J_3 = (X + Q_2)(X' + Q_2')(X + Q_1)$$

1.16 (a)

 

Present State	Next State		Output	
	X = 0	1	X = 0	1
S0	S1	S1	00	10
S1	S2	S4	10	00
S2	S3	S3	00	10
S3	S0	S0	00	10
S4	S3	S5	10	00
S5	S0	S0	10	01

(b) Guidelines:

I. (2,4),2x(3,5)

II. (2,4),(3,5)

III. (0,2,3),(1,4,5)

For state assignment:

S0 = 000 S1 = 010 S2 = 001 S3 = 101 S4 = 011 S5 = 111

Equations for NAND gate network:

$$D_1 = Q_1'Q_3$$

$$D_2 = Q_2'Q_3' + XQ_1'Q_2$$

$$D_3 = Q_1'Q_3 + Q_2Q_3' \text{ or } Q_1'Q_3 + Q_1'Q_2$$

$$S = XQ_2' + X'Q_2$$

$$V = XQ_1Q_2$$


For NOR gate network, use product of sums form:

$$S = (X + Q_2)(X' + Q_2')$$

$$D_2 = Q_1'(Q_2 + Q_3')(X + Q_2')$$

$$D_3 = Q_1'(Q_2 + Q_3)$$

1.17 (a)

 

Present State	Next State		Output	
	X = 0	1	X = 0	1
S0	S1	S1	00	10
S1	S2	S3	10	00
S2	S4	S5	10	00
S3	S5	S5	00	10
S4	S0	S0	11	00
S5	S0	S0	00	10

(b) Guidelines:

- I. (4,5),(2,3)
- II. (2,3),(4,5)
- III. (0,3,5),(1,2,4)

For state assignment:

S0 = 000 S1 = 100 S2 = 101 S3 = 001 S4 = 111 S5 = 011


Equations for NAND gate network:

$$\begin{aligned}
 J_1 &= Q_3' & K_1 &= X + Q_2 \\
 J_2 &= Q_3 & K_2 &= 1 \\
 J_3 &= Q_1 & K_3 &= Q_2 \\
 D &= X'Q_1 + XQ_1'Q_3 \\
 B &= X'Q_1Q_2
 \end{aligned}$$

For NOR gate network, use product of sums form:

$$D = (X' + Q_1')(X + Q_1)(Q_1 + Q_3)$$

1.18

 

Present State	Next State		Output
	X = 0	1	
S0	S0	S1	0
S1	S0	S2	0
S2	S0	S3	0
S3	S4	S3	1
S4	S5	S3	1
S5	S0	S3	1

1.19

Present State ($Q_2Q_1Q_0$)	Next State ($Q_2^+Q_1^+Q_0^+$)
000	001
001	010
010	011
011	100
100	101
101	000

$$\begin{aligned}
 J_2 &= Q_1Q_0 & K_2 &= Q_0 \\
 J_1 &= Q_2'Q_0 & K_1 &= Q_0 \\
 J_0 &= 1 & K_0 &= 1
 \end{aligned}$$

1.20

Present State ($Q_2Q_1Q_0$)	Next State ($Q_2^+Q_1^+Q_0^+$)
001	010
010	011
011	100
100	101
101	110
110	001

$$\begin{aligned}
 D_2 &= Q_1Q_0 + Q_2Q_1' \\
 D_1 &= Q_2'Q_0' + Q_1'Q_0 \\
 D_0 &= Q_0'
 \end{aligned}$$

1.21

Present State ($Q_2Q_1Q_0$)	Next State ($Q_2^+Q_1^+Q_0^+$)
000	001
001	010
010	011
011	100
100	101
101	110
110	000

$$\begin{aligned}
 J_2 &= Q_1Q_0 & K_2 &= Q_1 \\
 J_1 &= Q_0 & K_1 &= Q_2 + Q_0 \\
 J_0 &= Q_2' + Q_1' & K_0 &= 1
 \end{aligned}$$

1.22

Present State ($Q_2Q_1Q_0$)	Next State ($Q_2^+Q_1^+Q_0^+$)
001	010
010	011
011	100
100	101
101	110
110	111
111	001

$$D_2 = Q_2'Q_1Q_0 + Q_2Q_1' + Q_2Q_0'$$

$$D_1 = Q_1Q_0' + Q_1'Q_0$$

$$D_0 = Q_2Q_1 + Q_0'$$

1.23


Present State ($Q_2Q_1Q_0$)	Next State ($Q_2^+Q_1^+Q_0^+$)
000	001
001	011
010	XXX
011	101
100	XXX
101	111
110	XXX
111	000

$$D_2 = Q_2'Q_1 + Q_2Q_1'$$

$$D_1 = Q_1'Q_0$$

$$D_0 = Q_2' + Q_1'$$


1.24

 


present state	next state		output	
	$X = 0$	$X = 1$	$X = 0$	$X = 1$
A	B	G	0	1
B	A	D	1	1
C	F	G	0	1
D	H G	A	0	0
E	G	C	0	0
F	C	D	1	1
G	G	E D	0	0
H	G	D	0	0

1.25 $Eni = 0$ $Ena = 0$ $Enb = 0$ $Enc = 1$ $Lda = 1$ $Ldb = 1$ $Ldc = 0$

1.26

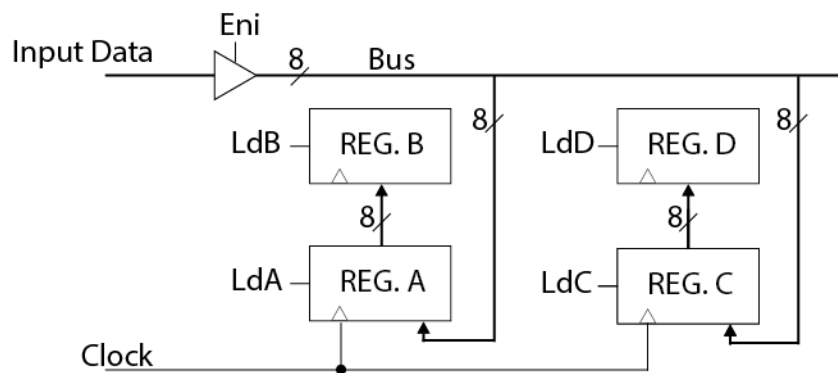


The circuit requires one tri-state gate.

 


Minimum of 5 cycles for the transfer.

1.27

 

 The circuit requires five tri-state gates.



Minimum of 10 cycles for the transfer.

