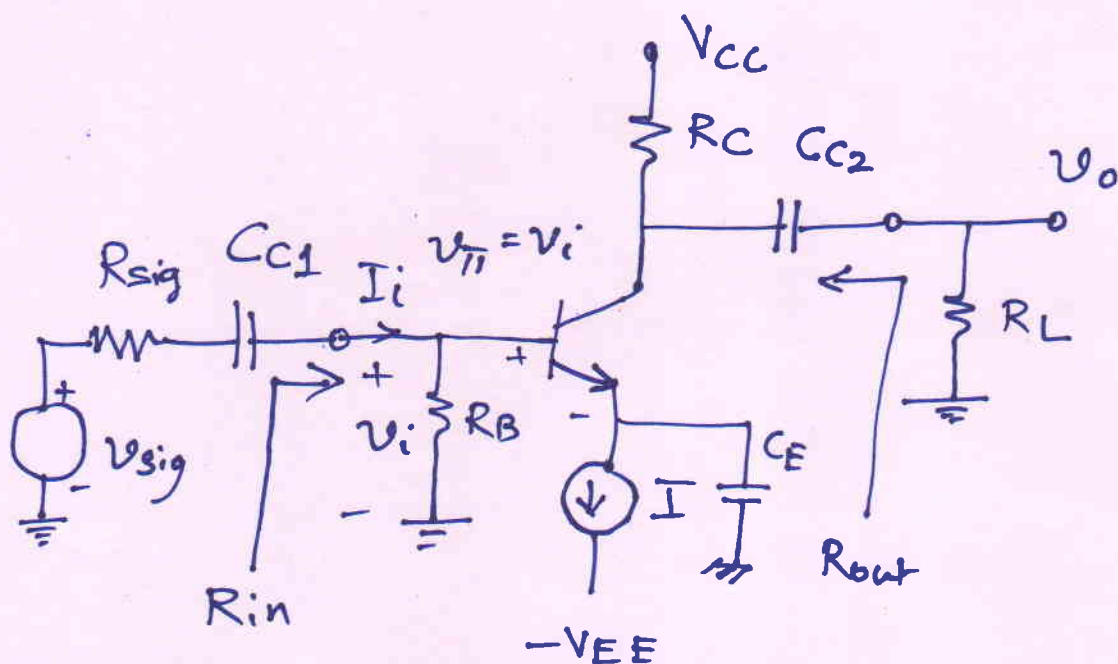


SINGLE STAGE AMPLIFIER (CE)

①



C_{C1} & C_{C2} = inter-stage coupling capacitors
Act like perfect short circuit at

lowest frequency of operation.
Usually $10 \rightarrow 100 \mu F$

R_B = To provide dc biasing path to I_B . It

reduces $R_{in} = R_B \parallel \beta_{in}$.


If signal source can pass I_B then we can dispense with R_B .

C_E = Emitter Bypass Capacitor to bring Emitter to 0V as far as AC is concerned.

So it becomes Common Emitter Amplifier.

Usually $100 \mu F$ or more.

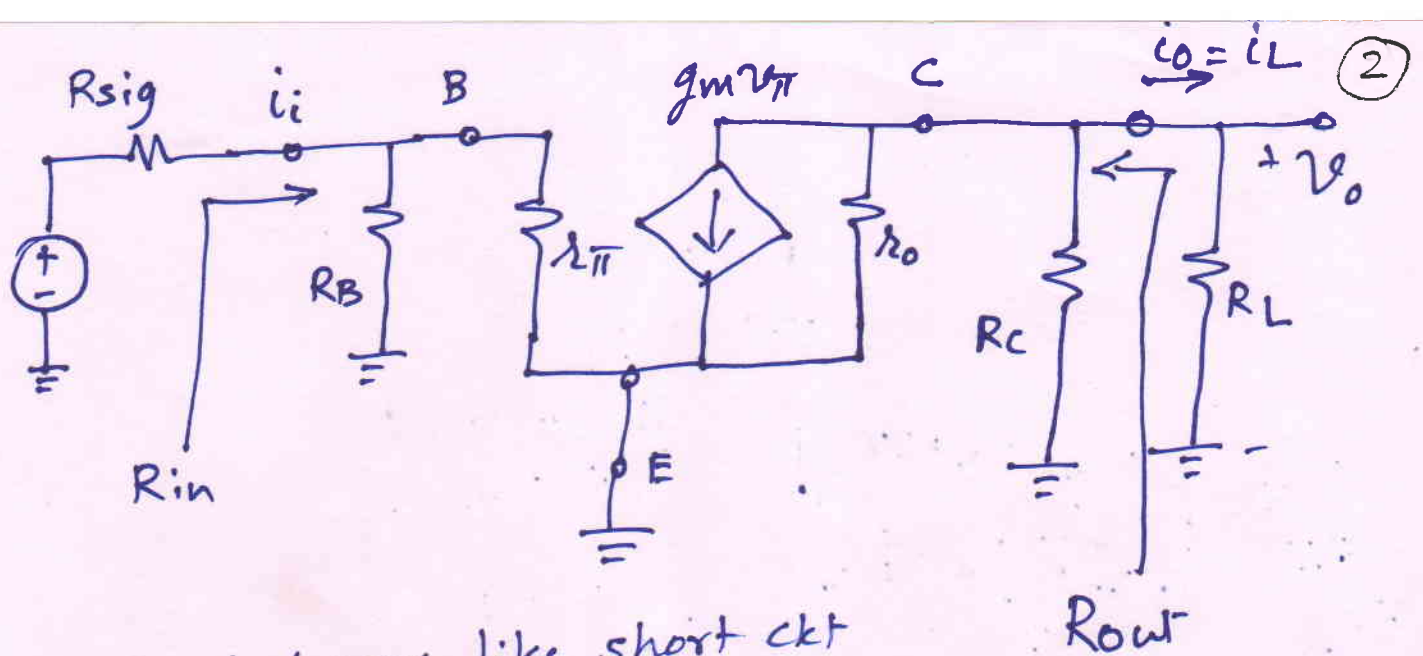For AC purposes V_{CC} & $-V_{EE}$ are at same potential or one end of R_C is grounded.



$\therefore C_{C2}$ behaves like short ckt

$$v_o = v_c$$

Note: R_L could be actual load or it could be R_{in} of next stage amplifier

$$R_{in} = \frac{v_i}{i_i} = \frac{R_B \cdot r_{\pi}}{R_B + r_{\pi}} \quad \left(\text{if } R_B \gg r_{\pi} \right)$$

$100k \gg 2.5k$

$$\text{then } R_{in} \approx r_{\pi}$$

$$v_i \approx v_{sig} \frac{r_{\pi}}{r_{\pi} + R_{sig}} = v_{\pi}$$

Using g_m as transconductance, the output current source $g_m \cdot v_{\pi}$ drives 3 loads in parallel

$$v_o = -g_m v_{\pi} (r_o \parallel R_C \parallel R_L)$$

Voltage Gain of Amplifier Proper (Base to Collector)

$$A_v = -g_m (r_o \parallel R_C \parallel R_L)$$


Open Circuit Voltage Gain (When $R_L = \infty$)

$$A_{v_o} = -g_m (r_o \parallel R_C) \quad \because r_o \approx 100k$$

$$R_C = 1k$$

$$A_{v_o} \approx -g_m \cdot R_C$$

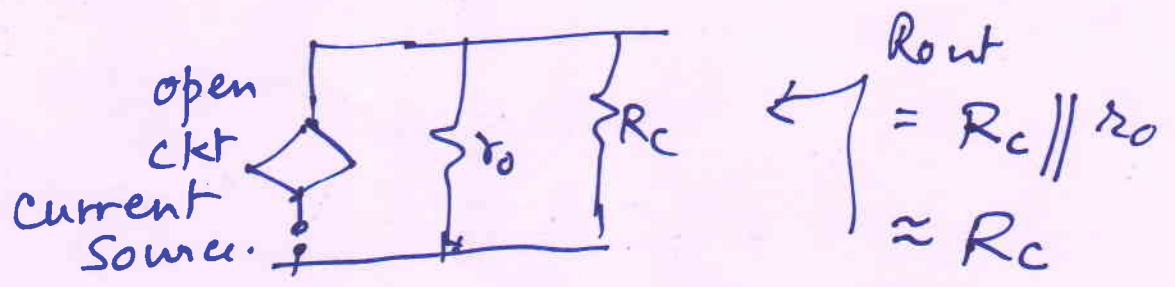Output Resistance R_{out} can be calculated by (3) measuring resistance when $V_{sig} = 0$. This gives us only resistors R_c & r_o in parallel



Voltage Gain with R_L Connected

$$A_v = A_{vo} \frac{R_L}{R_L + r_o}$$

Overall Voltage Gain — From Source to Load is

$$G_v = \frac{v_o}{v_{sig}} = \frac{v_i}{v_{sig}} \cdot \frac{v_o}{v_i}$$

$$= \left\{ \frac{(R_B \parallel r_{\pi})}{(R_B \parallel r_{\pi}) + R_{sig}} \right\} \cdot \frac{g_m (r_o \parallel R_c \parallel R_L)}{1}$$

if $R_B \gg r_{\pi}$

$$= \frac{(r_{\pi} \cdot g_m)}{r_{\pi} + R_{sig}} (r_o \parallel R_c \parallel R_L)$$

$$= \frac{\beta}{r_{\pi} + R_{sig}} (r_o \parallel R_c \parallel R_L)$$

Thus, Voltage Gain is highly dependent upon β if $R_{sig} \approx r_{\pi}$. If $R_{sig} \ll r_{\pi}$ then

$$G_v \approx -g_m (R_C \parallel R_L \parallel r_o)$$

In other words, overall voltage gain is nearly the gain of proper amplifier, irrespect of β value & dependence on β reduces.

So it is important to have small R_{sig} as compared to r_{π} .

Let us calculate Short Circuit Current Gain A_{is} .
When R_L is short circuited, all of current source current $-g_m v_{\pi}$ flows through it as i_L .

$$i_{os} = -g_m v_{\pi}$$

$$i_i = \frac{v_{\pi}}{r_{\pi}} = \frac{v_i}{R_{in}}$$

$$\therefore A_{is} = \frac{i_{os}}{i_i} = \frac{-g_m v_{\pi}}{v_i / R_{in}} = -g_m R_{in}$$

So HIGH input impedance R_{in} gets us higher Current Gain. So R_B must be chosen as high as possible.

$$A_{is} = -g_m \frac{(R_B \parallel r_{\pi})}{R_B + r_{\pi}}$$

For $R_B = 100k$, $R_C = 8k$, $\beta = 100$, $\alpha = 0.99$, $V_A = 100V$.
 $R_L = 5k$, $R_{sig} = 5k$


Calculate g_m , r_{π} , r_o , r_e , R_{in} , A_{vo} (without r_o), R_{out} (with and without r_o). Find Overall A_v .

COMMON EMITTER AMPLIFIER with


5

Emitter Resistance

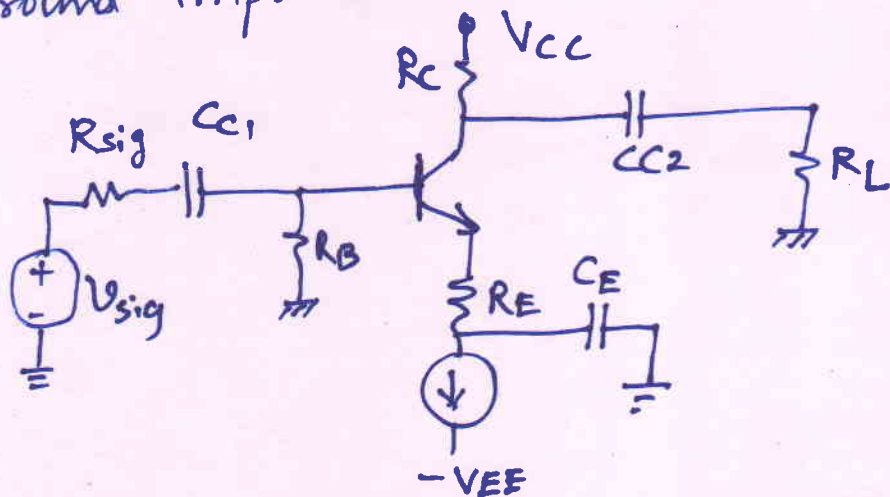Adding a resistor R_E between emitter and ground improves characteristics considerably.



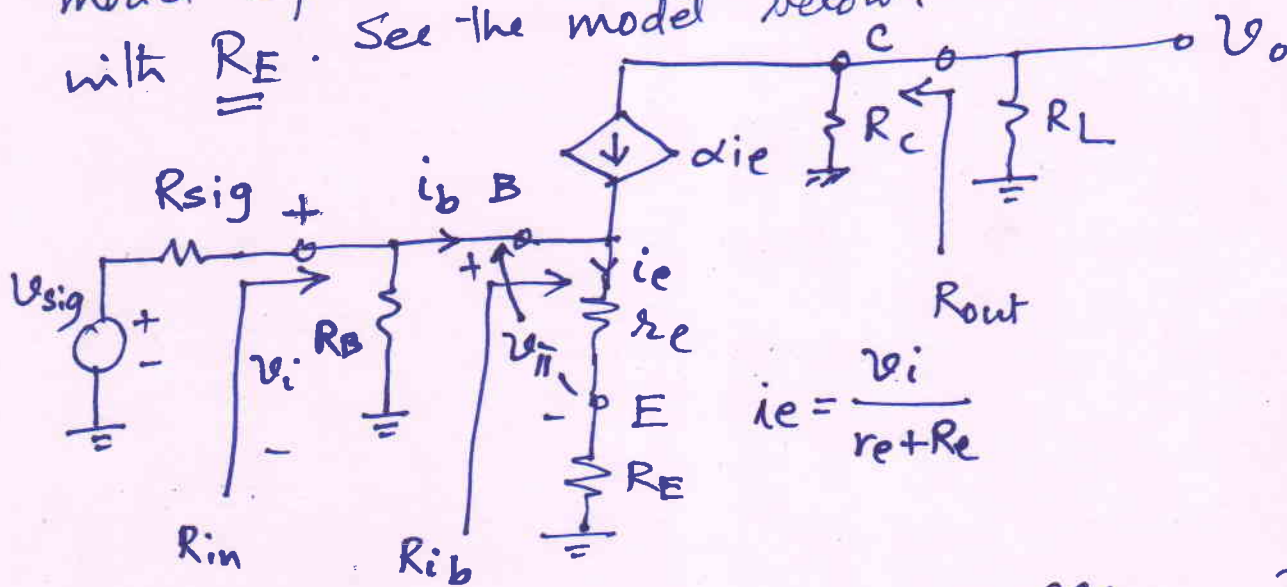We will use T-model as it is more convenient. Its model ~~input~~ ^{emitter} resistance r_e will appear in series with R_E . See the model below:



$$i_e = \frac{v_i}{r_e + R_E}$$

$$R_{in} = R_B \parallel R_{iB}$$

$$R_{iB} = \frac{v_i}{i_b} = \frac{v_i}{i_e / (1 + \beta)}$$

$$\text{also, } i_e = \frac{v_i}{r_e + R_E} \therefore R_{iB} = (1 + \beta)(r_e + R_E)$$

Input Resistance looking into Base is β TIMES R_E .
Thus a $R_E = 100 \Omega$ can add $100 \times 100 = 10K$ to R_{iB} if $\beta = 100$.
INPUT RESISTANCE INCREASED.

R_E effect gets "multiplied" when viewed from Base. This is called "Resistance Reflection Rule". (6)

Improvement in R_{ib} by addition of R_E is

$$\frac{R_{ib}(\text{without } R_E)}{R_{ib}(\text{with } R_E)} = \frac{(\beta+1)(r_e + R_E)}{(\beta+1)r_e} = 1 + \frac{R_E}{r_e} = (1 + g_m R_E)$$

Determine Voltage Gain A_v , we calculate

$$v_o = -i_c (R_C \parallel R_L) \\ = -\alpha i_e (R_C \parallel R_L)$$

substituting $i_e = \frac{v_i}{r_e + R_E}$

$$v_o = -\alpha (R_C \parallel R_L) \cdot \frac{v_i}{(R_E + r_e)}$$

$$A_v = \frac{v_o}{v_i} = - \frac{\alpha (R_C \parallel R_L)}{r_e + R_E}$$

VOLTAGE GAIN IS RATIO OF TOTAL COLLECTOR RESISTANCE ($R_C \parallel R_L$) TO TOTAL EMITTER RESISTANCE ($r_e + R_E$) and independent of g_m or β .

This is a big advantage.

Open Circuit Voltage Gain (with $R_L = \infty$)

$$A_{v_o} = - \frac{\alpha R_C}{r_e + R_E} = - g_m R_C \left(\frac{1}{1 + g_m R_E} \right)$$

Note that for amplifier proper the A_{vo} is $-g_m R_c$ (7)

\therefore Addition of series resistor R_E reduces Voltage Gain.

This is the cost we pay to enjoy two gains mentioned earlier:

$(1+g_m R_E)$ is the factor by input resistance is increased & by the same factor the Voltage Gain is decreased.

Output Resistance R_{out} can be seen as
 $R_{out} = R_c$ (when Current Source is open circuited)
& $V_{sig} = 0$.

Short Circuit Current Gain A_{is} is

$$i_{os} = -\alpha i_e$$

$$i_i = v_i / R_{in}$$

$$\therefore A_{is} = \frac{i_{os}}{i_i} = \frac{-\alpha i_e \cdot R_{in}}{v_i}$$

$$\therefore i_e = \frac{v_i}{r_e + R_E}$$

$$A_{is} = -\frac{\alpha R_{in}}{(r_e + R_E)} = \frac{-\alpha}{(r_e + R_E)} (R_B \parallel R_{ib})$$

if $R_B \gg R_{ib}$

$$= -\frac{\alpha (R_{ib})}{r_e + R_E} = -\frac{\alpha (1+\beta)(r_e + R_E)}{r_e + R_E} \approx -\beta$$

So current gain remains β even though voltage gain is reduced. (8)

Overall ~~Voltage~~ Gain calculated as:

$$G_v = \frac{V_i}{V_{sig}} \cdot A_v = - \frac{R_{in}}{R_{sig} + R_{in}} \cdot \frac{\beta (R_C \parallel R_L)}{(r_e + R_e)}$$

$$\therefore R_{in} = R_B \parallel R_{ib} \quad \& \text{ neglecting } R_B \\ \approx R_{ib} \quad \because R_B \gg R_{ib}$$

$$G_v = - \frac{\beta (R_C \parallel R_L)}{R_{sig} + (\beta + 1)(r_e + R_e)}$$

The gain is lower because of a factor $(1 + \beta)R_e$ in denominator.

$$\frac{V_{\pi}}{V_i} = \frac{r_e}{r_e + R_e} = \frac{1}{1 + g_m R_e}$$

Note: For the given V_i , we get small V_{π} therefore output voltage is less by factor $(1 + g_m R_e)$.

Summary :

Adding a resistor R_E in series of Emitter Causes:

1. Input Resistance R_{iB} increases by a factor of $(1 + g_m R_E)$.
2. Voltage Gain reduces by factor $(1 + g_m R_E)$
3. For the same non-linear distortion, the input signal v_i can be increased by a factor $(1 + g_m R_E)$.
4. Overall Voltage Gain is less dependent on β variation or value.
5. Other benefits will be discussed later.