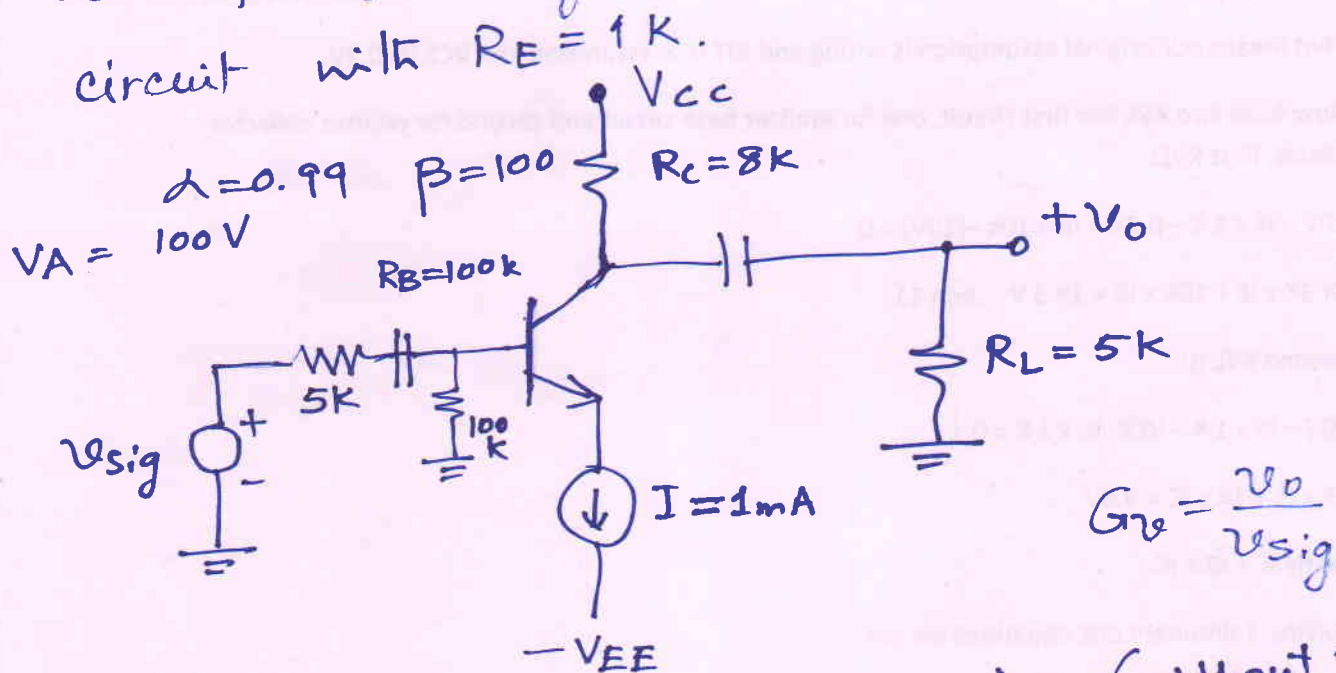


Problem To Be Solved in Class CE Amplifier ①
Solve for following circuit as well as second circuit with $R_E = 1K$.



$$G_v = \frac{v_o}{v_{sig}}$$

Calculate g_m , r_{π} , r_o , r_e , R_{in} , A_{v_o} (without r_o), R_{out} (with and without r_o) and Overall Gain G_v .
In second circuit insert a $1K$ R_E between emitter and current source & recalculate.

Solution: $I_E = 1mA$ assuming $I_C \approx I_E = 1mA$

$$g_m = I_C / V_T = 1mA / 25mV = \boxed{40mS}$$

$$r_{\pi} = \beta / g_m = \frac{100}{40mS} = \boxed{2500\Omega}$$

$$\text{Early Effect resistance } r_o \approx V_A / I_C = \frac{100V}{1mA} \approx \boxed{100K}$$

$$r_e = \frac{1}{g_m} = \frac{1}{40mS} = \boxed{25\Omega} \text{ not used here in first part}$$

$$R_{in} = R_B \parallel R_{iB} = R_B \parallel r_{\pi} = 100K \parallel 2.5K = 2.439K$$

Voltage Gain of Amplifier ~~Proper~~

(2)

with r_o included and load connected

$$\begin{aligned} A_{v_o} &= -g_m (R_c \parallel R_L \parallel r_o) \\ &= -40 \text{ mV} (8\text{K} \parallel 5\text{K} \parallel 100\text{K}) \\ &= -40 \text{ mV} (2.985\text{K}) = \boxed{-119.4 \text{ V/V}} \end{aligned}$$

without r_o included

$$A_{v_o} = -40 \text{ mV} (8\text{K} \parallel 5\text{K}) = \boxed{-123.07 \text{ V/V}}$$

Output Impedance/Resistance R_{out} seen by R_L .

$$R_{out} = R_c \parallel \cancel{R_L} \parallel r_o = 8\text{K} \parallel 100\text{K} = \boxed{7.40\text{K}}$$

Overall Voltage Gain

$$G_v = \left(\frac{R_{in}}{R_{in} + R_{sig}} \right) \cdot g_m \cdot (r_o \parallel R_c \parallel R_L)$$

$$= - \frac{2.439\text{K}}{2.439\text{K} + 5\text{K}} \cdot 40 \text{ mV} \cdot (2.985\text{K})$$

$$= 0.327 \cdot (-119.4)$$

$$= \boxed{-39.14 \text{ V/V}}$$

With a emitter resistance $R_E = 1\text{K}$ inserted (3)

$$g_m = 40\text{mV} \quad \text{same as before}$$

$$r_{\pi} = 2500\Omega \quad " \quad " \quad "$$

$$r_o = 100\text{k}\Omega \quad " \quad " \quad "$$

$$R_{in} = R_B \parallel R_{iB} = 100\text{k} \parallel (r_{\pi} + (1+\beta)R_E)$$

$$= 100\text{k} \parallel (2.5\text{k} + 101 \cdot 1\text{k})$$

$$= 100\text{k} \parallel 103.5\text{k} = 50.85\text{k}$$

(Note R_{in} has improved from 2.43k to 50.85k)

$$\text{Voltage Gain } A_v = - \frac{\alpha (R_C \parallel R_L)}{r_e + R_E}$$

$$= - \alpha \frac{3.076\text{k}\Omega}{25 + 1\text{k}} = - \frac{0.99 \times 3.076\text{k}}{1.025\text{k}}$$

$$= \boxed{-2.971 \text{ V/V}}$$

(This was -123.07 earlier).

$$G_v = \frac{R_{in}}{R_{in} + R_{sig}} \cdot A_v$$


$$= \frac{50.85\text{k}}{50.8\text{k} + 5\text{k}} \cdot (-2.971)$$

$$= 0.910 \times (-2.971) = \boxed{-2.70 \text{ V/V}}$$

↑ This factor was 0.327 , so it is improved.

$$\begin{aligned} R_{out} &= R_C = 8\text{k} \\ \text{or } 7.40\text{k} \\ &\text{if } r_o \text{ taken into} \\ &\text{account.} \end{aligned}$$

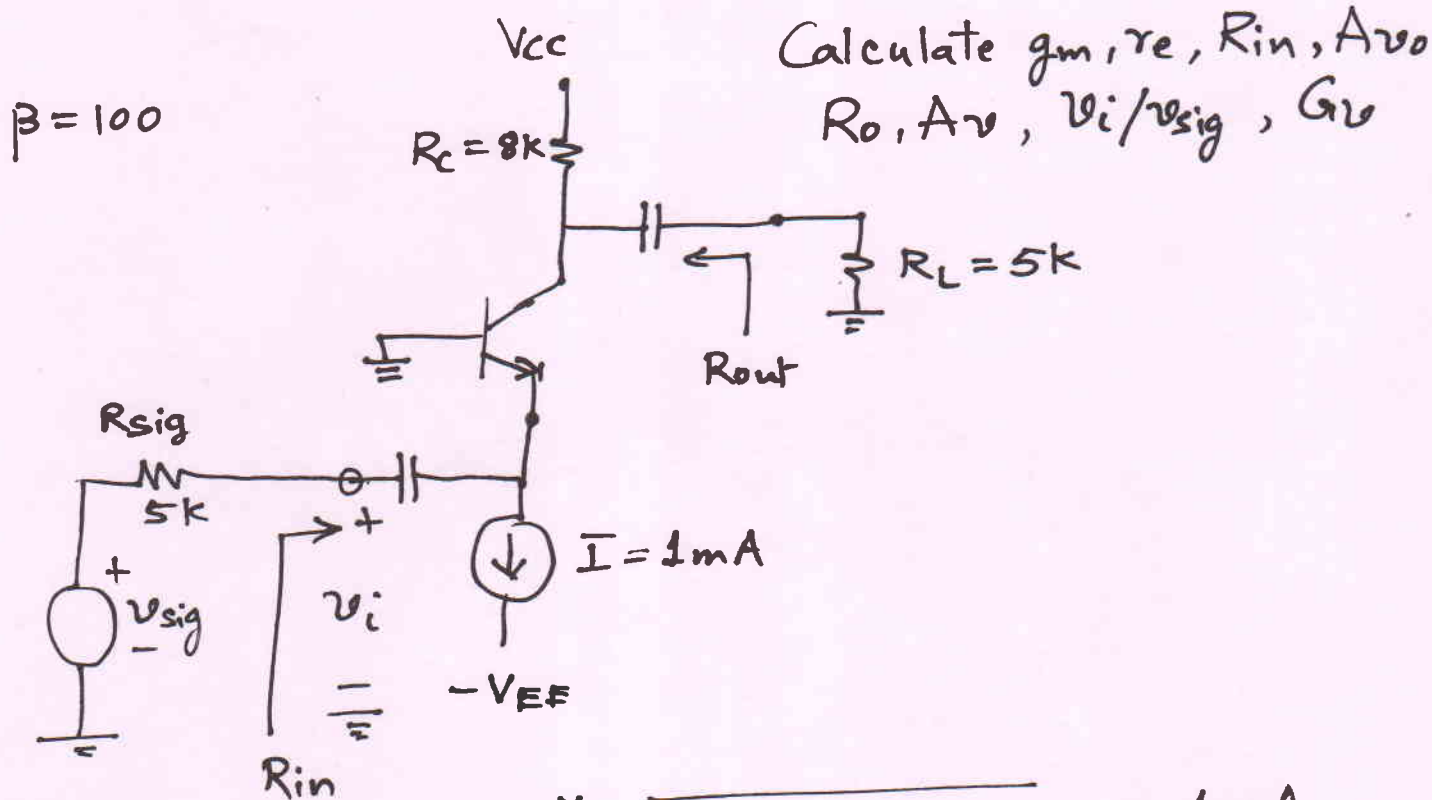Problem (4) to be solved in Class on CB Configuration.



Soln: $\because I_E = 1\text{mA}$ we assume $I_C \approx I_E \approx 1\text{mA}$

$\therefore g_m = I_C / V_T = 1\text{mA} / 25\text{mV} = 40\text{mS}$

$r_e = \frac{1}{g_m} = \frac{1}{40\text{mS}} = 25\Omega$

Signal source sees a very low input resistance

$R_{in} = r_e = 25\Omega$

$\frac{v_i}{v_{sig}} = \frac{r_e}{r_e + R_{sig}} = \frac{25}{25 + 5\text{k}} = \frac{25}{5.02\text{k}} = \frac{1}{201}$

$= 0.004975$

$A_{vo} = \frac{\alpha R_C}{r_e} = \frac{.99 \times 8\text{k}}{25\Omega} = \boxed{316.8 \text{ V/V}}$

(Note +ve sign)

$A_v \text{ (with load)} = \frac{\alpha (R_C \parallel R_L)}{r_e} = \frac{.99 (3.0769\text{k})}{25} = \boxed{121.84 \text{ V/V}}$

$$R_{out} = R_C = 8\text{K}\Omega$$

(5)

$$A_{is} = \frac{-i_{ie}}{i_i} = -\frac{\alpha i_e}{-i_e} = \alpha = 0.99$$

$$G_v = \left(\frac{v_i}{v_{sig}} \right) \times A_v$$


$$= \frac{1}{201} \times 121.84$$

$$= \boxed{0.606 \text{ v/v}}$$

Note that due to input impedance mismatch so much signal is lost in R_{sig} that overall voltage gain < 1 . So we are better off without an amplifier since this amplifier gain < 1 or it is an attenuator.

Problem to be solved in Class about CC Configuration (6)

(Emitter Follower)

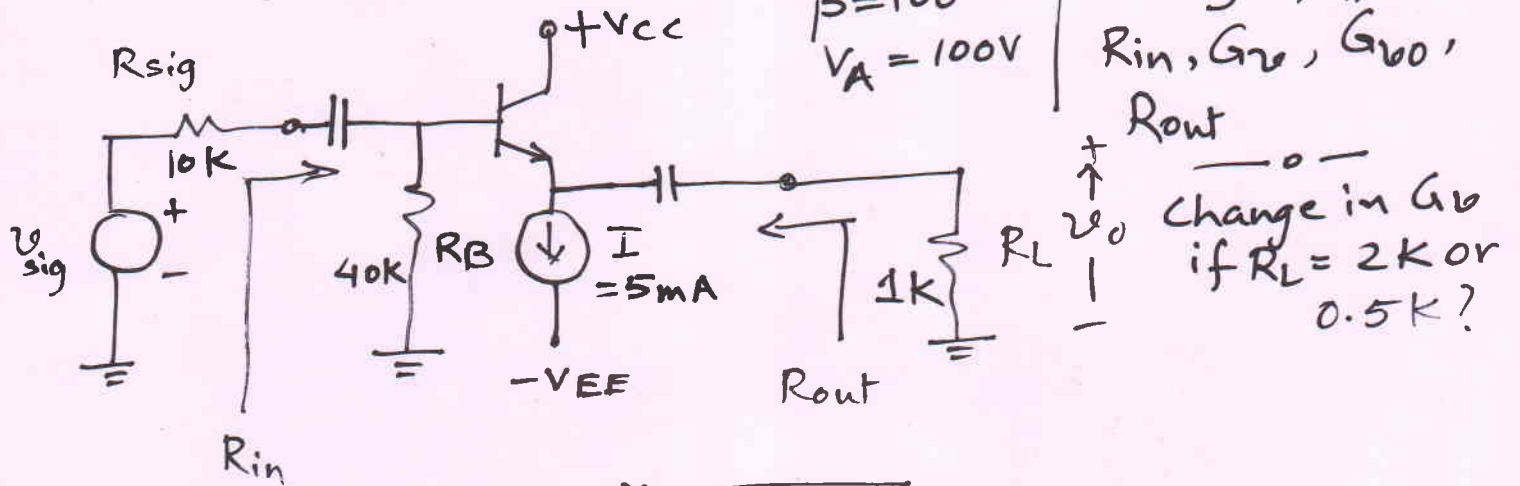

$$I_E = 5mA \quad I_C = 5mA \times 0.99 = 4.95mA$$

$$g_m = I_C / V_T = 4.95mA / 25mV = 198 mS$$

$$r_e = \frac{1}{g_m} = 5.05 \Omega$$

$$R_{ib} = (1 + \beta) [r_e + r_o \parallel R_L]$$

$$r_o = V_A / I_C \approx 100 / 4.95 = 20.2K$$

$$\therefore R_{ib} = (101) [5\Omega + 20.2K \parallel 1K]$$

$$= 101 [957.8] = 96.741K$$

(Note Such a high R_{ib}).

$$R_{in} = R_B \parallel R_{ib} = 40K \parallel 96.741K = 28.29K$$

$$G_v = \left(\frac{R_B}{R_{sig} + R_B} \right) \cdot \frac{(r_o \parallel R_L)}{\frac{(R_{sig} \parallel R_B)}{\beta + 1} + r_e + (r_o \parallel R_L)}$$

$$= (0.8) \frac{0.952K}{\frac{32K}{101} + 5\Omega + 0.952K}$$

$$= 0.8 \frac{0.952 \text{ k}}{0.316 \text{ k} + 0.005 \text{ k} + 0.952 \text{ k}}$$

$$= 0.8 \times \frac{0.952 \text{ k}}{1.274 \text{ k}}$$

$$G_v = \boxed{0.598 \text{ V/V}} \quad \text{For } R_L = 1 \text{ k}$$

G_{vo} is overall voltage Gain when $R_L = \infty$

$$G_{vo} = \left(\frac{R_B}{R_{sig} + R_B} \right) \left(\frac{r_o}{\left(\frac{R_{sig} \parallel R_B}{1 + \beta} \right) + r_e + r_o} \right)$$

$$= 0.8 \frac{20.2 \text{ k}}{\frac{32 \text{ k}}{101} + 5 \Omega + 20.2 \text{ k}}$$

$$= 0.8 \frac{20.2 \text{ k}}{0.316 \text{ k} + 0.005 \text{ k} + 20.2 \text{ k}} = 0.8 \times \frac{20.2 \text{ k}}{20.5 \text{ k}}$$

$$\boxed{G_{vo} = 0.788 \text{ V/V}}$$

Resistance seen from output R_{out}

$$\begin{aligned} R_{out} &= r_o \parallel \left(r_e + \frac{R_{sig} \parallel R_B}{\beta + 1} \right) \\ &= 20.2 \text{ k} \parallel \left(5 \Omega + \frac{8 \text{ k}}{101} \right) = \frac{20.2 \text{ k} \parallel 84.2}{\text{}} \\ &= \boxed{83.85 \Omega} \end{aligned}$$