

Lab-4 Analog Circuits


Bipolar Junction Transistor (BJT): Experiment List

In this session you will perform BJT based practical's using LTSpice. Based on the class lecture perform the following exercises. In your lab-book, remember to write your steps/methods, and the observations/results. The TA's shall sign and grade at the end of each lab. Discuss with your group mates. If you have any difficulty, you may consult TAs.

Note: LTSpice graphs data can be exported to excel sheet using the **export command**. You can then draw the graph as per requirement. Use 2N3904 npn for all the exercises.

1. Simulate a BJT circuit to get the input and output characteristics curves.

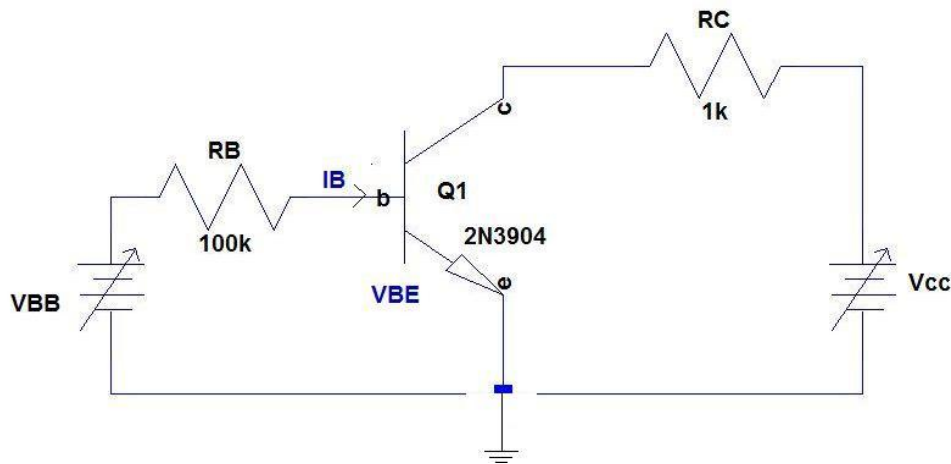
(A) Circuit setup for input characteristics:



- Hook up the circuit as shown in the figure above.
- Keep V_{CC} fix at 0V (Or do not connect V_{CC})
- Increase V_{BB} from 0V to 20V, note down readings of base current I_B and base to emitter voltage V_{BE} in the observation table.
- Repeat above procedure for $V_{CC} = +5V$ and $V_{CC} = +10V$
- Draw input characteristics curve. Plot V_{BE} on X axis and I_B on Y axis.

Note: In the analysis type select DC Sweep.

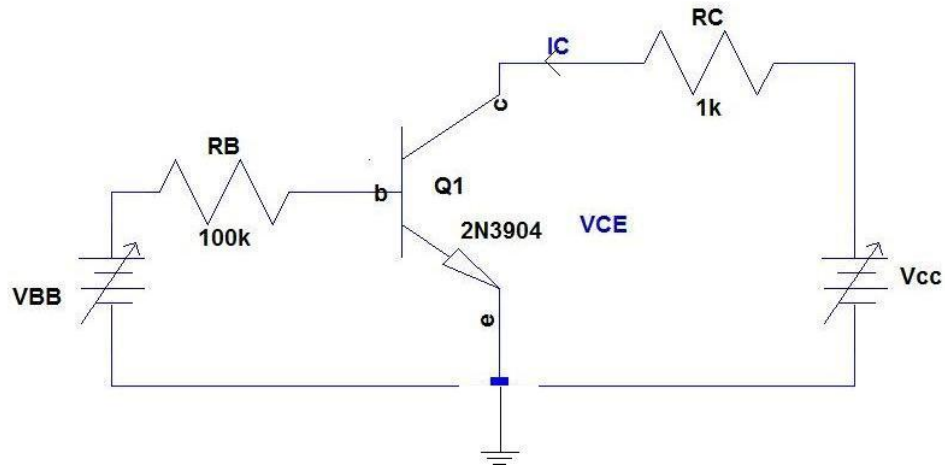
(B) Circuit setup for output characteristics:



- i. Connect circuit as shown in the circuit diagram.
- ii. Keep base current fix (Initially 0)
- iii. Increase V_{CC} from 0V to 20V, note down readings of collector current I_C and collector to emitter voltage V_{CE} in the observation table.
- iv. Repeat above procedure for base currents $I_B = 5\mu A, 50\mu A, 100\mu A$. Increase base current by increasing V_{BB} .
- v. Draw output characteristics curve. Plot V_{CE} on X axis and I_C on Y axis.

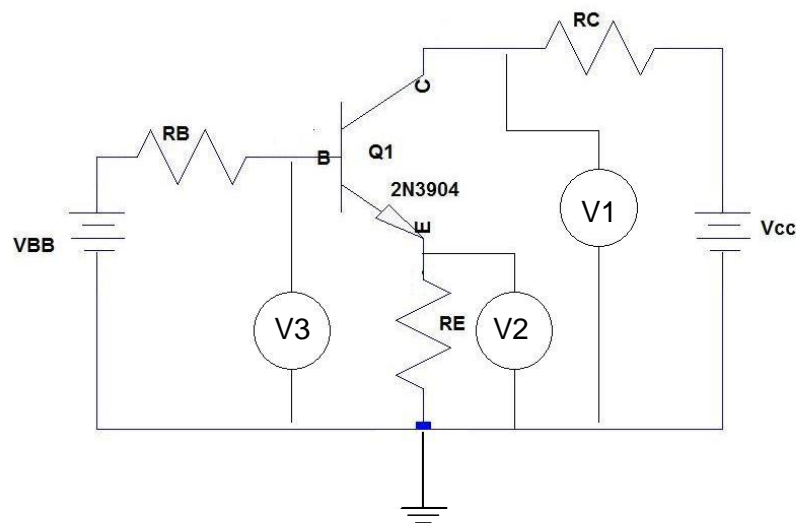
2. Determining the Operating Region of a BJT.

Specify the operating region of the transistor in the following cases. Use LTSpice measurements or manual calculation where required.



- (A) $V_{BB} = 4\text{ V}$, $V_{CC} = 12\text{ V}$, $R_B = 40\text{ k}\Omega$, $R_C = 1\text{ k}\Omega$, $R_E = 321\text{ }\Omega$, Measure V_1 , V_2 and V_3 .
- (B) $V_{BB} = 0$, $V_{CC} = 12\text{ V}$, $R_B = 40\text{ k}\Omega$, $R_C = 1\text{ k}\Omega$, $R_E = 500\text{ }\Omega$.
- (C) Data: $V_1 = V_B = 2.7\text{ V}$, $V_2 = V_E = 2\text{ V}$, $V_3 = V_C = 2.3\text{ V}$.

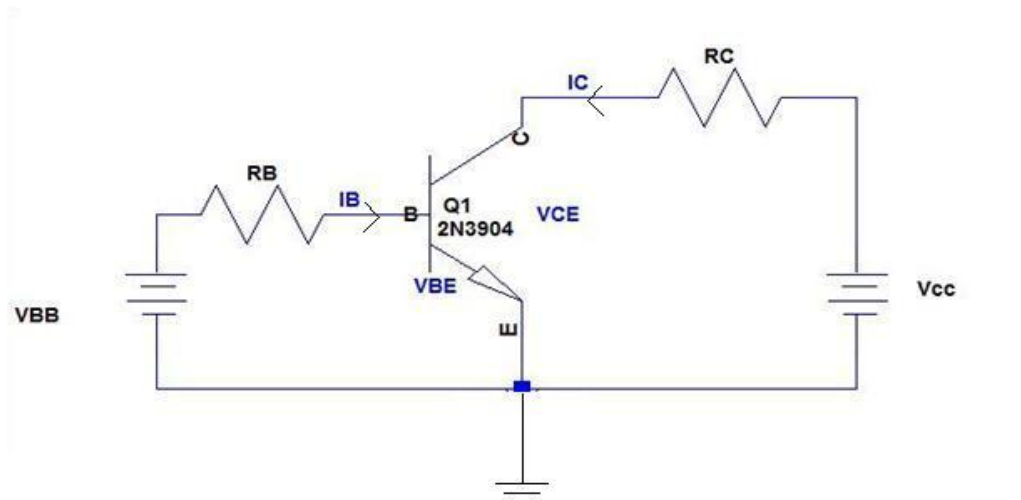3. (A) Determine the DC operating point of the BJT amplifier in the circuit below.




Data: $R_B = 62.7\text{ k}\Omega$, $R_C = 375\text{ }\Omega$, $V_{BB} = 10\text{ V}$, $V_{CC} = 15\text{ V}$.

Hint: First write the load line equation for the collector circuit. To determine the Q point, find the collector curve (from V_{CE} vs I_C graph) that intersects the load line. To do so, you must know the base current.

(B) How would the Q point change if the base current is changed to $100\text{ }\mu\text{A}$?

4. Built a BJT amplifier.

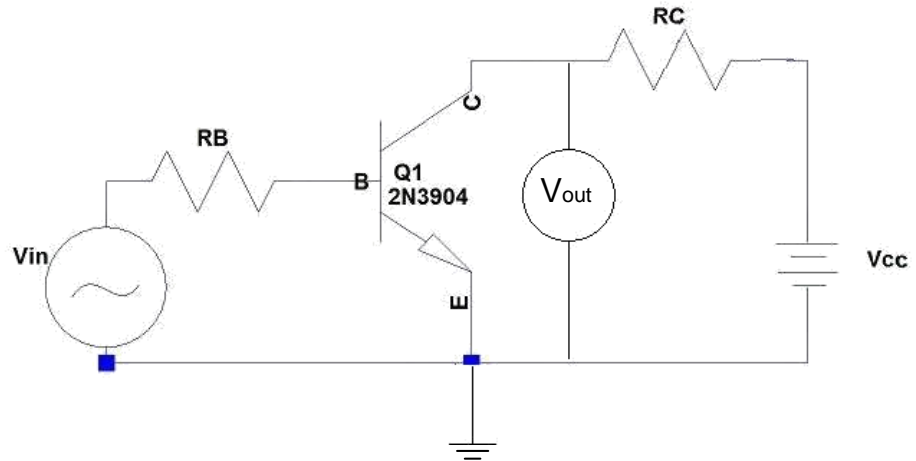(A) Connect the circuit as shown below. $R_B = 5\text{ k}\Omega$, $V_{CC} = 8\text{ V}$, and a 0.65 V DC input voltage with a 10 mV 10 kHz sine wave on top. Perform a transient analysis lasting about 1 ms with $1\text{ }\mu\text{s}$ time steps.



Plot V_{out} and V_{in} waveforms. The output waveform should be an amplified version of the input wave.

- (B) Explain why and what happens if you change (increase and decrease) the DC voltage for either V_{in} or V_{CC} ?
- (C) Explain why and what happens if you change the resistor value?
- (D) Explain why and what happens if you change the transistor model or change to a pnp transistor?