

$$A_d = 100 \quad A_{cm} = 0.01$$

$$V_{i1} = 1V + 5mV \times \sin(\omega t)$$


$$V_{i2} = 1V - 5mV \times \sin(\omega t)$$

$$V_{id} = V_{i1} - V_{i2} = 10mV \times \sin(\omega t)$$

$$V_{ic} = \frac{V_{i1} + V_{i2}}{2} = 1V$$

$$V_o = A_d V_{id} + A_{cm} V_{ic}$$


$$= 1V \times \sin(\omega t) + 10mV$$

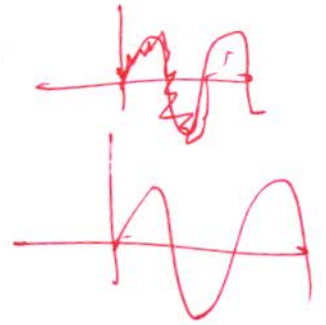

Whatever is common is rejected & whatever is different is amplified.

Application.

① Noise Cancellation.

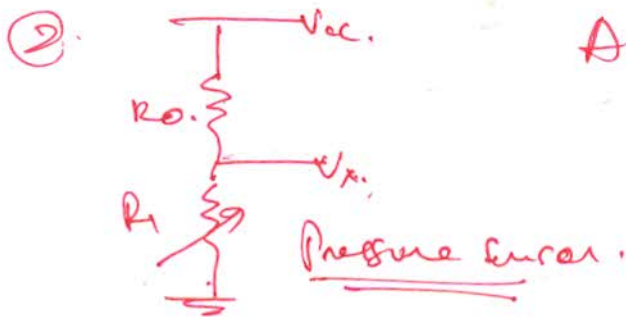

Amplifying small signal immersed in a large signal.

$$V_x = 0.5V_{cc} + 0.5V_{cc} \times \frac{\Delta R}{R_0}$$


Unwanted component. ← Interested in this signal.

$$V_{cc} = 5V \quad \frac{\Delta R}{R_0} = 1\%$$

$$V_x = 2.5V + 25mV \quad (\text{Both signal and dc})$$

If Amplified then will saturate & can't detect signal.

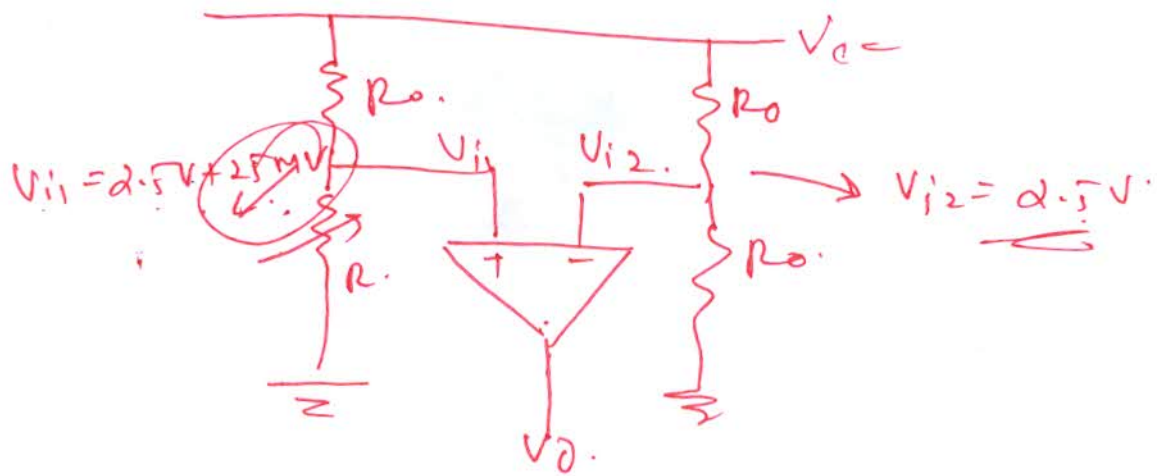Differential Amplifier is a natural  $\frac{1}{2}$  rule.



only the signal will appear at the output & the common mode signal will be cancelled.