
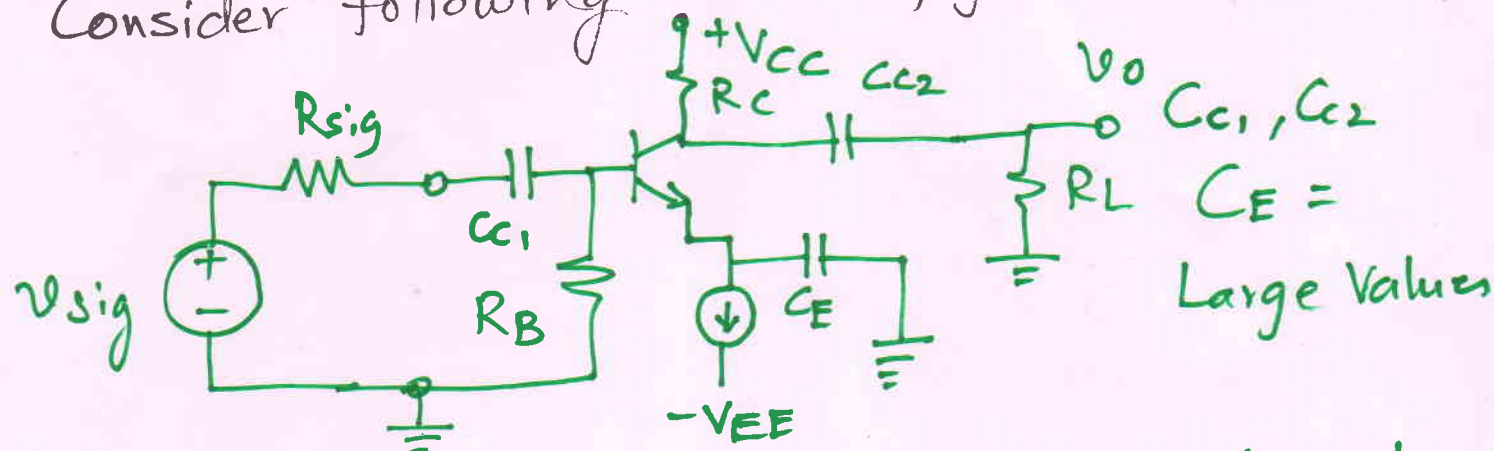


FREQUENCY RESPONSE OF THE COMMON EMITTER AMPLIFIER ①

Consider following CE configuration:

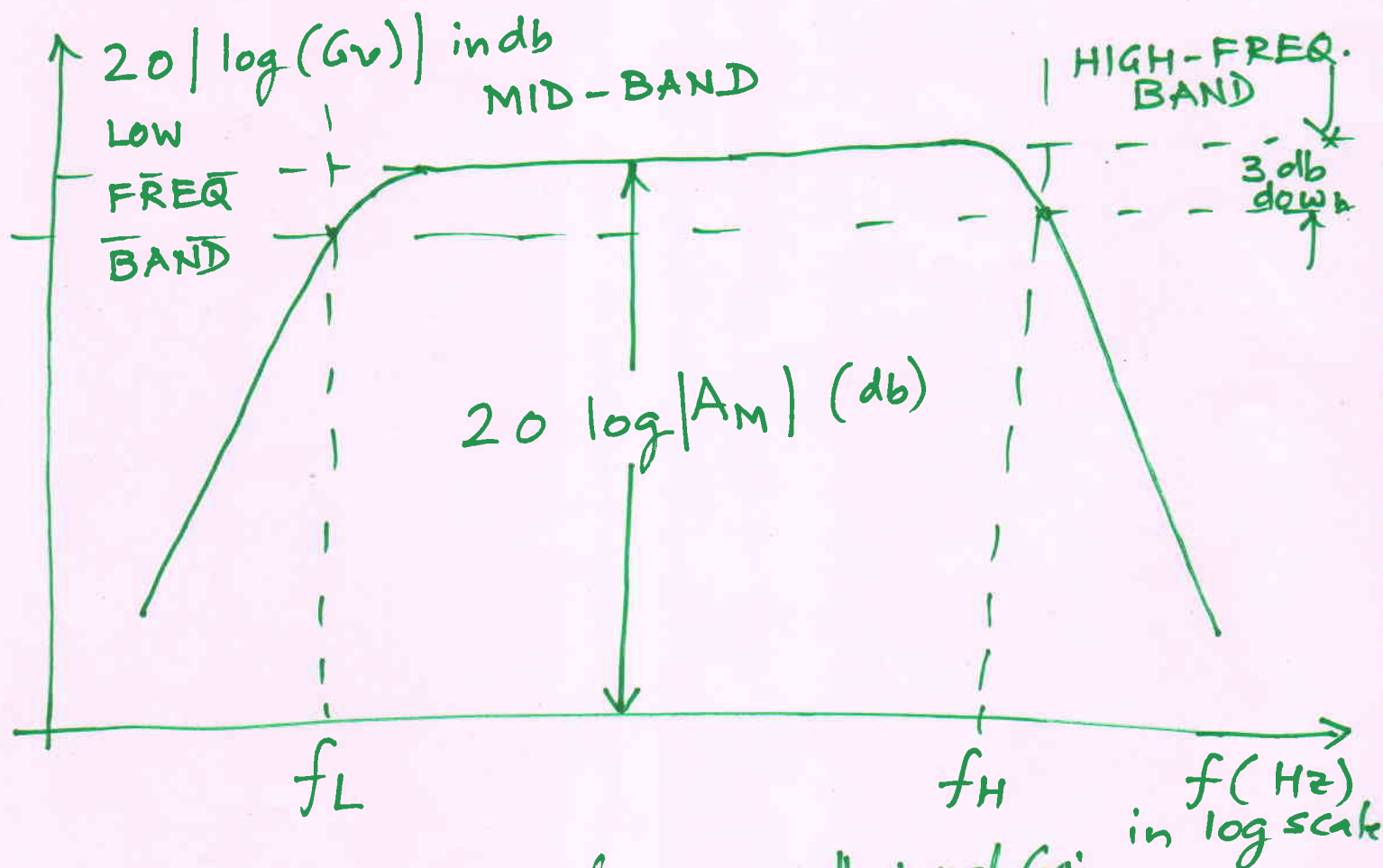

Normalized G_v in db plotted on Log f scale:



What we considered as small signal Gain or G_v can now be called as MID BAND GAIN A_m

$$A_m = \frac{v_o}{v_{sig}} = \frac{(R_B \parallel r_{\pi})}{(R_B \parallel r_{\pi}) + R_{sig}} \cdot g_m (r_o \parallel R_C \parallel R_L)$$

As the frequency increases, C_{π} and C_{μ} start exercising their effect and the gain starts reducing. The frequency at which gain falls to 3 db of midband gain or 0.707 of A_M is called as Upper Cutoff Frequency f_H = A_M in db - 3 db

$$\text{Gain at } f_H = |A_M| \text{ in db} - 3 \text{ db} \\ = \frac{|A_M|}{\sqrt{2}} = |A_M| \times 0.707$$

At low frequencies C_E offers non-zero reactance and behaves like emitter degenerated which means V_o is reduced. Similarly at low frequencies C_{c1} and C_{c2} do not behave like perfect short circuit but offer series reactance (like R_{sig}) and drop off a portion of signal input or signal output voltage. This reduces V_o at lower frequency. The frequency on lower side at which $|G_v|$ or $|A_v|$ falls to 0.707 of A_M is called f_L or LOWER CUTOFF FREQUENCY.

Gain at $f_L = A_M$ in db - 3 db

(3)

$$= \frac{|A_M|}{\sqrt{2}} = |A_M| \times 0.707$$

We define a term BANDWIDTH OF an amplifier as

$$BW = f_H - f_L$$

BW represents usable frequency band or zone or area or spectrum over which amplifier offers "reasonable" or "nearly constant" voltage gain.

A figure of Merit for any Amplifier is defined as GAIN BANDWIDTH product


$$GB = |A_M| \times BW$$

Later on, we will see that- to get larger bandwidth, we can sacrifice voltage gain.

HIGH FREQUENCY RESPONSE OF A CE (4)


AMPLIFIER

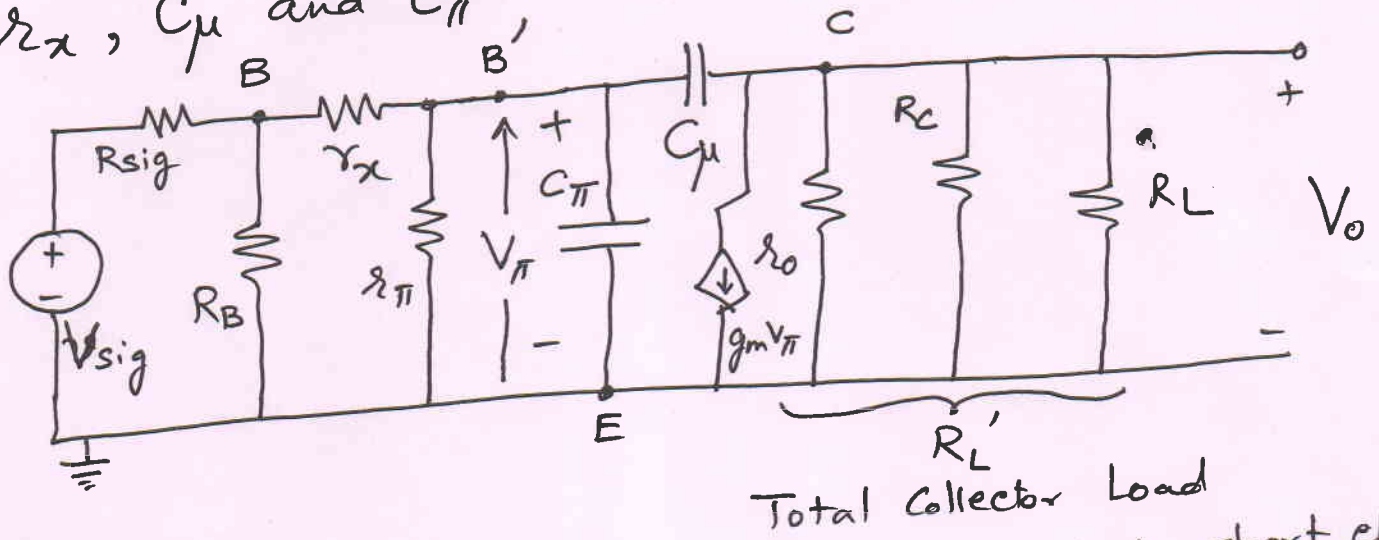Draw the high frequency model incorporating r_x , C_μ and C_π ;



At high frequency C_c , C_{c2} and C_E will be short ckt.
 Note that V_{sig} & R_{sig} drive a load of $r_x + (r_\pi \parallel C_\pi)$.
 The part of V_{sig} which appears across B' & E is V_π .
 This is true input to amplifier. This multiplied by g_m gives us the magnitude of current source between Collector & Emitter i.e. output terminals. There are 3 resistors in parallel in output circuit R_c , r_o & R_L .
 R_L' represents equivalent value of these 3 loads.
 The output voltage $V_o = g_m \cdot V_\pi \cdot R_L'$ without taking into consideration feedback or 'leakage' through C_μ .

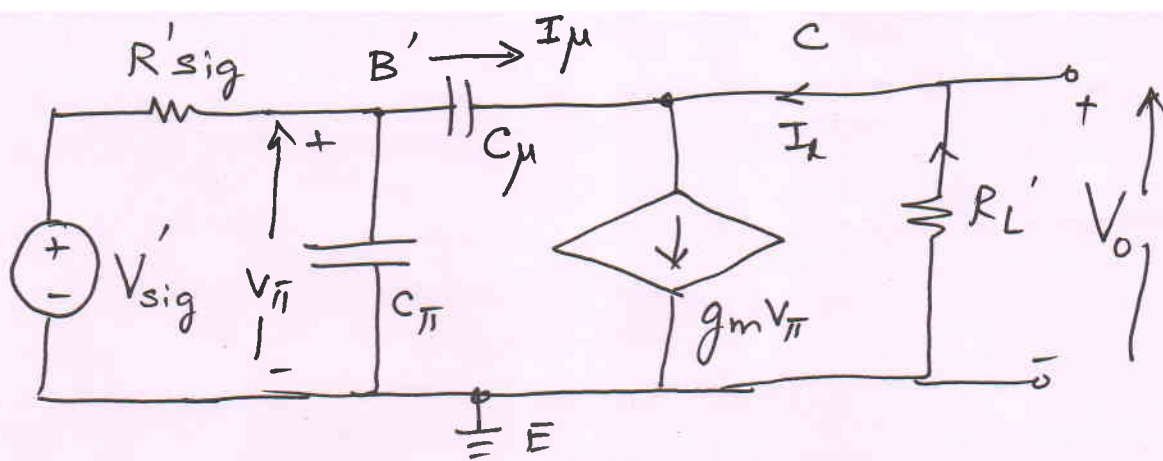To solve, let us replace all resistors in input side by a single R_{TH} or Thevenin Equivalent as follows; with V_{TH} as Thevenin Voltage source.




(5)

$$V_{sig}' = V_{sig} \left(\frac{R_B}{R_B + R_{sig}} \right) \cdot \left(\frac{r_{\pi}}{r_{\pi} + r_x + (R_{sig} \parallel R_B)} \right)$$

$$R_L' = r_o \parallel R_C \parallel R_L$$

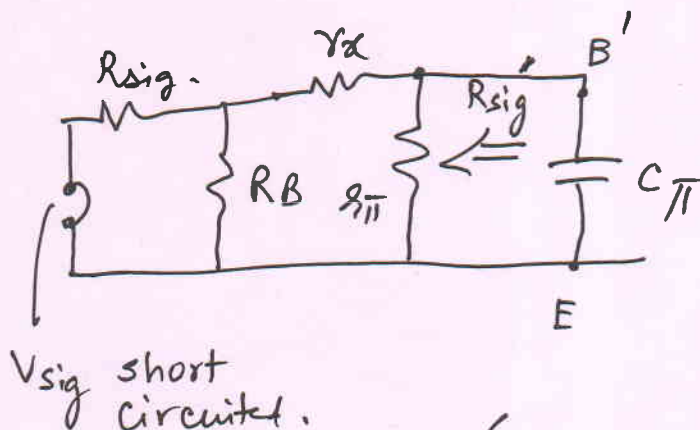R_{sig}' = resistance seen from C_{π} towards left with all voltage sources short circuited & current sources open circuited.



$$R_{sig}' = r_{\pi} \parallel \left\{ (r_x + R_{sig} \parallel R_C) \right\}$$

Now we will represent C_{μ} by an equivalent capacitance C_{eq} between B' & E in shunt with C_{π} .

At node C load $I_L = g_m V_{\pi} - I_{\mu}$
 At 3 db point, f_H we can assume that $g_m V_{\pi}$ is quite high as compared to I_{μ} & $I_L \approx g_m V_{\pi}$
 $\therefore V_o \text{ approx.} = g_m V_{\pi} \cdot R_L$ --- (1)

Approximate Voltage Gain from B' to C is (6)
 Same as midband gain $-g_m R_L'$. In s plane,

$$I_\mu = s C_\mu (V_\pi - V_o)$$

= ~~reactance~~ ^{sustenance} \times voltage across C_μ .


$$= s C_\mu [V_\pi - (-g_m R_L' V_\pi)]$$

$$= s C_\mu [1 + g_m R_L'] V_\pi$$

$$= s C_{eq} \cdot V_\pi$$


where $C_{eq} = C_\mu [1 + g_m R_L']$

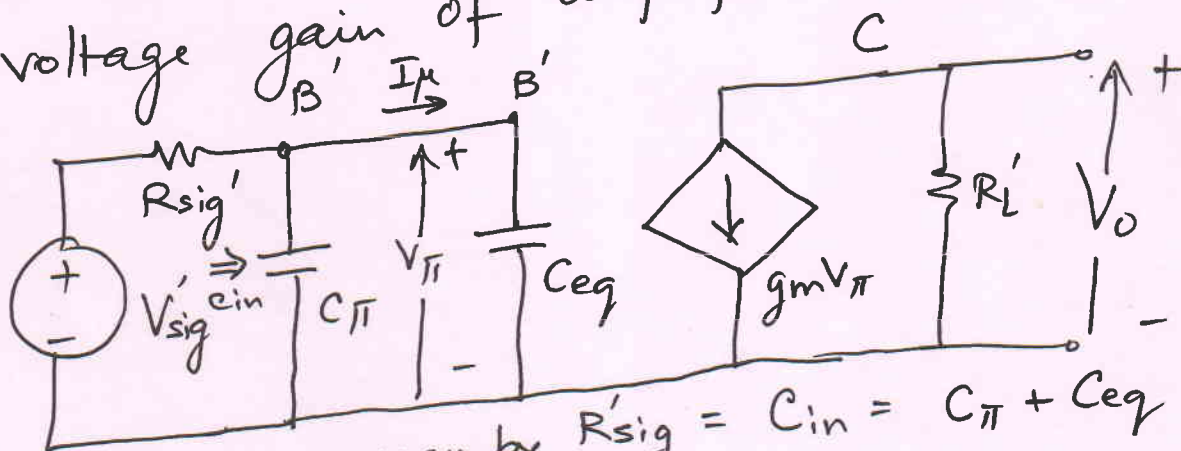Note that $\because g_m R_L'$ could be 10 to 200, a small C_μ appears as very large capacitor in shunt with C_π . Hence a small C_μ gets magnified & becomes more dominant than C_π due to high voltage gain of amplifier. The net circuit is



Total C_{in} seen by $R_{sig}' = C_{in} = C_\pi + C_{eq}$
 $C_{in} = C_\pi + C_\mu (1 + g_m R_L')$

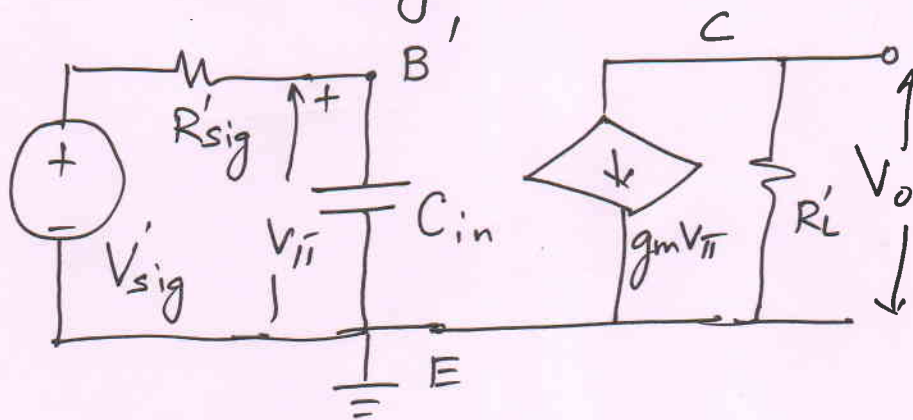Now we have reduced input side to ⑦
a single time constant circuit having
a resistor R'_{sig} and capacitor C_{in}



$$V_{\pi} = V'_{sig} \frac{1}{1 + s/\omega_0}$$

$$\text{where } \omega_0 = \frac{1}{R'_{sig} \cdot C_{eq}} = \frac{1}{R'_{sig} \cdot (C_{\pi} + (1 + g_m R'_L) C_{\mu})}$$

So we calculate overall voltage Gain

$$\frac{V_o}{V_{sig}} = - \left[\left(\frac{R_B}{R_B + R_{sig}} \right) \cdot \left(\frac{r_{\pi} g_m R'_L}{r_{\pi} + r_x + (R_{sig} \parallel R_B)} \right) \right] \left(\frac{1}{1 + \frac{s}{\omega_0}} \right)$$

$$= \frac{A_M}{1 + \frac{s}{\omega_0}}$$

Note that r_x is
also taken into
account here.

where [] quantity is A_M or midband gain.

Notes :

(8)

$$f_H = \frac{\omega_0}{2\pi} = \frac{1}{2\pi \cdot C_{in} \cdot R'_{sig}}$$

1. If R_{sig} is quite small compared to R_B i.e. if $R_B \gg R_{sig}$ and semiconductor material resistance $r_x \ll R_{sig}$ then effective resistance $R'_{sig} \approx r_{\pi} \parallel R_{sig}$. Now if $R_{sig} \gg r_{\pi}$ then f_H is decided almost alone by r_{π} . If $R_{sig} \approx r_{\pi}$ then f_H is largely affected by R_{sig} . Note R_{sig} is not an amplifier property, it is the property of signal source. Thus a high R_{sig} will ~~lower~~ increase R'_{sig} and produce lower value of f_H for the same amplifier.
The best case is where R_{sig} is very small & r_{π} is very large & then f_H will be very high.
2. $C_{eq} = (1 + g_m R'_L) C_{\mu}$. The factor $(1 + g_m R'_L)$ is known as Miller Multiplier due to Miller Effect. Due to this CE amplifier has high C_{in} and \therefore low f_H .
3. We have neglected I_{μ} as compared to $g_m V_{\pi}$. Actually at higher frequencies this is not valid & actual f_H is lower than estimated.
4. If R'_L is reduced then C_{eq} goes down & f_H goes up.