

State Encoding

- States which have the same NS for a given i/p should be clubbed together. $X=1$ column.
- States which are the NS of the same state should be clubbed together.
- States which have the same o/p for a given i/p should be clubbed together.

Q_1, Q_2, Q_3

Q_1	0	1
Q_2		
00	S_0	S_1
01		S_2
11	S_5	S_3
10	S_6	S_4

(S_0, S_1, S_4, S_6)
 (S_2, S_3, S_5)

$S_1, S_2 \rightarrow S_4$
 $S_3, S_4 \rightarrow S_5$
 $S_5, S_6 \rightarrow S_0$
 $(1, 2) \quad (3, 4) \quad (5, 6)$
 $(1, 2) \quad (3, 4) \quad (5, 6)$
 S_1, S_2 are NS of S_0
 S_3, S_4 are NS of S_1
 S_5, S_6 are NS of S_4

$S_0 = 000$ $S_3 = 011$
 $S_1 = 100$ $S_6 = 010$
 $S_2 = 101$
 $S_3 = 111$
 $S_4 = 110$

~~Q₁Q₂Q₃~~

	00	01	11	10
00	1	1	0	0
01	x	0	1	x
11	0	0	1	1
10	1	1	0	x

$$Z = Q_3'x + Q_3x'$$

Q_2Q_3

	00	01	11	10
00	0	1	1	0
01	x	1	1	x
11	0	1	1	0
10	0	1	1	x

$$D_2 = Q_2' = Q_1$$

$Q_1Q_2Q_3$

PS	$x=0$	$x=1$	
S0000	S1 100	S2 101	
S1100	S3 111	S4 110	
S2101	S4 110	S5 110	
S3111	S5 011	S6 011	
S4110	S6 011	S7 010	
S5011	S7 000	S8 000	
S6010	S8 000	S9 000	

Q_2Q_3

	00	01	11	10
00	0	1	0	1
01	x	0	0	x
11	0	1	1	0
10	0	1	0	x

$$D_3 = Q_3' = Q_2'xQ_1' + Q_2Q_3' + Q_3'x'Q_1'$$

Z ✓


Q_2Q_3

	00	01	11	10
00	1	1	1	1
01	x	1	1	x
11	0	0	0	0
10	0	0	0	x


$$D_1 = Q_1' = Q_2'$$

Chosen for Minter
😊
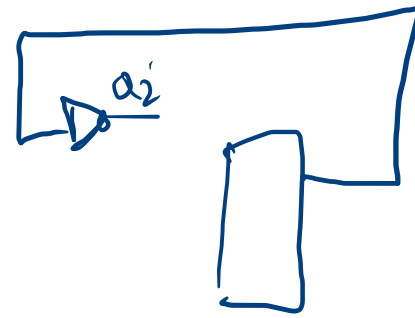
$$\begin{aligned}
 D_1 &= Q_2' \\
 D_2 &= Q_1 \\
 D_3 &= Q_2' \times Q_1' + Q_2 Q_3 Q_1 + Q_3' \times Q_1 \\
 Z &= Q_3' \times X' + Q_3 X
 \end{aligned}$$



Code Converter Circuit:-

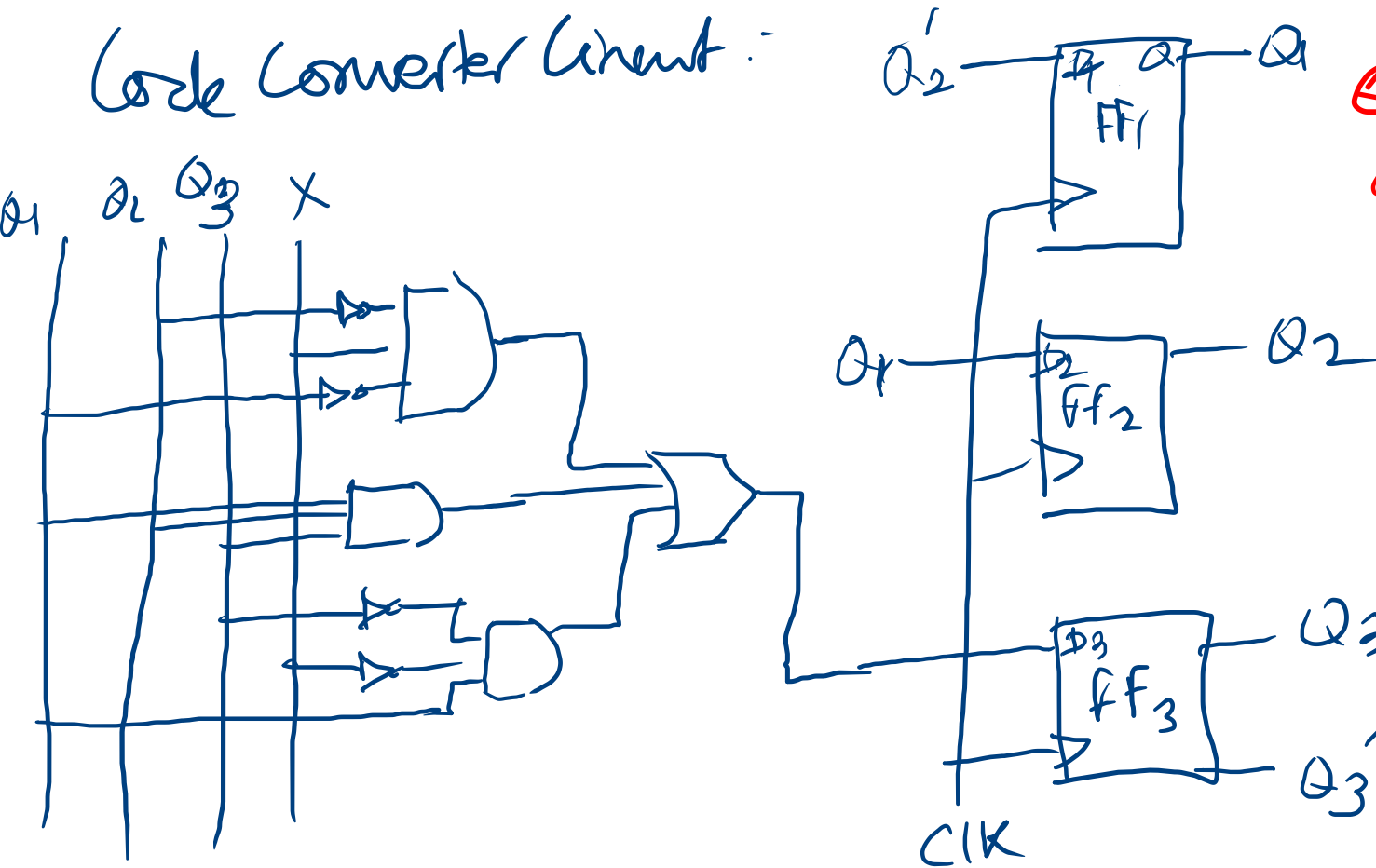

~~Convert~~
all of them to
nand gates -
have bubbles at
i/p & o/p as appropriate
and convert them as
discussed previously.

