

See Fig. 6-10. Note that since the voltage source does not remain constant for t > 0 but returns to zero at $t = 1 \mu s$, the traveling waves are zero along portions of the line. For instance, in the 0.75 μs after the leading edge of the original pulse has reached $z = \zeta = 400 \text{ m}$, three-quarters of the pulse has "passed through" $z = \zeta$, taving the trailing edge at z = 350 m; during the same time the first reflected pulse has reached z = 250 m. The superposition of these two pulses is the two-step distribution shown in Fig. 6-10(b).

Attansmission line [Fig. 6-11(a)] has $R_S = 300 \Omega$, $R_L = 60 \Omega$, $R_C = 100 \Omega$, $u = 400 \text{ m/}\mu\text{s}$, $\zeta = 400 \text{ m}$, and $V_S(t) = 400 u(t) \text{ V}$, where u(t) is the unit step function. Sketch V(0, t) for $0 < t \le 10 \mu\text{s}$.

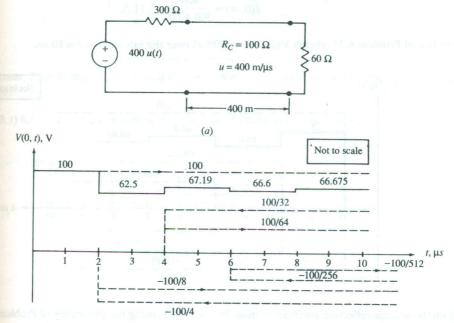


Fig. 6-11

214 CHAPTER 6

■ The voltage reflection coefficients are

$$\Gamma_S = \frac{300 - 100}{300 + 100} = \frac{1}{2}$$
 $\Gamma_L = \frac{60 - 100}{60 + 100} = -\frac{1}{4}$

The initial voltage is

$$V_1^+ = \frac{R_C V_S(0^+)}{R_C + R_S} = \frac{(100)(400)}{100 + 300} = 100 \text{ V}$$

V(0, t) is sketched in Fig. 6-11(b); the steady-state voltage is

$$V(0, \infty) = \frac{60}{300 + 60} \times 400 = 66.67 \text{ V}$$

6.32 For the line of Problem 6.31, sketch I(0, t) for $0 < t \le 10 \mu s$.

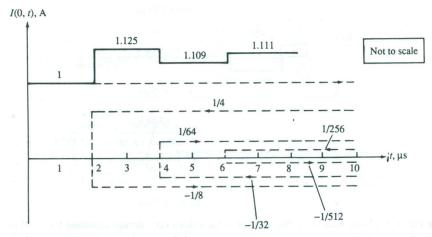


Fig. 6

The current reflection coefficients are the negatives of the voltage reflection coefficients (Problem 6.19), at the initial current is

$$I_1^+ = \frac{400}{300 + 100} = 1 A$$

The required I(0, t) is sketched in Fig. 6-12, where the steady-state current is

$$I(0, \infty) = \frac{400}{300 + 60} = 1.11 \text{ A}$$

6.33 For the line of Problem 6.31, sketch $V(\zeta, t) = V(400, t)$ over the interval $0 < t \le 10 \ \mu s$.

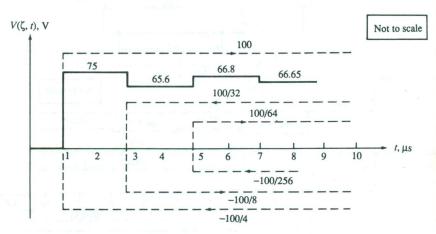


Fig. 6

With the voltage reflection coefficients from Problem 6.31, using the procedure of Problem 6.29 we obtain the plot shown in Fig. 6-13.