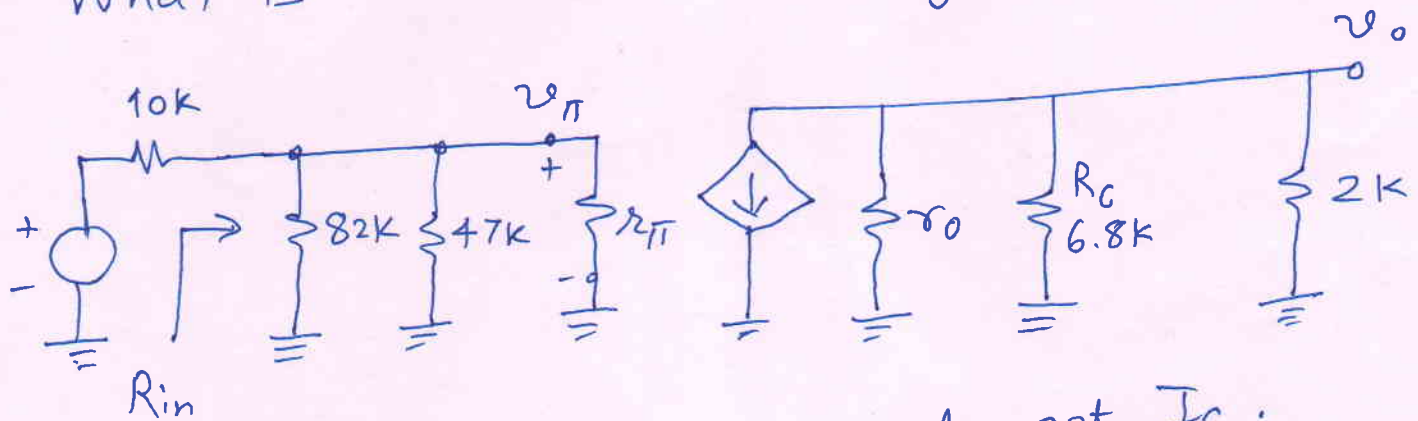


3.132


The original resistor values have been multiplied by 3 to get higher gain. They are

$$R_1 = 82K, R_2 = 47K, R_E = 3.6K, R_C = 6.8K$$

What is the overall voltage Gain?



First solve the DC currents to get I_C .

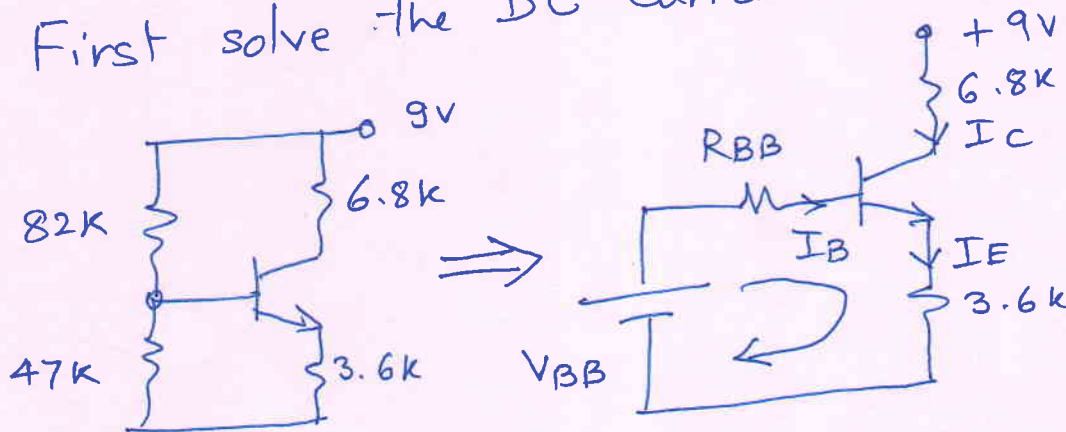

$$V_{BB} = \left(\frac{47K}{47K + 82K} \right) \cdot 9V = \boxed{3.279V}$$

$$R_{BB} = 47K \parallel 82K = \boxed{29.8K}$$

KVL in Loop.

$$3.279V - I_B \cdot 29.8K - 0.7V - (1+100)3.6K \cdot I_B = 0$$

$$\therefore I_B = 6.55\mu A \quad I_C = 0.655mA$$

Note I_C is now less than 2mA of first Case.

For $I_c = 0.655 \text{ mA}$, Calculate g_m , r_{π} & r_o (2)

$$g_m = 0.655 \text{ mA} / 25 \text{ mV} = \boxed{26.2 \text{ mV}}$$

$$r_{\pi} = \beta / g_m = 100 / 26.2 = \boxed{3.816 \text{ k}\Omega}$$

$$r_o = V_A / I_c = 100 / 0.655 = \boxed{152.63 \text{ k}\Omega}$$

Note that g_m has reduced but other two has increased. That will reduce loading.

$$R_{in} = R_1 \parallel R_2 \parallel r_{\pi} = 47 \text{ k} \parallel 82 \text{ k} \parallel 3.816 \text{ k} \\ = 3.383 \text{ k}$$

$$v_{be} = \left(\frac{3.383 \text{ k}}{3.383 \text{ k} + 10 \text{ k}} \right) \cdot v_{sig}$$

$$= 0.252 \cdot v_{sig}$$

$$\text{Total Collector Resistance } R_{eq} = R_c \parallel r_o \parallel R_L$$

$$= 6.8 \text{ k} \parallel 152.63 \text{ k} \parallel 2 \text{ k} = 1.523 \text{ k}$$

$$v_o = -g_m v_{be} \cdot R_{eq}$$


$$= -26.2 \text{ mV} \cdot 1.523 \text{ k} (0.252) v_{sig}$$

$$\therefore \frac{v_o}{v_{sig}} = G_v = -26.2 \times 1.523 \times 0.252 \\ = \boxed{-40.08}$$

GAIN HAS INCREASED BY 5 TIMES
BY IMPROVING RESISTANCES THOUGH
TRANSCONDUCTANCE WAS REDUCED.

3.136 v_{sig} is sinusoidal small signal source.
 $\beta = 100$. Find R_{in} and G_v . If v_{be} is
 to be limited to 5 mV, what is the largest signal
 that can be applied at input? What is the
 corresponding output voltage of signal?

4
 pg. 3
 not there

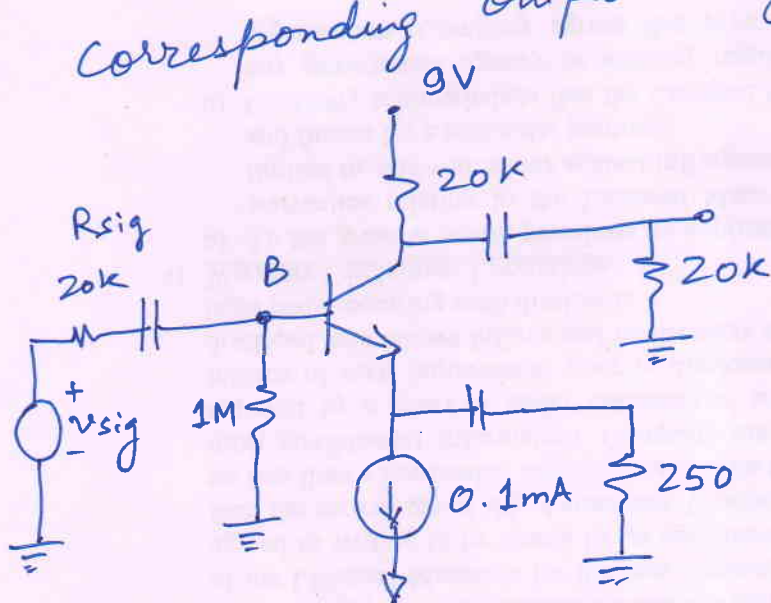


$$I_E \approx I_C = 0.1 \text{ mA}$$

$$g_m = I_C / V_T = 0.1 \text{ mA} / 25 \text{ mV}$$

$$= \boxed{\frac{1}{250}} = 4 \text{ mS}$$

$$r_e = \frac{1}{g_m} = 250 \Omega$$

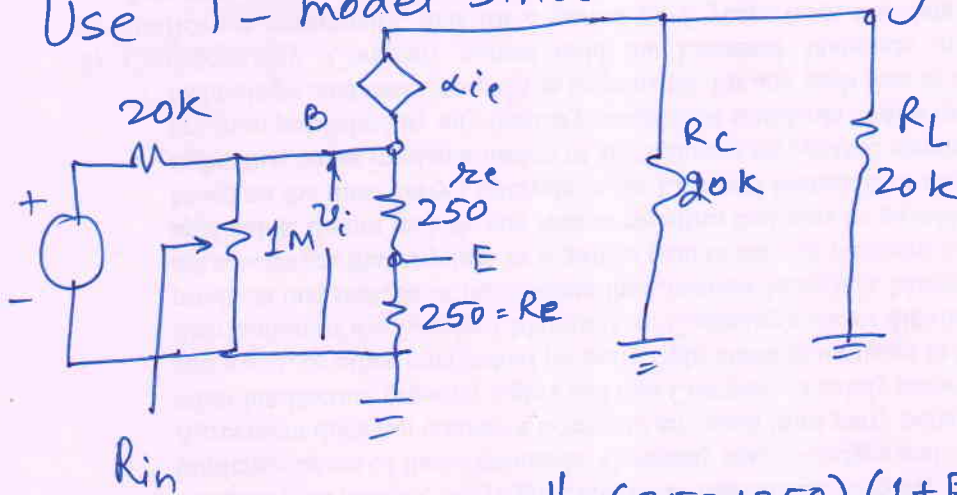Use T-model since emitter is grounded thru 250Ω



$$R_{in} = 1 \text{ M} \parallel (250 + 250)(1 + \beta)$$


$$= 1 \text{ M} \parallel 0.5 \text{ k} \times 101$$

$$= 1 \text{ M} \parallel 50.5 \text{ k}$$

$$R_{in} = 1000 \text{ k} \parallel 50.5 \text{ k} = \boxed{48.07 \text{ k}}$$

Draw Thevenin Equivalent Circuit For

(5)

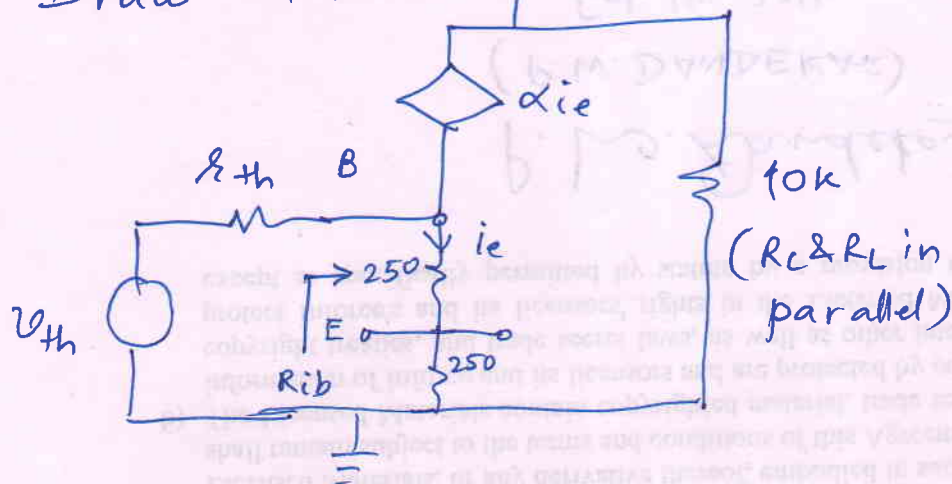

$$v_{th} = \frac{1M \times 20k}{1M + 20k} \left(\frac{1M}{1M + 20k} \right) v_{sig} = \frac{0.718}{19.6} v_{sig} = 0.980 v_{sig}$$

$$R_{th} = \frac{1M \times 20k}{1M + 20k} = 19.607k$$

$$v_i = \frac{R_{ib}}{R_{ib} + R_{th}} \cdot v_{th}$$

$$= \frac{(250+250) \cdot (1+100)}{(250+250)(1+100) + 19.607k} \cdot 0.980 v_{sig}$$

$$= 0.720 \times 0.980 \times v_{sig}$$

$$= 0.706 v_{sig}$$

$$i_e = \frac{v_i}{R_e + R_e} = \frac{v_i}{250 + 250} = \frac{v_i}{0.5k} = 2 \cdot v_i \frac{V}{k\Omega}$$

$$v_o = -\alpha i_e \cdot 10k$$

$$v_o = -\alpha \cdot 10k (2 \cdot v_i) \quad v/k\Omega$$

$$= -20 v_i$$

$$= -20 \times 0.706 \times v_{sig}$$

$$\therefore \frac{v_o}{v_{sig}} = -20 \times 0.706 = \boxed{-14.12}$$

Proper Amplifier's Voltage Gain

$$A_v = \frac{-\alpha (R_c \parallel R_L)}{(R_e + r_e)}$$

$$= -\alpha \frac{(20k \parallel 20k)}{(250\Omega + 250\Omega)} = \frac{10k}{500\Omega} = \boxed{-20}$$

Note: Amplifier's Voltage Gain -20 has reduced to -14.12 due to loading at input side by a factor 0.706.


$$v_{be} = \frac{r_e}{r_e + R_e} \cdot v_i = \frac{250}{250 + 250} \cdot v_i$$

$$= 0.5 v_i$$

So if max. v_{be} can be 5 mV then max. v_i can be 10 mV. For this $v_o = 10mV(-20) = \boxed{-200 mV}$

$$\text{Maximum } v_{sig} = 10mV / 0.706 = \boxed{14.16mV}$$

P3.137.

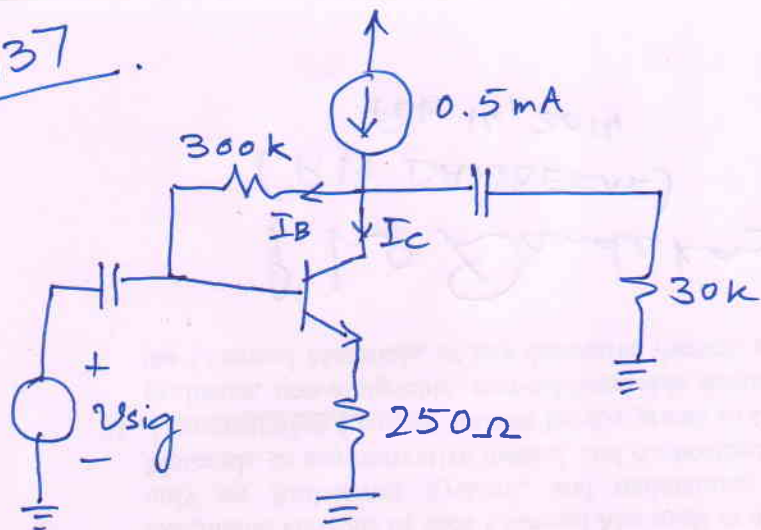

Neglect r_o . (7)

$$\beta = 100$$

$$I_C \approx 0.5 \text{ mA}$$

Find V_C, V_B, V_E

Find I_C

$$I_C + I_B = 0.5 \text{ mA} = 500 \mu\text{A}$$

$$\text{or } 100 \cdot I_B + I_B = 500 \mu\text{A} \therefore I_B = 500/101 = \boxed{4.95 \mu\text{A}}$$


$$I_C = 4.95 \mu\text{A} \times 100 = \boxed{495 \mu\text{A}}$$

$$\beta = 100 \text{ \& } I_C = 0.5 \text{ mA}$$

$$\therefore g_m = 0.5 \text{ mA} / 25 \text{ mV} = 1/50 = 20 \text{ mS}$$

$$r_e = \frac{1}{g_m} = 50 \Omega$$


Draw T-model.

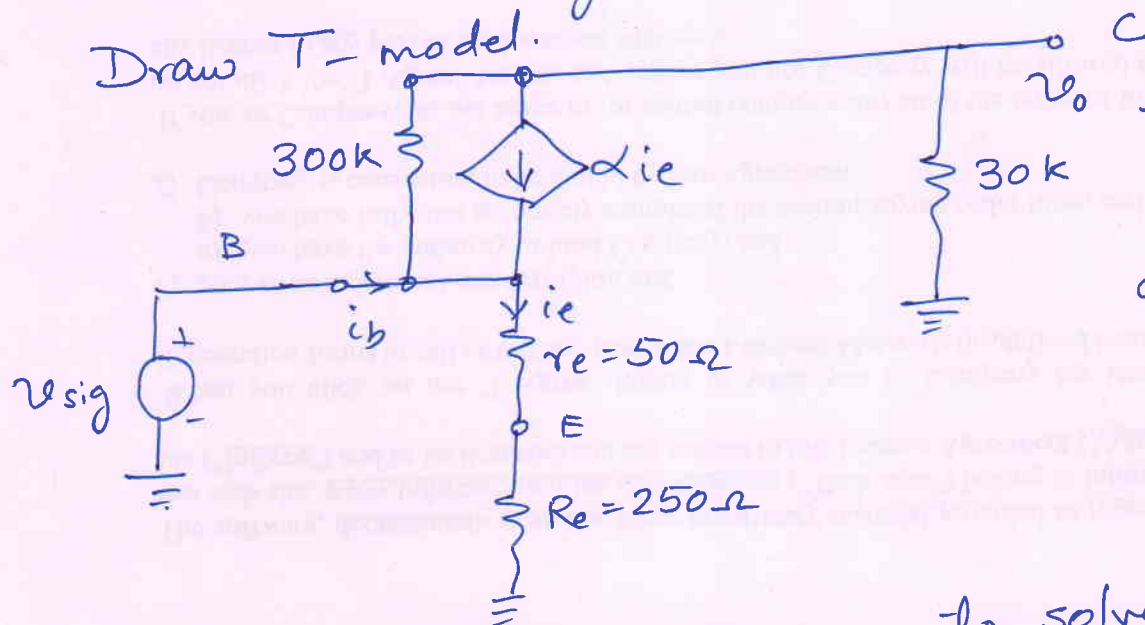

There is no RC and no r_o .

We will use Miller's Theorem to solve the effect of 300k. It is a Output to input connection so it is called as feedback. Since output & input is out of phase, it is called negative feedback.

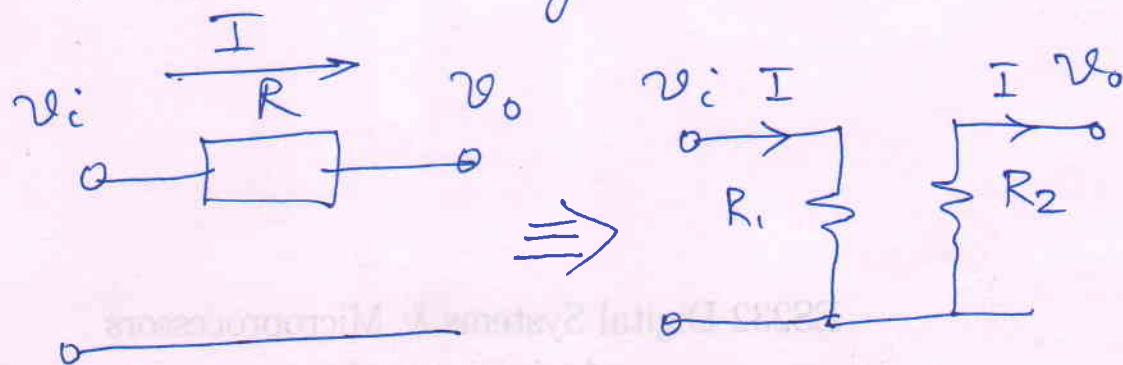If v_o/v_i can be called as A (voltage Gain) 8
 then miller's theorem says that



where $R_1 = R/(1-A)$

and $R_2 = R/(1-\frac{1}{A})$

In our case $R = 300k$. Let us first get an estimate of $A = v_o/v_i$ (without $300k$ connected)

$$A_v = \frac{v_o}{v_i} = -\alpha \frac{(R_c \parallel R_L)}{r_e + R_e}$$

(without $300k$) $= -\frac{30k}{300\Omega} = \boxed{-100}$


$$\therefore R_1 = \frac{300k}{1-(-100)} = \frac{300k}{101} = 2.97k$$

$$R_2 = \frac{300k}{1-(-\frac{1}{100})} = \frac{300k}{1.01} = 297k$$

We calculate A_v with $R_2 \parallel R_L$

$$A_v = -\alpha \frac{(297k \parallel 30k)}{300\Omega} = \boxed{-90.82}$$

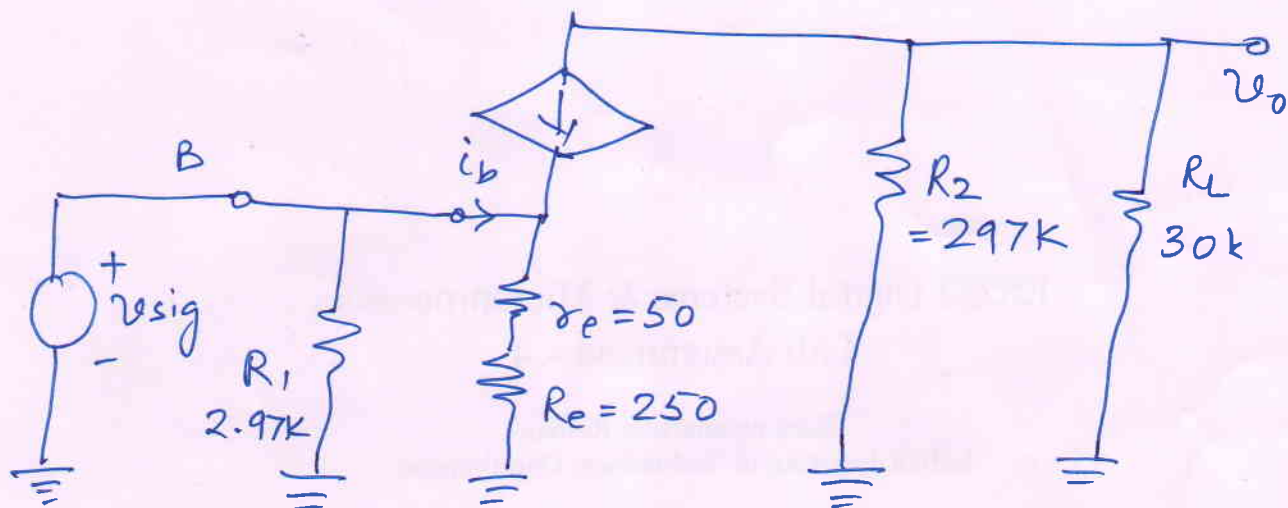T-model with $300k$ represented by Miller Effect Resistors (9)



Note - that there is no effect of $2.97k$ on G_v because v_{sig} can drive $2.97k$ as well as base-emitter without any loading because $R_{sig} = 0$.

Note that $300k$ in shunt $v_o \rightarrow v_i$ is equivalent of roughly $\frac{300k}{\beta}$ in parallel with r_{π} or base-emitter. So a $C \rightarrow B$ resistor reduces input resistance drastically and increases attenuation of input signal due to heavy loading. It gets us lot less v_i for a given v_{sig} .

To calculate all voltages.

10

$$I_E = 0.5 \text{ mA} = 500 \mu\text{A}$$

$$V_E = I_E \cdot R_E = 500 \mu\text{A} \times 0.25 \text{ k} = \boxed{0.125 \text{ V}}$$

$$V_B = V_E + 0.7 = 0.125 + 0.7 = \boxed{0.825 \text{ V}}$$

$$V_C = V_B + I_b \cdot 300 \text{ k} = 0.825 + 5 \mu\text{A} \times 300 \text{ k} = \boxed{2.325 \text{ V}}$$