

07/04/2021

RF behavior of capacitor


Dielectric constant (ϵ_r) \rightarrow Electric permittivity

Complex

$$\epsilon_r = \epsilon_r' + j\epsilon_r''$$


measure of charge retention capacity
of medium

DC eqvt ckt:

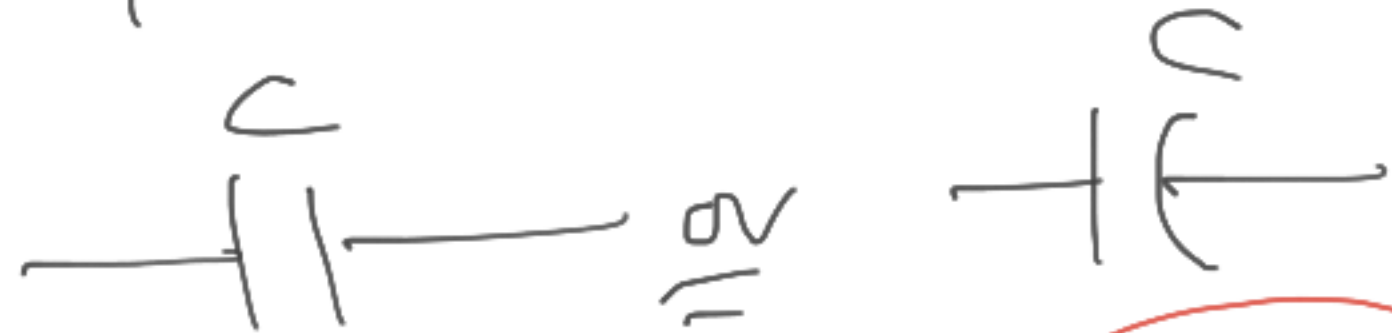


AC eqvt ckt

Resonant or SH ckt

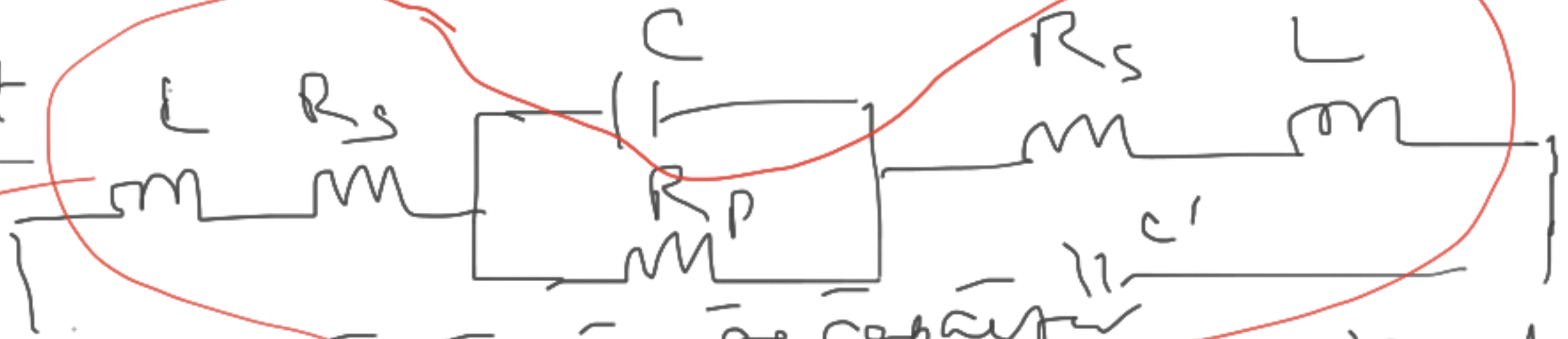

R_p = in parallel resistance of capacitor
 R_s = series resistance & L = inductance of lead

$|Z|$
(Ω)

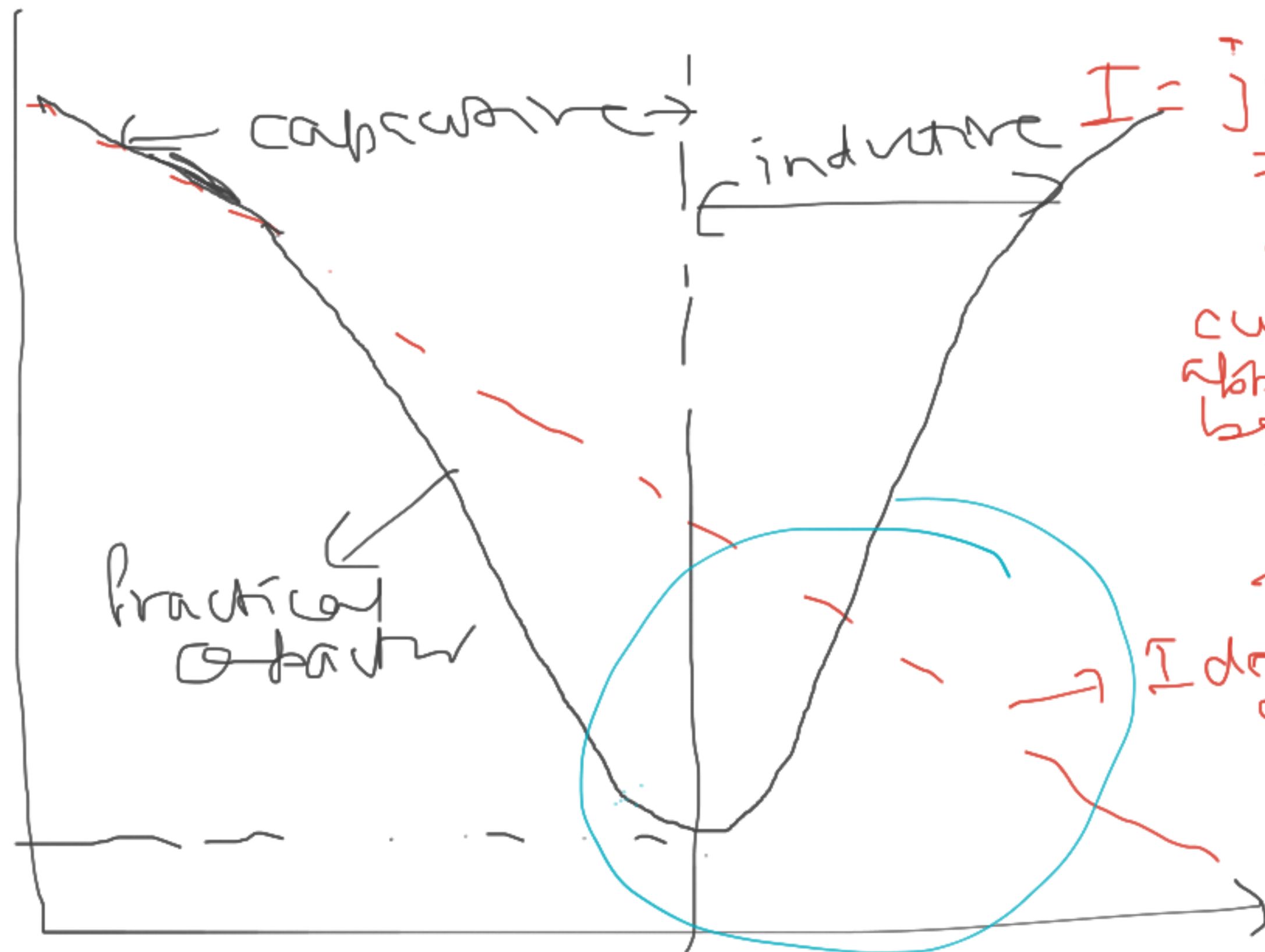

$$I = j\omega CV - j\omega L$$

$$= \omega CV e^{j90^\circ}$$

current leads
applied voltage
by exactly
 90°

Ideal (or perfect)
cap $= \frac{1}{j\omega C}$

$$= \frac{1}{j2\pi fC}$$

CIVIL


$R_s + R_p$
 $= R_{eq}$
 $= ESR$
resistor

$$X_L = X_C$$

$$j\omega L = \frac{1}{j\omega C}$$

$$\Rightarrow f = \frac{1}{2\pi\sqrt{LC}}$$

(i). Power factor (PF)

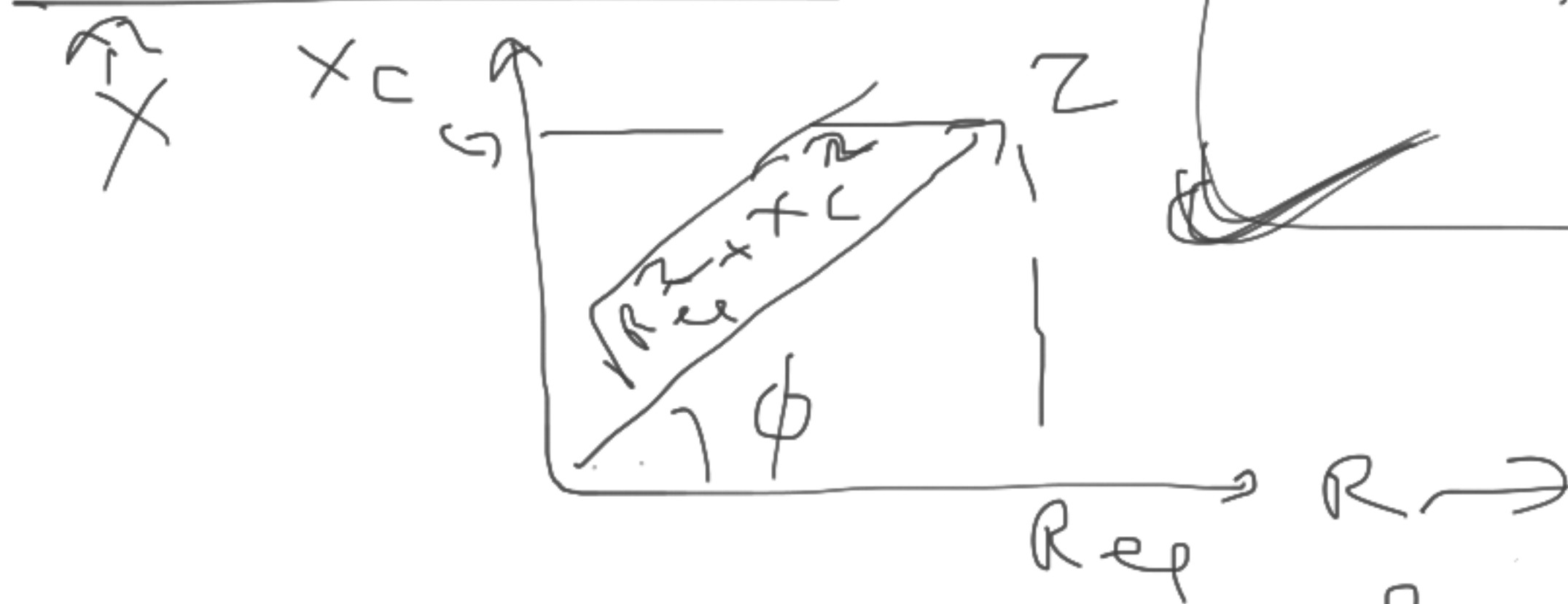

$$= \cos \phi = \frac{R_{eq}}{\sqrt{R_{eq}^2 + X_c^2}}$$

$$X_c = \frac{1}{j\omega C}$$

Usually, $R_{eq} \ll X_c$, ($\omega \gg \text{ESR}$)

approximate

$$PF \approx \cos \phi \approx \frac{R_{eq}}{X_c}$$

(ii)

R_{eq} or ESR
(Equivalent resistance, effective series resistance)

$$= R_s + R_p = \text{ac resistance of capacitor}$$

(iii) Dissipation Factor (DF) : ratio of ac work
to reactance of capacitor

$$DF = \frac{R_{eq}}{X_C} \times 100\%$$

(iv) Quality factor (Q) = $\frac{X_C}{R_{eq}} = \frac{1}{\omega C R_{eq}}$

$$\approx \frac{1}{PF} \approx \frac{1}{DF}$$

(v) Loss tangent ($\tan \delta$) ^{here} $\delta \neq$ skin depth


$$\tan \delta = \frac{-E''}{E'}$$

$$\left(\epsilon_r = \epsilon_{r, \text{real}} + \epsilon_{r, \text{imag}} \right) = \epsilon'_r + \epsilon''_r$$

$$\tan \delta = \frac{\sigma}{\omega \epsilon}$$

$$\frac{\sigma + \omega \epsilon''}{\omega \epsilon'} = \frac{1}{Q} \text{ or } \tan \delta$$

$\sigma = \text{conductivity}$

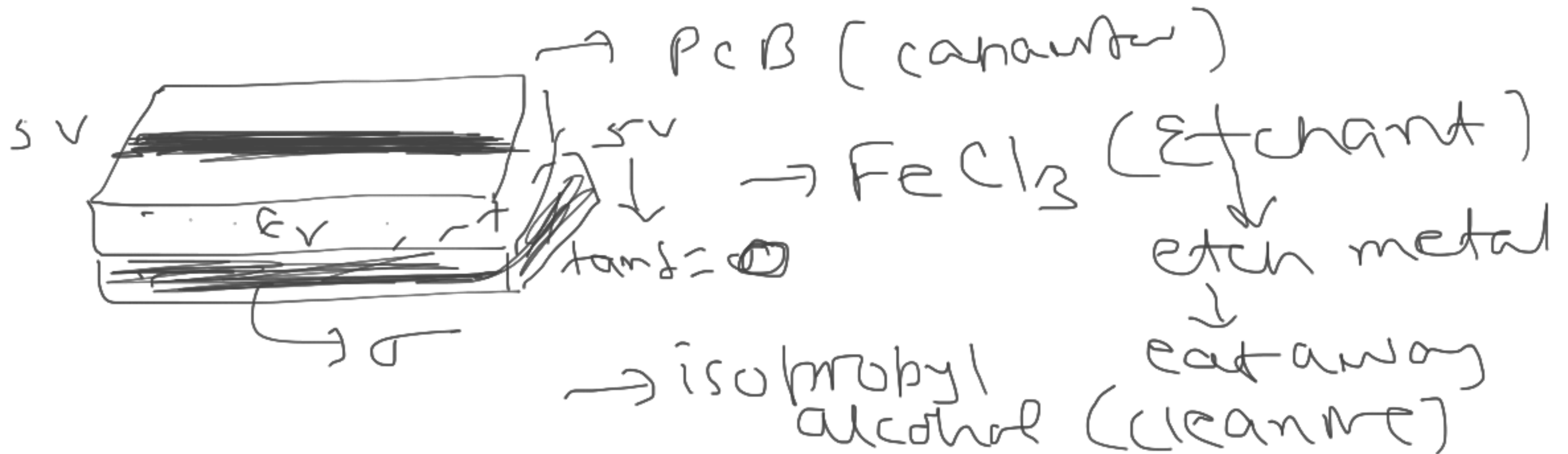

PCB = FR4 ($\epsilon_r = 4$)

Reinforced fabric



$\tan \delta = 0.0001$ at 10 kHz

$= 0.001$ at 100 kHz

$= 0.01$ at 1000 kHz (1 MHz)

$= 0.1$ at 1 GHz

very loss at 1 GHz

Shear PCBs \rightarrow Dielectric Substrate

$\tan \delta = 0.0001$ at 1 GHz

(very low loss at 1 GHz)

- RT Durovd
 - Arlon
 - Tacon
- Dielectric Substrates
 $\tan \delta \approx 0.0001$ at 1 GHz

For a perfect capacitor

$$R_{eq} \text{ (or ESR)} = 0$$

$$PF = 1$$

$$DF = 0\%$$


$$Q = \infty$$

$$\tan \delta \approx 0$$

Applications
 of Cap

- Resonator
- filter
- DC block

RF behavior of Inductor (L)

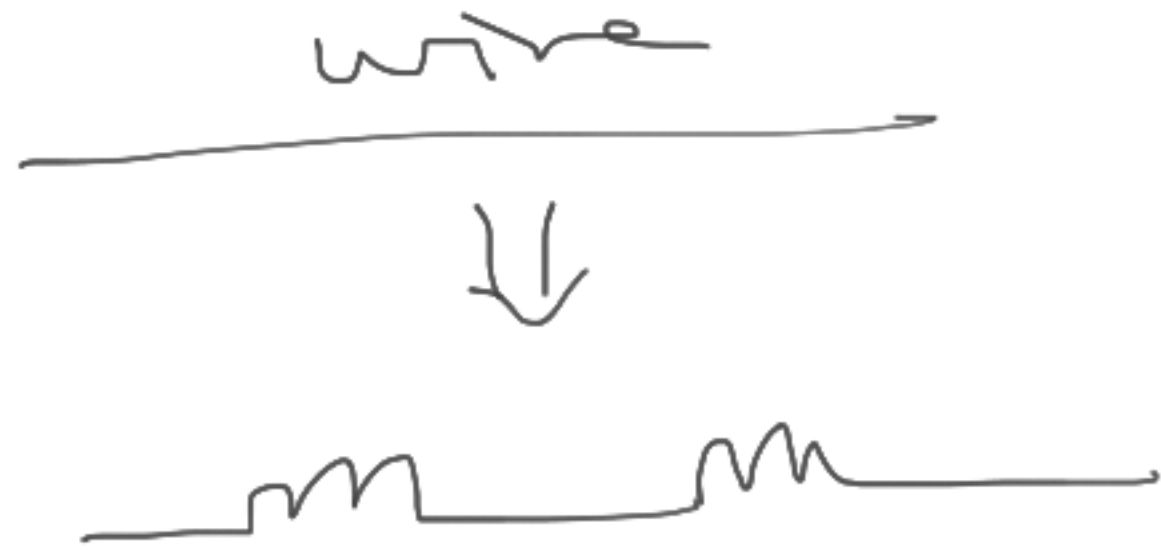


a wire that is
coiled (or wound)
in such a manner
so as to increase
magnetic flux linkage
between turns of
coil



DC:
eff
ckt
of
L

AC (or RF) eqn ckt of inductor

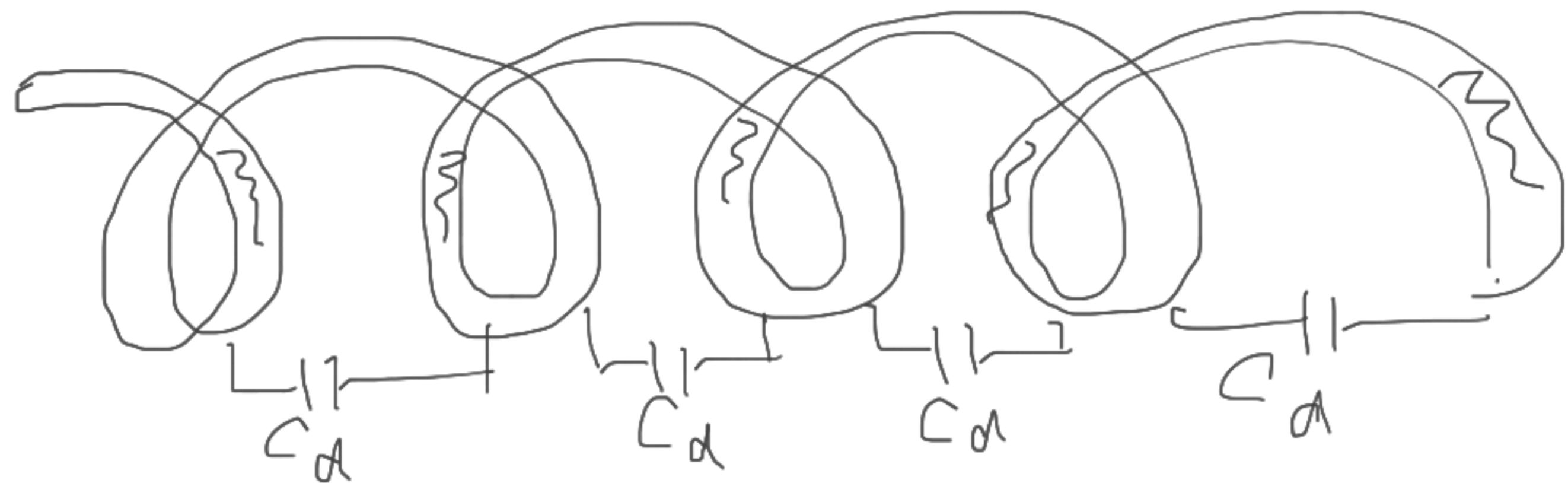


C_d = distributed cap

L = inductance of material of wire


R = resistance of material of wire

Parameter
or
Storage elements

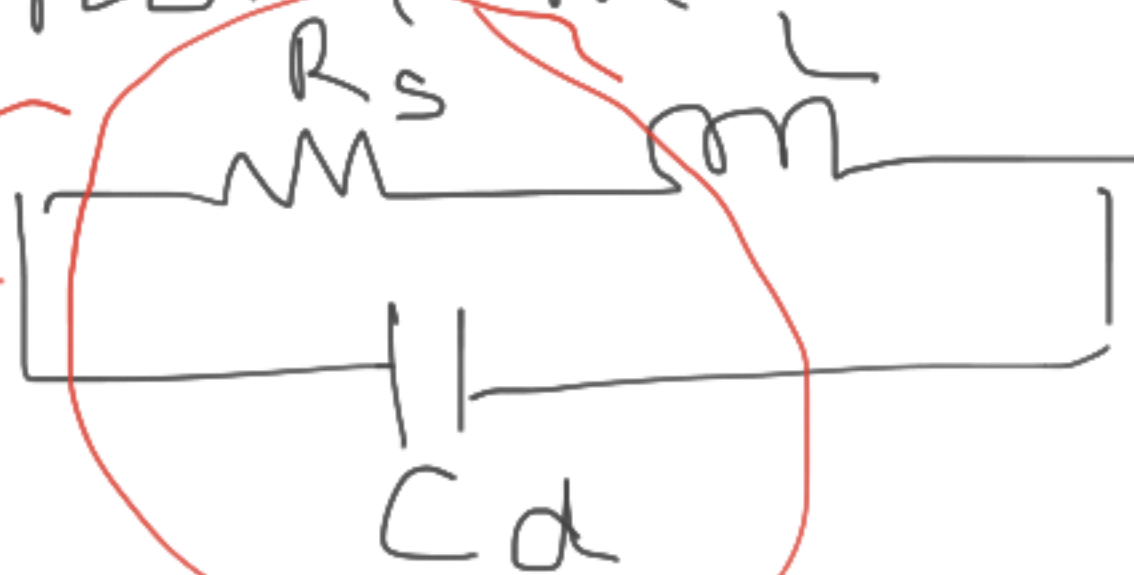

L, C
→ storage

$|Z|$
(Ω)

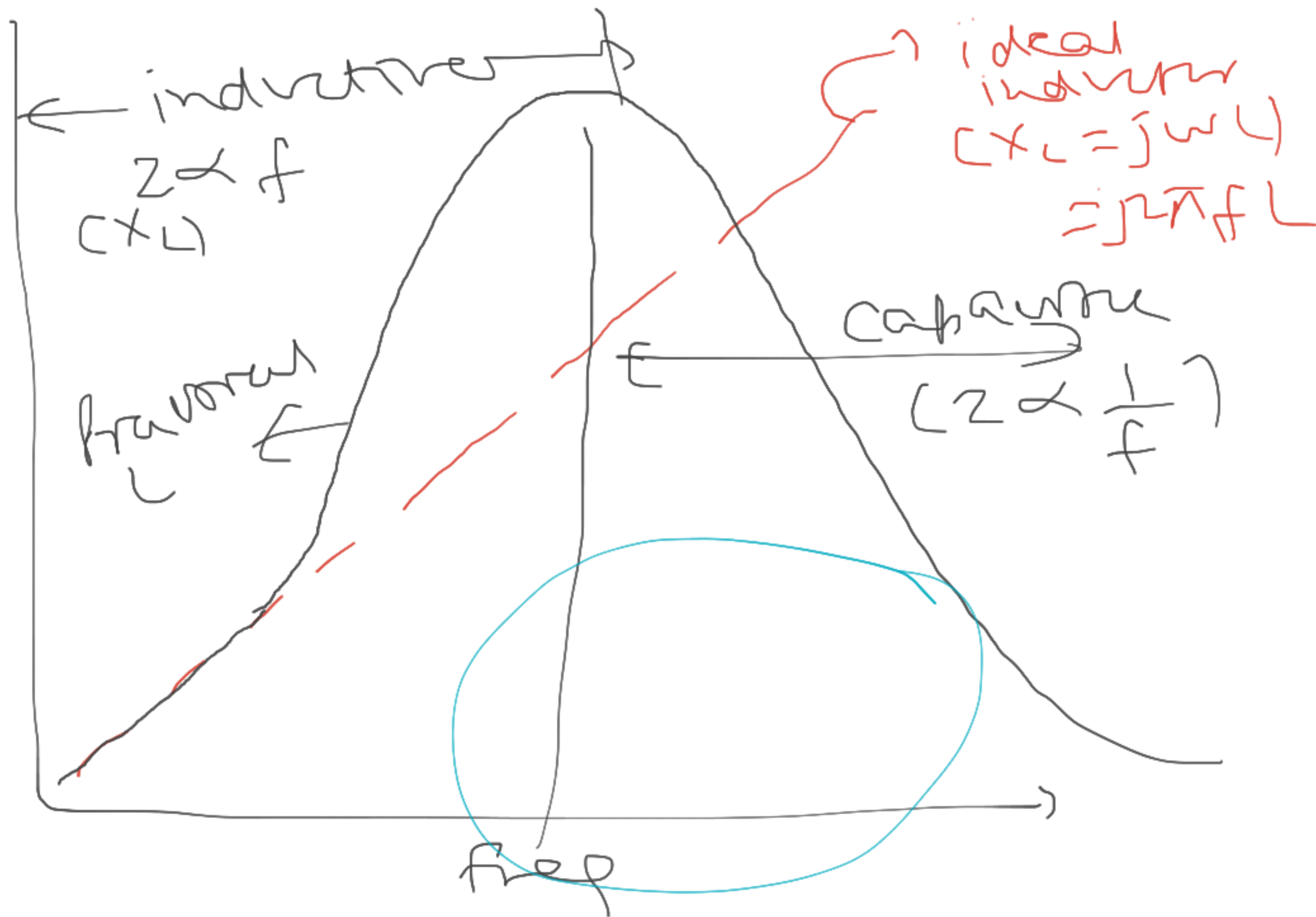

For a perfect inductor

$$R_s = 0$$

$$Q = \frac{X_L}{R_s} = \frac{\omega L}{R_s} = \frac{2\pi f L}{R_s} = \infty$$

To increase Q of inductor

- (i) use a larger diameter of wire
→ area is larger → $R = \frac{\rho l}{A}$ = smaller
- (ii) Spread the windings apart
→ d will increase ⇒ $C = \frac{\epsilon A}{d}$ = smaller
(distance) between windings
- (iii) increase L by increasing permeability of
magnetic core → ferrite rod

Applications of inductor


Resonant circuit

Filter

Phase shifter (ϕ)

Delay network (Δt)

RF choke (blocks the RF or ac)

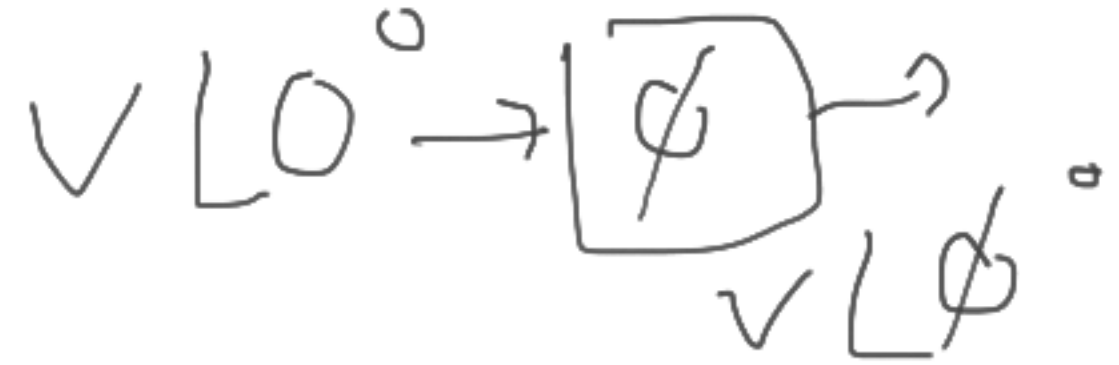

Bias Tee (Bias T)

