

D3.140 Common Base Amplifier


Given (i) $R_{in} = 50 \Omega$

(ii) $R_{sig} = 50 \Omega$

(iii) Calculate I & R_C , G_{v0} , G_v

(iv) If $v_{be} = \max. \pm 10 \text{ mV}$ then there should be no distortion. This should decide Q point.

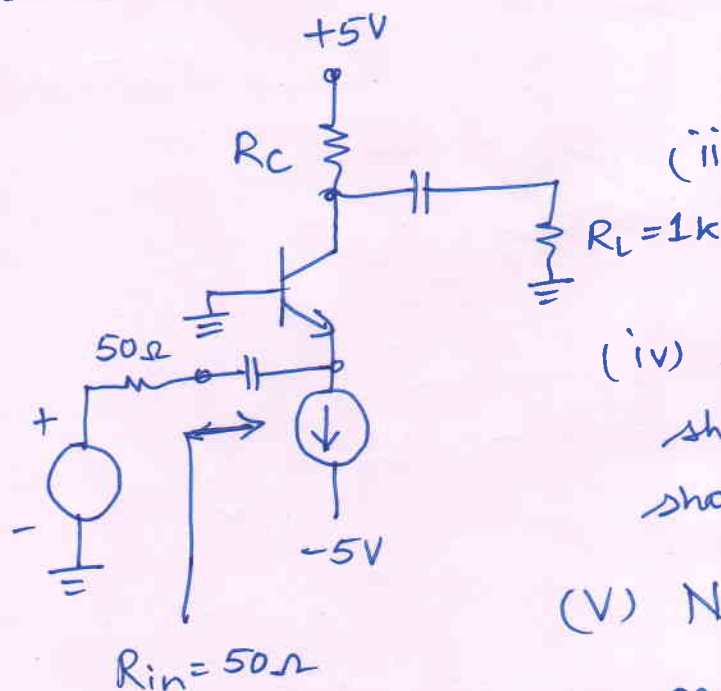(v) Note β is not specified & will not be needed.



Given $R_{in} = R_{sig} = 50 \Omega = r_e$. Calculate I

based on r_e and g_m as follows:

$$r_e = \frac{\alpha}{g_m} = \frac{1}{g_m} \therefore g_m = \frac{1}{r_e} = \frac{1}{50}$$

$$\therefore g_m = I/V_T \therefore I = g_m \cdot V_T = \frac{1}{50} \times 25 \text{ mV}$$

$$\boxed{I = 0.5 \text{ mA}}$$

What should be V_C at Q point? It should be mid point between two extremes - cutoff or

$$V_C = 5 \text{ V and saturation when } V_C = V_B - 0.5 \text{ V}$$

$$= 0 - 0.5 \text{ V.}$$

So Q point should be between 5V & -0.5V.

The room for swing is $5 \text{ V} - (-0.5 \text{ V}) = 5.5 \text{ V}$

The Q point should be set $5.5V/2 = 2.75V$
From both extremes

$$\therefore I_C R_C = 2.75V$$

$$\therefore I_C = 0.5 \text{ mA}$$

$$R_C = 2.75V / 0.5 \text{ mA} = \boxed{5.5 \text{ K}}$$

$$G_{vo} = \frac{\alpha R_C}{R_{sig} + r_e} \quad \cdot \quad G_v = \frac{\alpha (R_C \parallel R_L)}{R_{sig} + r_e}$$


$$= \frac{(5.5 \text{ K} \parallel 1 \text{ K})}{50 \Omega + 50 \Omega} = \frac{(5.5 \text{ K} \times 1 \text{ K}) / (6.5 \text{ K})}{100 \Omega}$$

$$G_{vo} = \boxed{55 \text{ V/V}} \quad G_v = \boxed{8.4 \text{ V/V}}$$

3.141

Find R_{in} , G_v
Given $\beta = 100$.

13

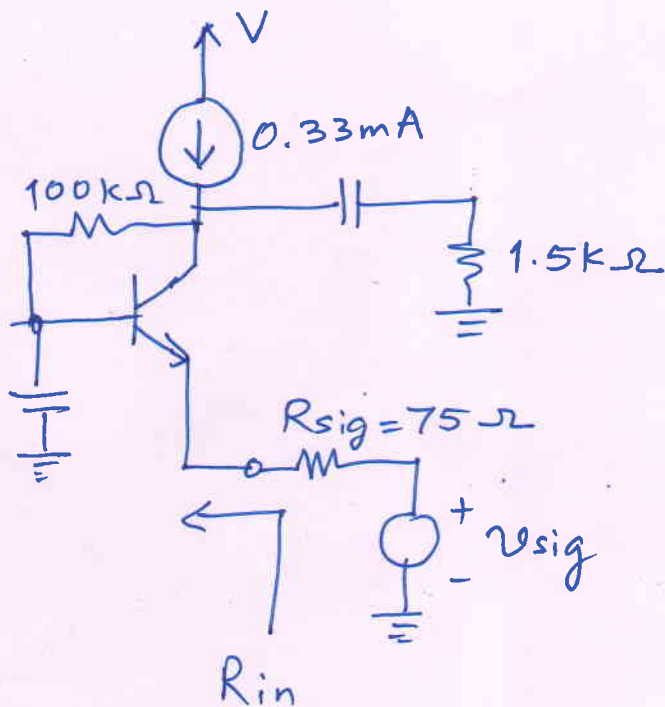

$$I_C = 0.33 \text{ mA} = \frac{1}{3} \text{ mA}$$

$$g_m = \frac{0.33 \text{ mA}}{25 \text{ mV}} = \frac{1}{3 \times 25} = \frac{1}{75} \text{ S}$$

$$r_e = \frac{1}{g_m} = 75 \Omega$$

$$G_v = \frac{v_o}{v_{sig}} = \frac{\alpha (R_C \parallel R_L)}{R_{sig} + r_e} = \frac{1.5 \text{ k}\Omega}{75 + 75} = \boxed{10}$$

Let us Calculate DC Voltage:

DC resistance of $v_{sig} = 0$.

$$V_E = I_E \cdot R_{sig} \approx \frac{1}{3} \text{ mA} \times 75 \Omega = \boxed{25 \text{ mV}}$$

$$V_B = V_E + 0.7 \text{ V} = 25 \text{ mV} + 700 \text{ mV} = \boxed{725 \text{ mV}}$$

$$I_B = I_C / 100 = \frac{1}{3 \text{ mA}} \cdot \frac{1}{100} = \frac{1 \text{ mA}}{300} = 3.33 \mu\text{A}$$

$$V_C = V_B + I_B \times 100 \text{ k}\Omega = 725 \text{ mV} + 3.3 \mu\text{A} \times 100 \text{ k}\Omega = \boxed{1058 \text{ mV}}$$

3.142 Emitter Follower Circuit

$$I = 1 \text{ mA}$$

$$\beta = 100$$



$$V_A = 100 \text{ V}$$

$$R_B = 100 \text{ k}$$


$$R_{\text{sig}} = 20 \text{ k}$$

$$R_L = 1 \text{ k}$$


Find R_{in} , v_o/v_{sig} and R_{out} .

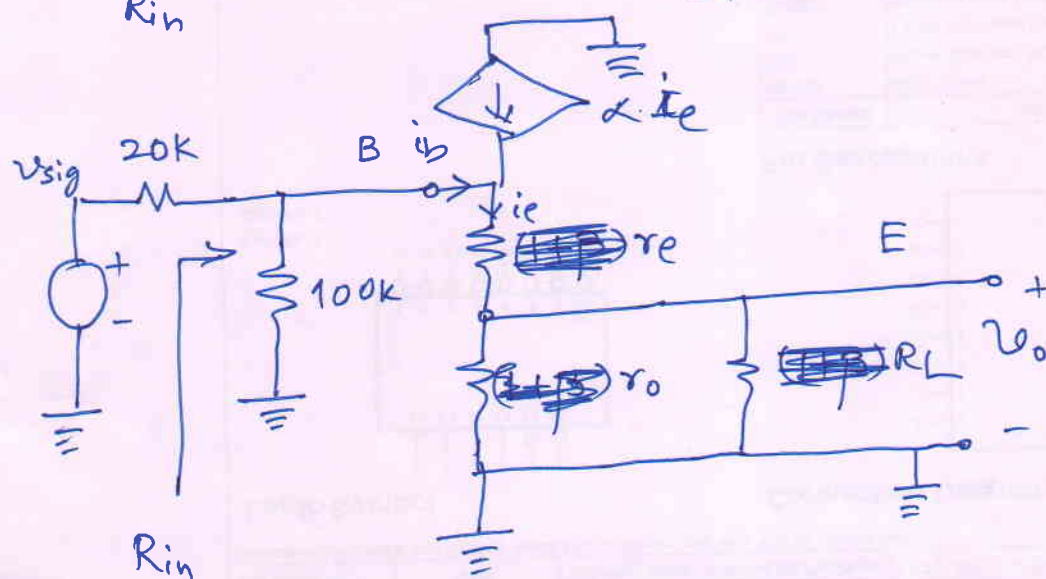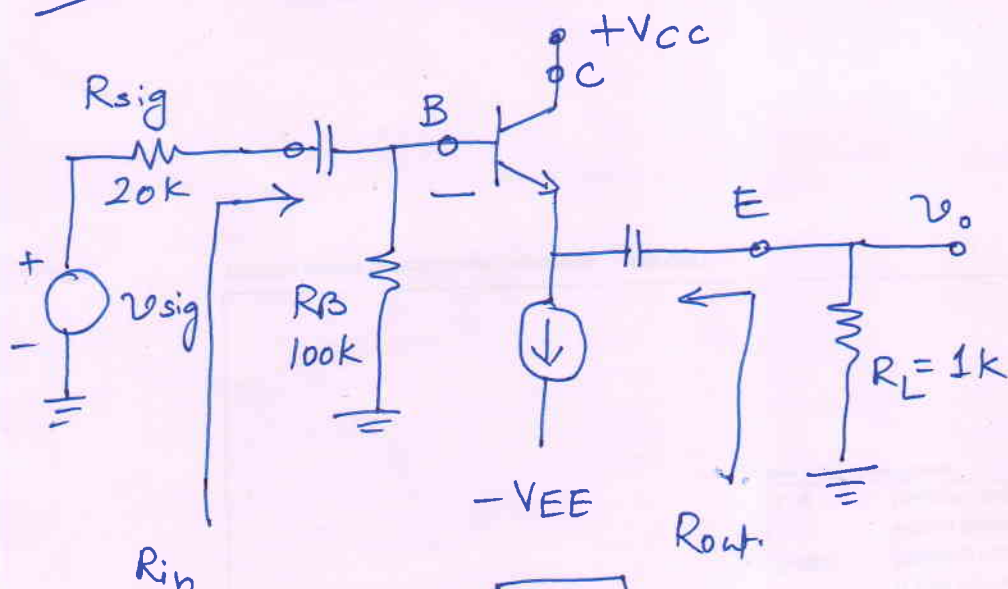

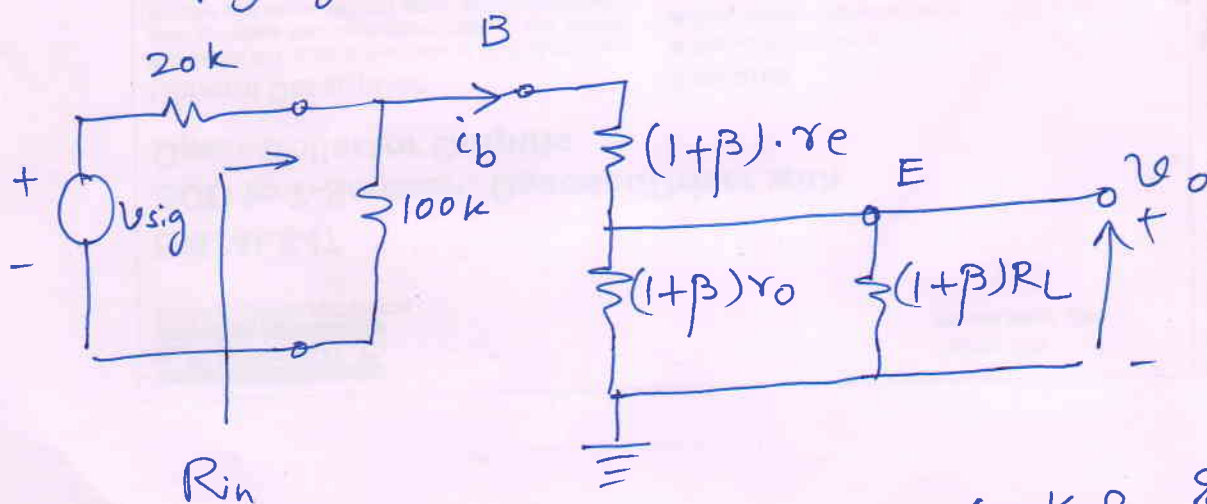
Note that $r_e, (r_o \parallel R_L)$ has current i_e . Now we reflect resistors in emitter circuit in base by multiplying them with $(1+\beta)$



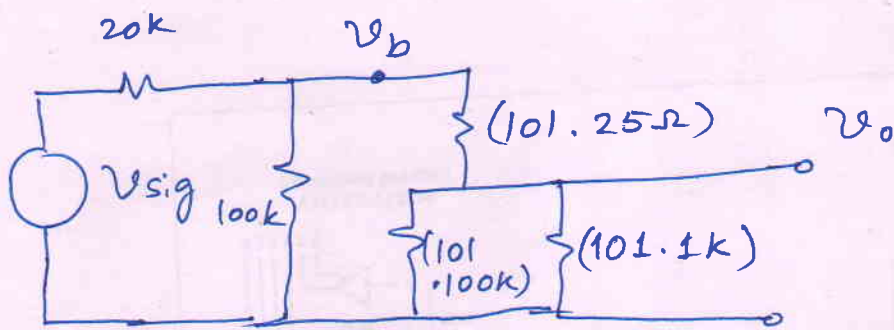Calculate $g_m = 40 \text{ mV}$ $r_o = 100 \text{ k}\Omega$, $r_e = 25\Omega$



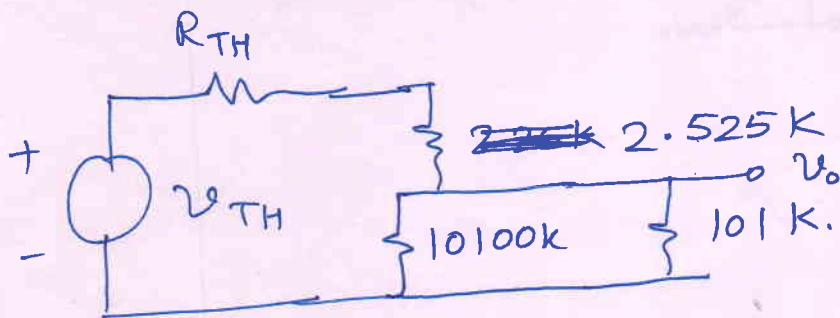Replace 20k & 100k by thevenin equivalent



$$R_{TH} = \frac{20k \times 100k}{20k + 100k} = \frac{2000k \cdot k}{120k} = 16.66k$$

$$V_{TH} = \frac{100k}{100k + 20} \cdot v_{sig} = 0.833 v_{sig}$$

$$v_o = \frac{100k}{100k + 2.525k + 16.66k} \cdot v_{TH}$$

$$= \frac{100k}{119.19k} \times 0.833 \times v_{sig}$$

$$\boxed{\therefore \frac{v_o}{v_{sig}} = 0.698} = G_v$$

$$\frac{v_o}{v_b} = \frac{100k}{100k + 2.525k} = \boxed{0.975}$$

$$\frac{V_b}{V_{sig}} = \frac{100 + 2.525K}{100K + 2.525K + 16.66K}$$


$$= 0.8601$$

$$R_{in} = 100K \parallel (2.525K + 100K)$$

$$= 100K \parallel 102.525K$$

$$= 50.61K$$

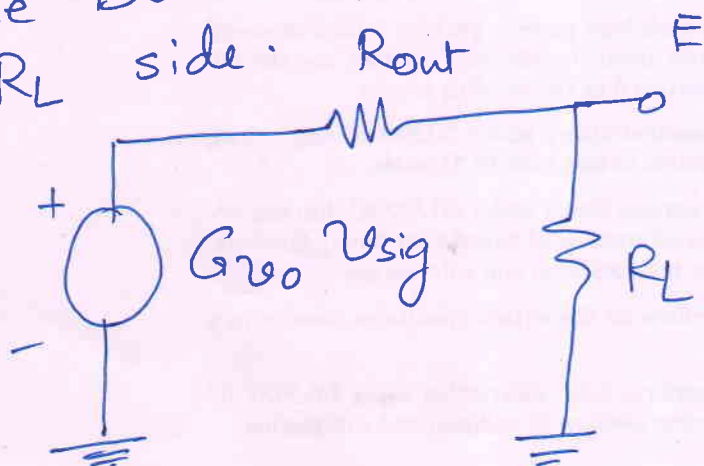If V_{sig} is a sine wave what should be the max. value at which BJT will remain conducting? At this V_{sig} what is V_b ?
The BJT appears as a Thevenin Model from R_L side.



When V_{sig} goes negative the signal current in R_L will flow from GND into Emitter. When this becomes equal to DC biasing current I , BJT goes into Cutoff.


The most negative signal output voltage \hat{V}^o (17)
can be given as

ac signal peak value $\rightarrow \frac{\hat{V}^o}{R_L} = I$ (dc bias current)

or $\hat{V}^o = I \cdot R_L$

or $G_v \cdot \hat{V}_{sig} = I \cdot R_L$

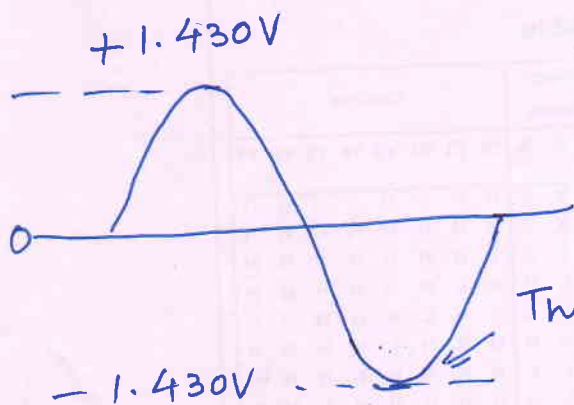\therefore max. permissible signal voltage (negative swing)
 $= \frac{I \cdot R_L}{G_v} = \frac{1 \text{ mA} \times 1 \text{ K}}{0.698} = \boxed{1.430 \text{ V}}$



This will cause BJT to go in cutoff.

V_b at this $V_{sig} = 0.8601 \times 1.430 = \boxed{1.230 \text{ V}}$

$R_{out} = r_o \parallel \left(r_e + \frac{R_{sig} \parallel R_B}{\beta + 1} \right)$ Note Low Output Resist.

$= 100 \text{ K} \parallel \left(25 \Omega + \frac{16.66 \text{ K}}{101} \right) = 100 \text{ K} \parallel \boxed{191.3 \Omega}$