
 


LOW FREQUENCY RESPONSE OF A CE AMPLIFIER


We will now draw small signal model at low frequencies where C_{C1} , C_{C2} and C_E will not be perfect short circuits (as we assumed before in Mid Band & High Frequency Band) but will show significant reactance (or impedance). Similarly at such low frequencies the effect of C_{π} and C_{μ} will be negligible & we will not consider them. We will neglect r_o also assumed to be too high compared to R_C and R_L . Lastly we will neglect r_x which is in series with much larger quantity z_{π} .

Original Circuit with biasing

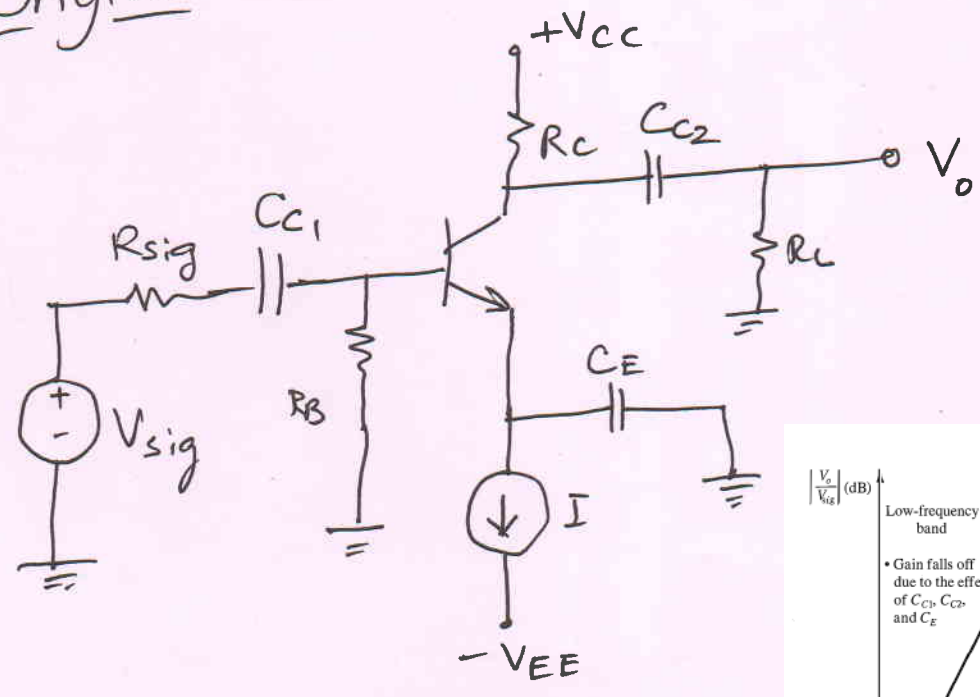

We will solve this circuit to find out effect of C_{c1} , C_{c2} and C_E by considering effect of each of one of them separately assuming that when one is considered, other two are perfect short circuit. So while evaluating effect of C_{c1} , we will assume C_{c2} and C_E to be SC.

Case I: Consider only C_{c1} .

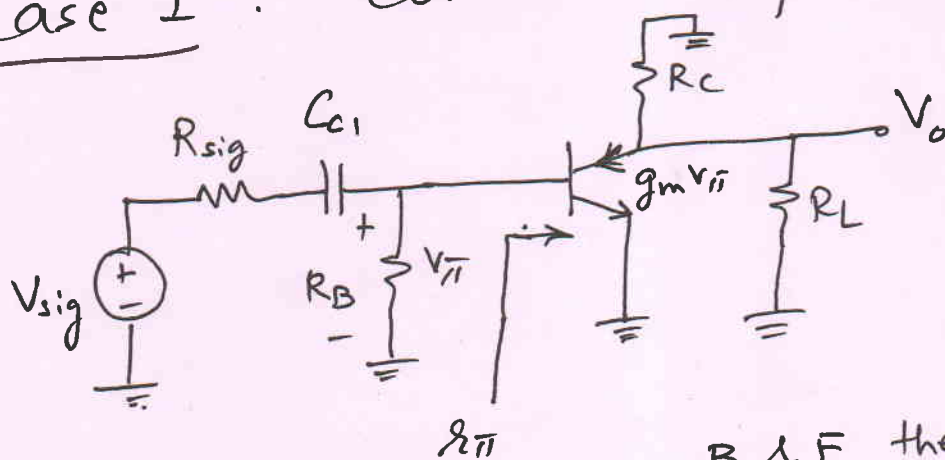

We can see that between B & E there are R_B & r_{π} in \parallel .
 V_{sig} sees three elements in series — R_{sig} , C_{c1} & $(R_B \parallel r_{\pi})$.

$$\therefore V_{\pi} = \frac{R_B \parallel r_{\pi}}{(R_B \parallel r_{\pi}) + R_{sig} + \frac{1}{sC_{c1}}} \cdot V_{sig}$$

Output Voltage

$$V_o = -g_m \cdot V_{\pi} (R_C \parallel R_L)$$


\therefore Overall Voltage Gain

$$\frac{V_o}{V_{sig}} = -g_m (R_C \parallel R_L) \left\{ \frac{(R_B \parallel r_{\pi})}{(R_B \parallel r_{\pi}) + R_{sig}} \right\} \left[\frac{s}{s + \frac{1}{C_{c1} [(R_B \parallel r_{\pi}) + R_{sig}]}} \right]$$

The right side part is frequency sensitive (3) and represents a STC zero or High Pass type circuit with a corner frequency ω_{P1}

$$\omega_{P1} = \frac{1}{C_{C1} [(R_B \parallel r_{\pi}) + R_{sig}]}$$

 
The part in [] brackets is R_{eq} as seen across the terminals of C_{C1} when V_{sig} is set to 0.




R_{eq} is between A & B
 $= R_{sig} + R_B \parallel r_{\pi}$

We have obtained R_{eq} & ω_{P1} connected with C_{C1}

 Case II : Consider only C_E
 C_{C1} & C_{C2} are perfect short circuits.



 We reflect r_e and C_E into base circuit.



$$R_{TH} = \frac{R_B \cdot R_{sig}}{R_B + R_{sig}}$$

$$\Rightarrow V_{TH} = \frac{R_B}{R_B + R_{sig}} \cdot V_{sig}$$

Hence I_b will be

$$I_b = \frac{V_{TH}}{R_{TH} + (1+\beta)r_e + (1+\beta)\frac{1}{sC_E}}$$

$$= \frac{R_B}{R_B + R_{sig}} \left\{ \frac{1}{(R_B \parallel R_{sig}) + (1+\beta)\left(r_e + \frac{1}{sC_E}\right)} \right\} \cdot V_{sig}$$

The output current source = βI_b

and output Voltage $V_o = -\beta \cdot I_b \cdot (R_C \parallel R_L)$

$$\therefore \text{Overall Voltage Gain} = \frac{V_o}{V_{sig}}$$

$$= -\left(\frac{R_B}{R_B + R_{sig}}\right) \left\{ \frac{\beta(R_C \parallel R_L)}{(R_B \parallel R_{sig}) + (1+\beta)r_e} \right\} \frac{s}{s + \frac{1}{C_E\left(r_e + \frac{R_B \parallel R_{sig}}{\beta+1}\right)}}$$

The extreme right side factor gives STC high pass filter with 3 db corner frequency ω_{P_2} as

$$\omega_{P_2} = \frac{1}{C_E \left[r_e + \frac{R_B \parallel R_{sig}}{(1+\beta)} \right]}$$

Note that the resistor component or R_{eq} can be given as

$$R_{eq} = r_e + \frac{R_B \parallel R_{sig}}{1+\beta}$$

= resistor^{ance} seen by C_E looking into Emitter when V_{sig} is grounded. The base resistance to ground $R_B \parallel R_{sig}$ is reflected $1/(\beta+1)$ when transferred from base to emitter and put in series with r_e .

$$f_{P_2} = \frac{1}{2\pi C_E \left[r_e + \frac{R_B \parallel R_{sig}}{1+\beta} \right]}$$

Note - that r_e is small and $(R_B \parallel R_{sig})$ get divided by $(1+\beta)$ which is large so they also contribute small. Thus f_{P_2} will be higher than f_{P_1} (and possibly than f_{P_3} also).

Case III


Consider Only C_{c2} .

(6)

Since C_{c1} and C_{cE} are perfect short circuit,
we can write V_{π} as in mid band —

$$V_{\pi} = V_{sig} \frac{R_B \parallel r_{\pi}}{(R_B \parallel r_{\pi}) + R_{sig}}$$

and Now see the output in model :

 

$$V_o = I_2 \cdot R_L \quad \text{--- (1)} \quad g_m V_{\pi} = I_1 + I_2 \quad \text{--- (2)}$$

$$\frac{I_2}{I_1} = \frac{Y_2}{Y_{RC}} = \frac{Z_{RC}}{Z_1} = \frac{R_C}{R_L + \frac{1}{C_{c2} \cdot s}}$$

$$\therefore I_2 = I_1 \cdot \frac{R_C}{R_L + \frac{1}{C_{c2} \cdot s}} \quad \text{--- (3)}$$

Therefore,

$$\frac{V_o}{V_{sig}} = \left\{ \frac{-(R_B \parallel r_{\pi})}{(R_B \parallel r_{\pi}) + R_{sig}} \right\} g_m (R_C \parallel R_L) \left[\frac{s}{s + \frac{1}{C_{c2} (R_C + R_L)}} \right]$$

The part in rectangular bracket is frequency sensitive STC part and gives us corner frequency ω_{P_3} as (7)

$$\omega_{P_3} = \frac{1}{C_{C2}(R_C + R_L)}$$


where $(R_C + R_L)$ is resistance as seen by C_{C2} when $V_{sig} = 0$ and current source is opened.

— x —
We have estimated effect of each capacitor when contributing alone. Now if we assume that all 3 affect simultaneously but without interacting with each other. In other words, if they are widely separated in their f values then we can write transfer fn. as

$$\frac{V_o}{V_{sig}} = -A_{M1} \left(\frac{s}{(s + \omega_{P1})} \right) \left(\frac{s}{s + \omega_{P2}} \right) \left(\frac{s}{s + \omega_{P3}} \right)$$

Each one will contribute a 20 db/decade slope as shown.

(8)

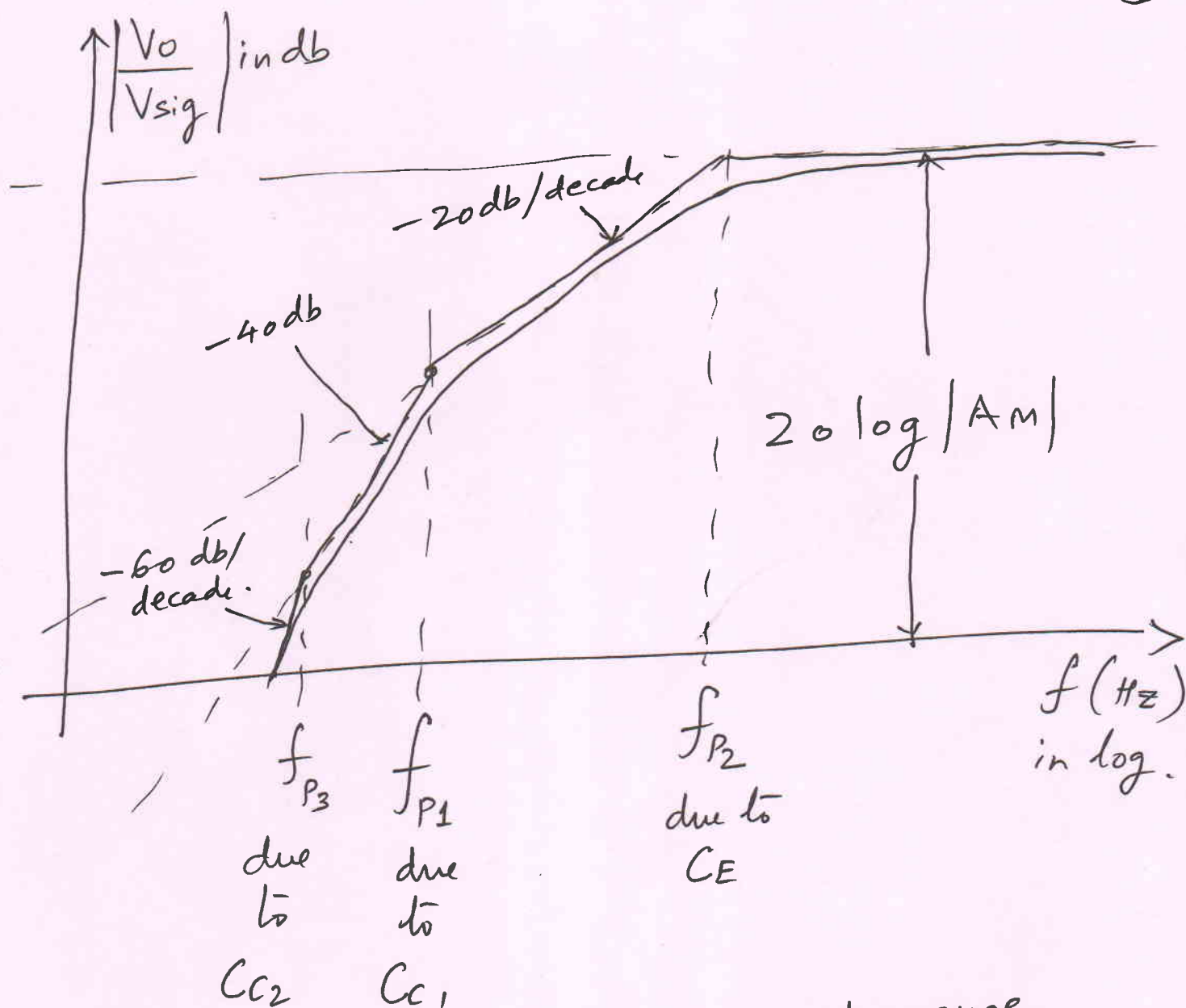

Usually f_{P2} is dominant one because f_L is largest of f_{P1} , f_{P2} and f_{P3} and that is usually f_{P2} .

If the 3 frequencies are close to each other and they interact then calculations become complex. As a first approx. we can assume

$$f_L = f_{P1} + f_{P2} + f_{P3}$$

Each corner frequency pushes lower cutoff freq f_L up and above & reduces Bandwidth.

How to select values of C_{C1} , C_{C2} & C_E ? (9)

The design objective is to place lower cutoff frequency f_L of the amplifier at a desired value or location. Since C_E sees a very small resistance, it is usually the dominant freq. and we should use C_E to affect f_{P2} which is close to f_L . Then select f_{P1} and f_{P3} far lower than f_{P2} . This method gives minimum sum total of 3 capacitors & saves cost & space.

For example in equation $f_L = f_{P1} + f_{P2} + f_{P3}$ if we set $f_{P2} = 0.8 f_L$ and rest both as $0.1 f_L$ then we will select C_E such that

$$f_{P2} = 0.8 f_L = \frac{1}{2\pi(R_E) C_E}$$

Calculate resistors seen by each capacitor by C_{C1} , let us call it R_{C1}

$$R_{C1} = (R_B \parallel R_{\pi}) + R_{sig}$$

$$0.1 f_L = \frac{1}{2\pi R_{C1} \cdot C_{C1}}$$

by C_E , let us call it R_E

$$R_E = r_e + \frac{R_B \parallel R_{sig}}{(1+\beta)}$$

$$0.8 f_L = \frac{1}{2\pi R_E \cdot C_E}$$

by C_{C2} , let us call it R_{C2}

(10)

$$R_{C2} = R_C + R_L \quad f_{p3} = 0.1 f_L = \frac{1}{2\pi R_{C2} \cdot C_{C2}}$$

Get exact value of C_{C1} , C_{C2} & C_E From above
and then put standard commercially
available capacitor values, just next higher
e.g. if you get $C_{C1} = 1.8 \mu F$, $C_E = 27 \mu F$
and $C_{C2} = 2.7 \mu F$ then use $C_{C1} = 2.2 \mu F$ or $3.3 \mu F$
 $C_E = ~~47~~ 33 \mu F$ or $47 \mu F$ and $C_{C2} = 3.3 \mu F$ or
 $4.7 \mu F$.

Putting slightly higher value of
Commercial value available will ensure that
your design lower cutoff frequency will be
slightly lower than what you wish to achieve
and give you slightly better or more
bandwidth.

Solve problems Example 3.19, Exercise 3.52
Solve unsolved problems 3.159, 3.160, 3.161 also
at home.