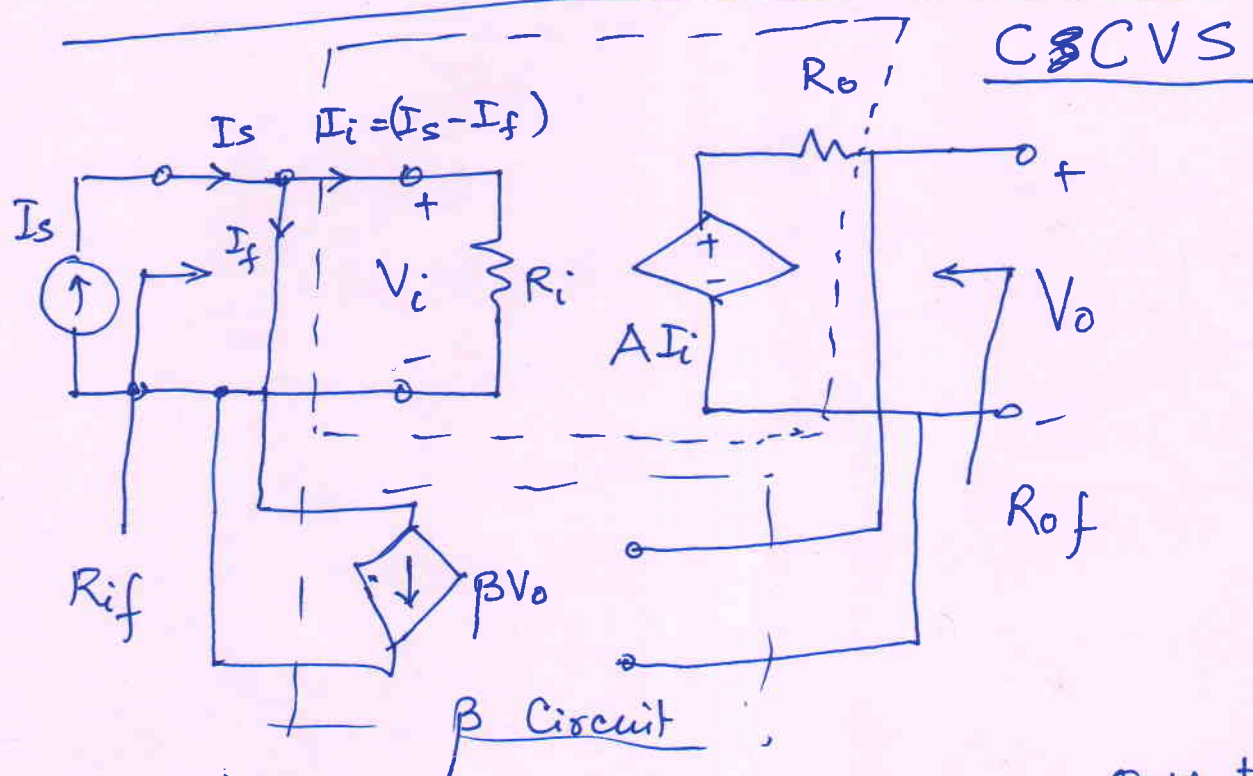


# SHUNT-SHUNT FEEDBACK

(1)

VOLTAGE FEEDBACK INSERTED IN  
SHUNT WITH INPUT VOLTAGE SIGNAL



Amplifier has input resistance  $R_i$ , Output is a current controlled voltage source  $A \cdot I_i$  where  $A$  has units of Trans-resistance.  $R_o$  is the output resistance.  $R_{if}$  and  $R_{of}$  are values when feedback is applied.  $\beta$  circuit senses output voltage  $V_o$  and produces feedback current  $I_f$  such that

$$I_f = \beta V_o \quad \text{where } \beta \text{ has units of transconductance}$$

Closed Loop Gain with feedback is defined as

$$A_f \equiv V_o / I_s$$

(1)

and is given by

(2)

$$A_f = \frac{A}{1 + A\beta}$$


$\therefore$  feedback is "inserted" in shunt with voltage/current ~~sh~~ source at input terminals, feedback will cause input resistance to decrease by a factor of  $D$ .

$$\therefore R_{if} = \frac{R_i}{D} = \frac{R_i}{1 + A\beta}$$


Similarly output resistance with Feedback will also decrease due to parallel connection (Voltage Sensing) of  $\beta$  to output.

$$\therefore R_{of} = \frac{R_o}{D} = \frac{R_o}{1 + A\beta}$$

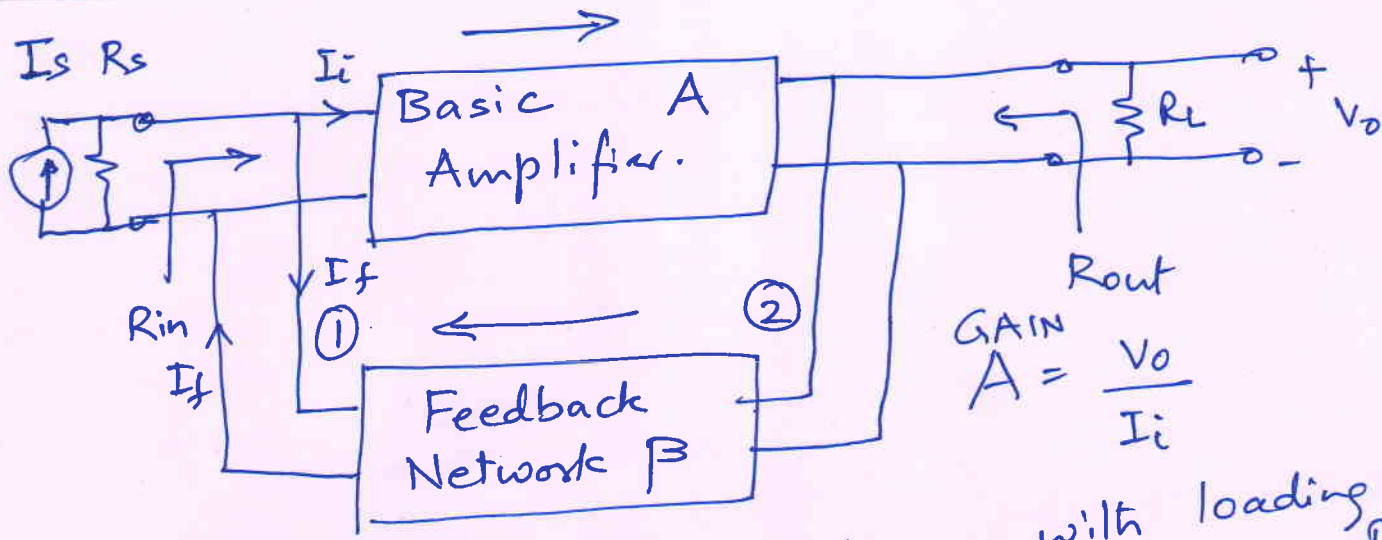
Now we will consider a practical shunt-shunt amplifier with feedback.



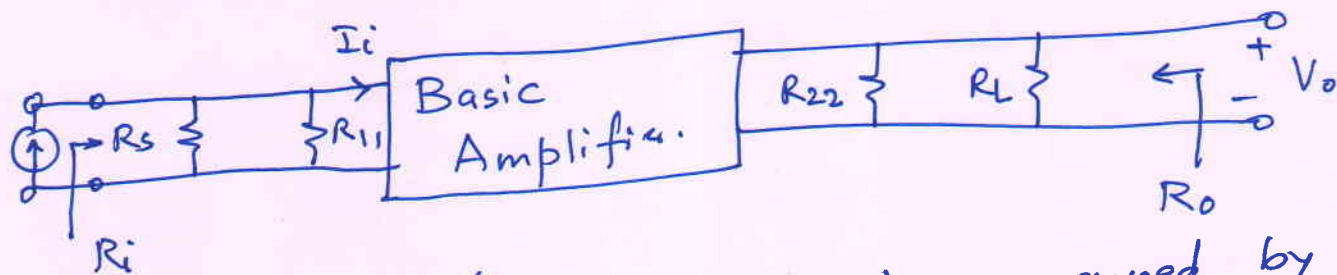
The above circuit is redrawn with loading of  $\beta$



$R_{11}$  is measured by

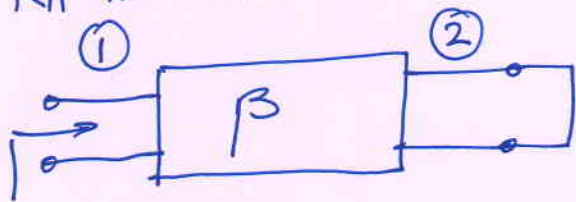

$R_{11}$   $\beta$  is measured from

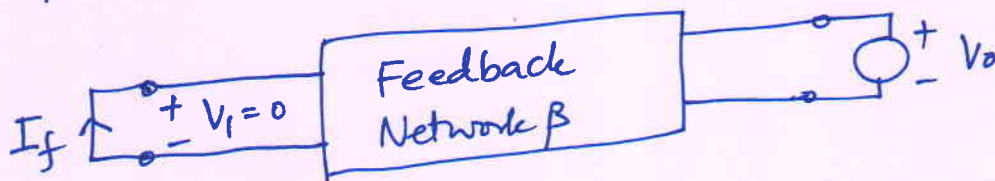


$R_{22}$  is measured by



$$\beta = \frac{I_f}{V_o} \bigg|_{V_1=0}$$

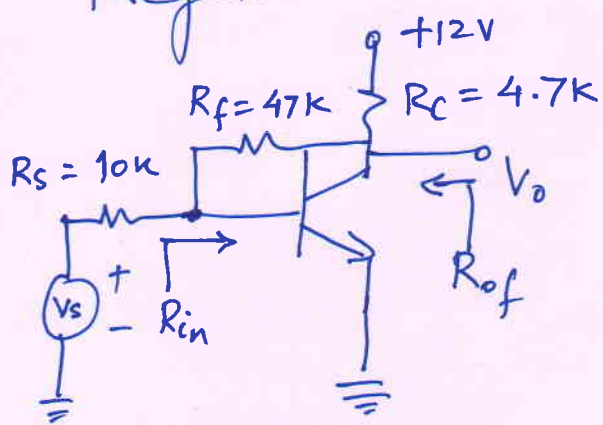Analyze following Self Bias Circuit as a Negative Feedback Amplifier. (4)



Assume current gain  $\beta = 100$ .

Find small signal Voltage Gain  $A_{vf}$   
 $R_{in}$  and  $R_{of}$ .

Calculate  $I_C$  &  $V_C$ .

$$V_E = 0 ; V_{BE} = 0.7 \therefore V_B = 0.7V$$

DC Current flowing into signal generator  
 $= \frac{0.7V}{R_S = 10K}$  (neglecting alternating signal source)

$$= (-7/10) mA = 0.07 mA$$

Now write KVL from +12V to GND through  $V_C$ ,  $R_C$ ,  $R_f$  and  $V_{BE}$ .

$$V_C = \text{drop across } V_f + V_{BE}$$

$$= (I_B + 0.07mA) \times 47k + 0.7 \quad \text{--- (1)}$$

$$+12V = I_C R_C + V_C$$

$$\text{or } V_C = 12V - I_C R_C$$


$$= 12V - \beta \cdot I_B R_C \quad \text{--- (2)}$$



This gives us  $I_B = 15\mu A$ ,  $I_C = 1.5mA$ ;  $V_C = 4.7V$


$$g_m = \frac{I_C}{V_T} = 60mS \quad r_{\pi} = 1.666K$$




Now we will draw small signal model (5)

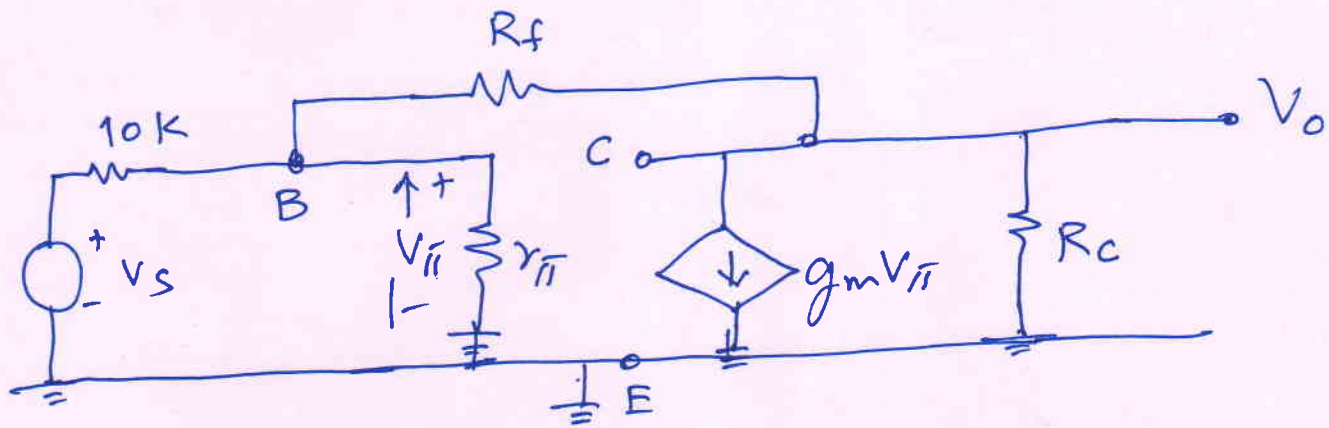

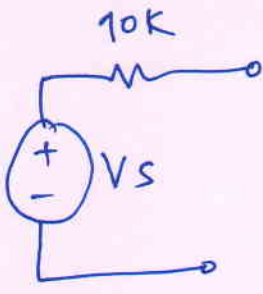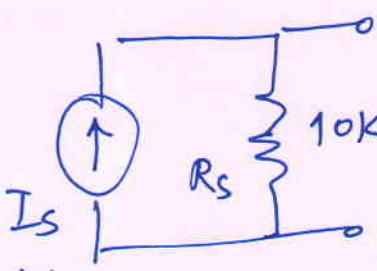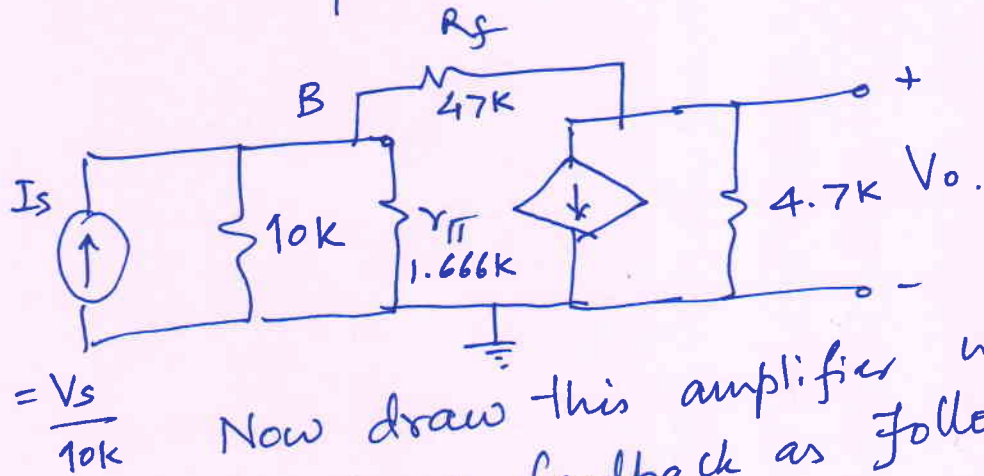Replace  
 By  
  
 $I_s = \frac{V_s}{R_s}$   
 $= \frac{V_s}{10k}$   
 Thevenin Source Representation      Norton Source Representation



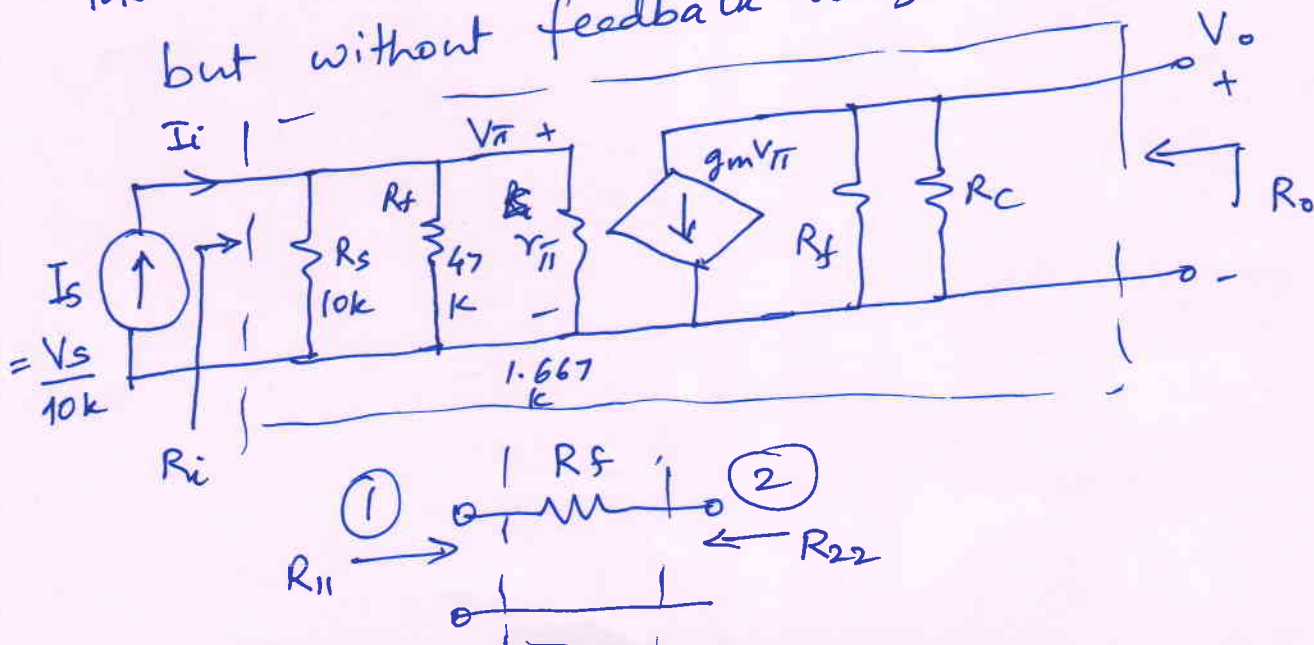Now draw this amplifier with loading of  $R_f$  but without feedback as follows:



Note - That to measure  $R_{11}$ , we short  $V_o$  and then other terminal (Collector) of  $R_f$  goes to 0  $\therefore R_{11}$  seen from port 1 is  $R_f$  to GND  $\therefore R_{11} = R_f$ . (6)

Similarly when we measure  $R_{22}$ , we short port 1 i.e. Base side terminal of  $R_f$  to ground & from Port 2 i.e. Collector side,  ~~$R_{11}$~~   $R_f$  appears as resistance to ground  $\therefore R_{22} = R_f$ .

So the loading of  $\beta$  network on A is just appearance of  $R_f$  in input & output, both places. Let us calculate Voltage Gain with Feedback.

$$V_{\pi} = I_i \cdot R_{\text{total in input circuit}}$$

$$= I_i \cdot (R_s \parallel R_f \parallel r_{\pi})$$

← loading of  $R_f$  input side.

$$\text{Similarly } V_o = -g_m V_{\pi} (R_f \parallel R_c)$$

← loading of  $R_f$  output side.


$\therefore$  Transresistance

$$A = \frac{V_o}{I_i} = -g_m (R_f \parallel R_c) (R_s \parallel R_f \parallel r_{\pi})$$

$$= -60 \text{ mV} (47\text{k} \parallel 47\text{k}) (10\text{k} \parallel 47\text{k} \parallel 1.667\text{k})$$

$$= 355.48 \text{ K}\Omega$$

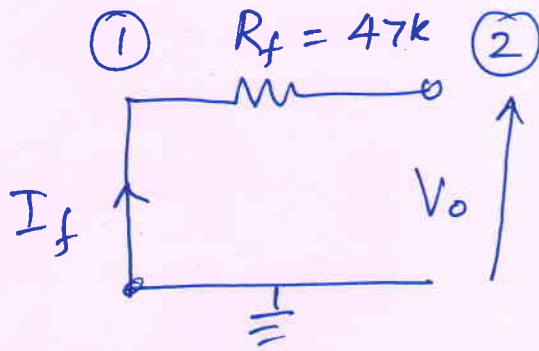$\beta$  network is shown below for  $\beta$  measurement (7)



$$\beta_f = \frac{-I_f}{V_o} = \frac{-V_o/R_f}{V_o} = \frac{-1}{R_f} = \text{Units of Conductance}$$

$$\beta_f = -\frac{1}{47k} \text{ mhos or A/V}$$

$\therefore$  Transresistance with Gain  $A_f$

$$A_f = \frac{V_o}{I_s} = \frac{A}{1 + A\beta_f}$$

$$\frac{V_o}{I_s} = \frac{355.4k}{1 + \frac{355.4k}{47k}} = \boxed{-41.511 k\Omega}$$

$$\boxed{D = 1 + \frac{355.4k}{47k} = 8.56}$$

Voltage Gain with Feedback.



$$\frac{V_o}{V_s} = \frac{V_o}{I_s \cdot R_s} = (-41.511 k\Omega) \cdot \frac{1}{10k}$$

$$\boxed{R_{if} = D (R_s || R_{\pi}) = 166.8 \Omega} \quad \boxed{-4.1511 V/V} \quad R_{of} = \frac{R_o}{D} = \frac{(47k || 4.7k)}{8.56} = 498 \Omega$$


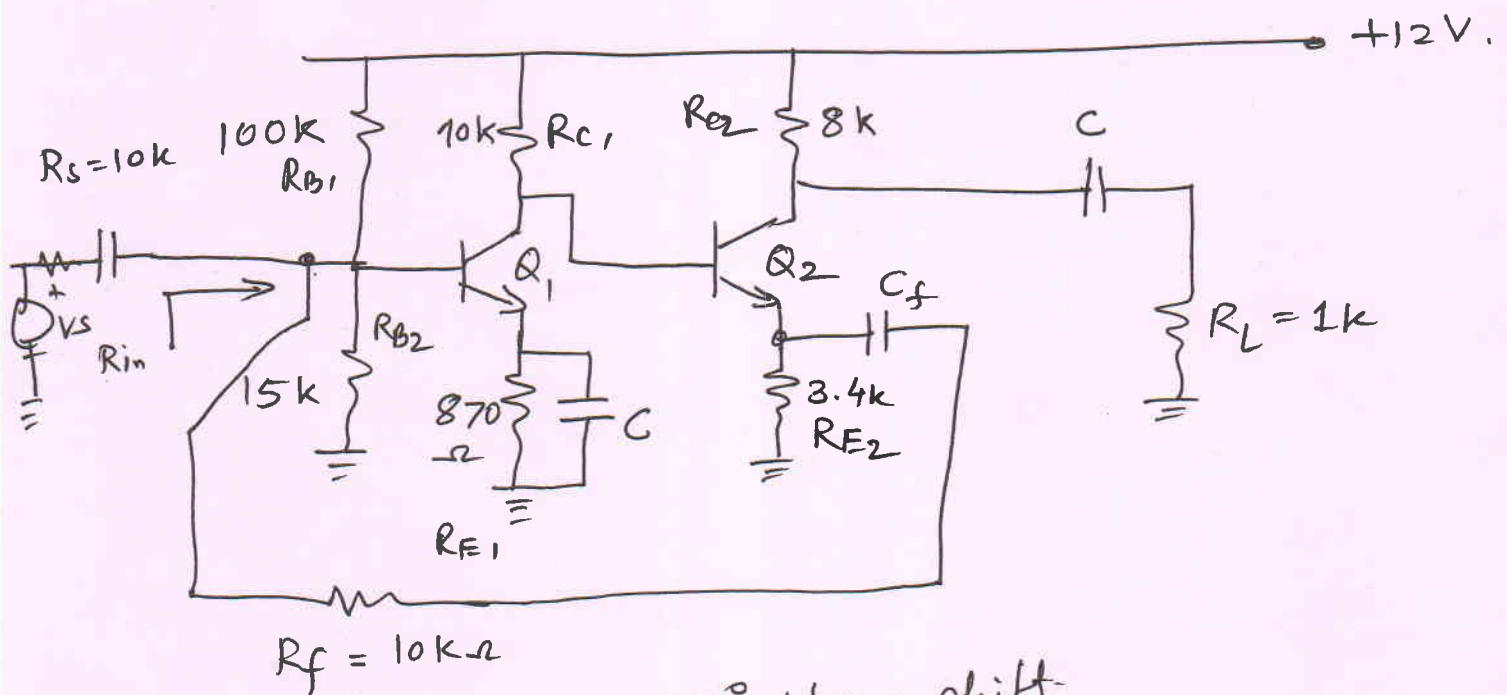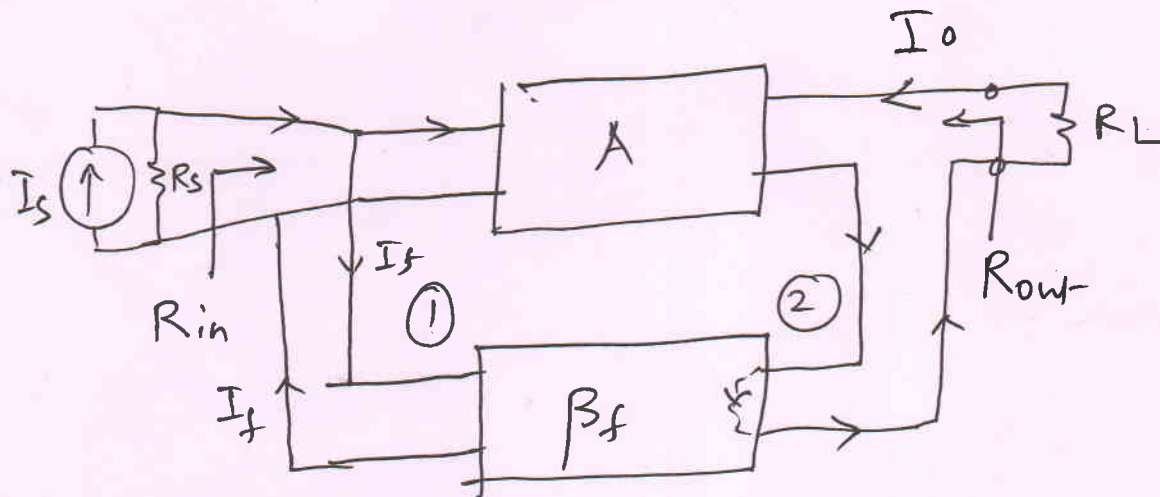
# SHUNT-SERIES FEEDBACK (8)

CURRENT ~~Voltage~~ Sampled inserted in input in Shunt.



$Q_1$  = first stage  $180^\circ$  phase shift  
 $Q_2$  = second stage  $0^\circ$  " " (like emitter follower)


$V_f$  = Output is voltage across  $R_{E2}$   
 $\therefore V_f \propto$  Output Current.

$V_f$  is inserted in shunt with  $V_s$ .  
 $C_f$  is to isolate DC in both places.




# Equivalent small signal model

(9)

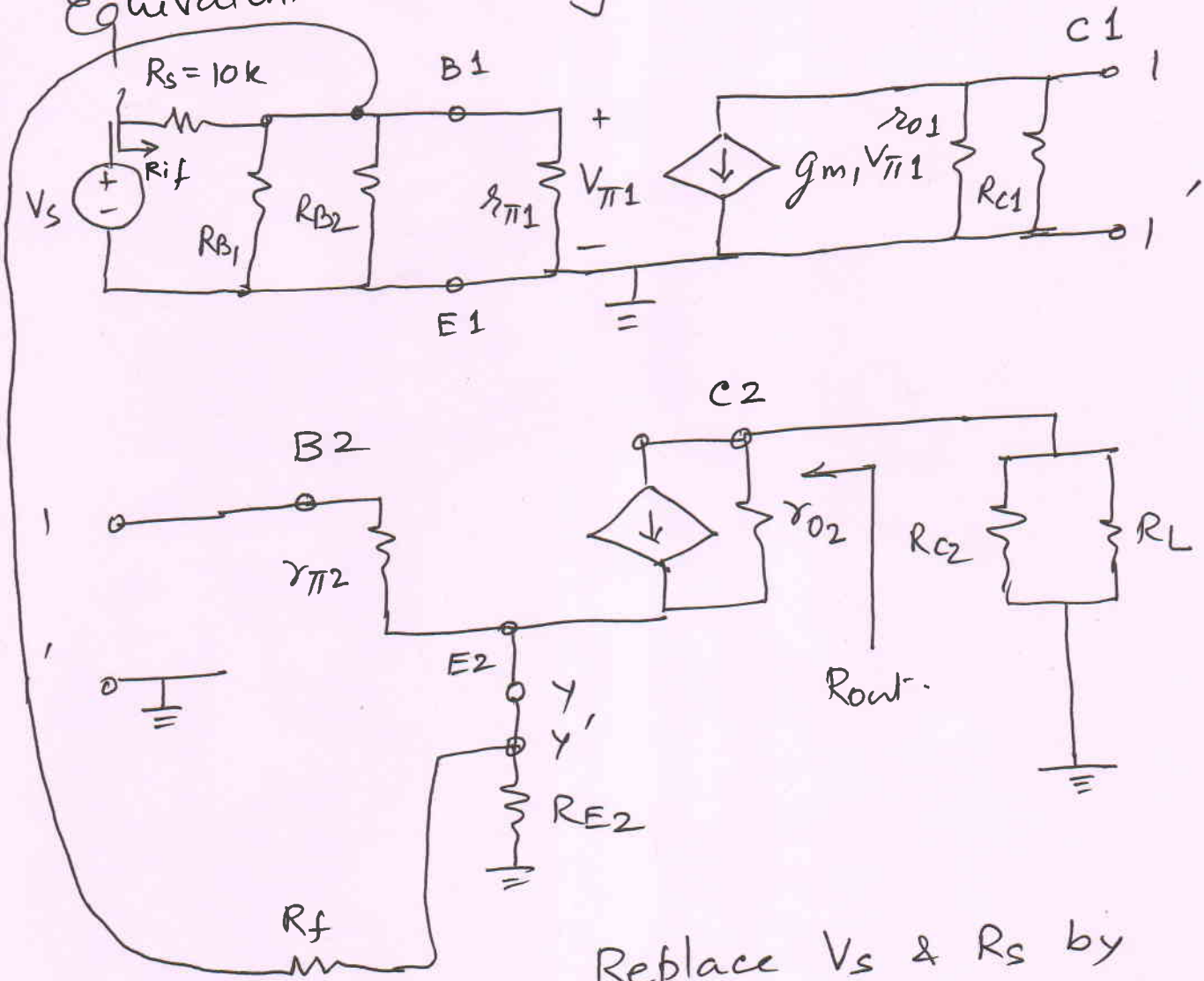



Replace  $V_s$  &  $R_s$  by Norton Equivalent.

$\beta_f$  network looks like

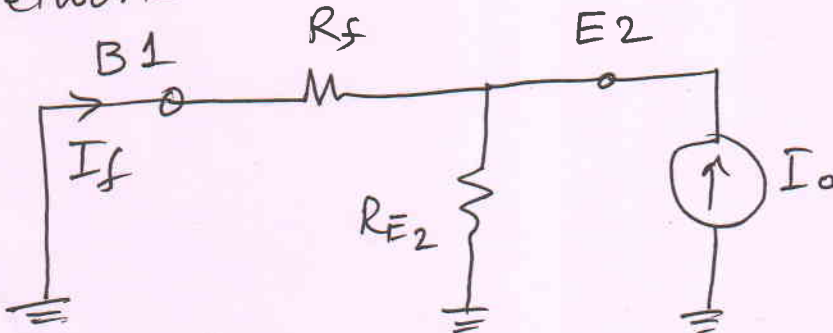


$$\beta_f = \frac{I_f}{I_o}$$
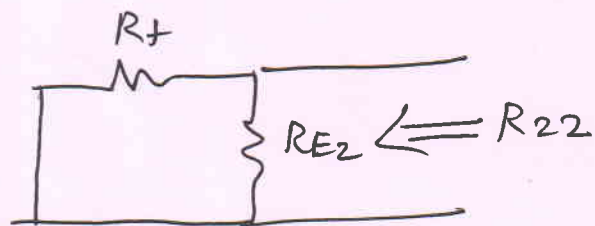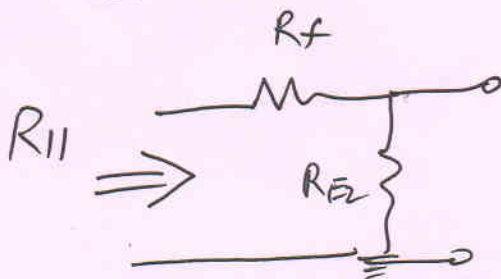
$$\beta_f = - \frac{R_{E2}}{R_{E2} + R_f}$$



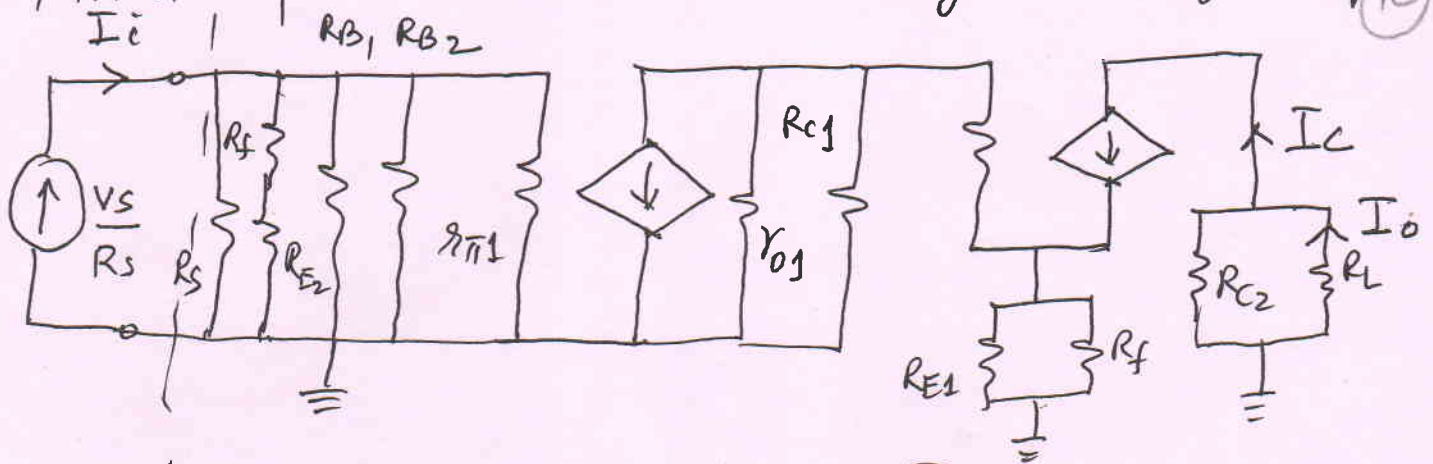Final Eqr. Circuit for A using loading of  $\beta$  (10)



We have to calculate  $A = \frac{I_o}{I_i}$   
Current gain

Knowing  $A$  &  $\beta_f$  get  $A_f$ ,  $R_{if}$ ,  $R_{of}$ .


$$R_{if} = \left\{ R_s \parallel (R_f + R_{E2}) \parallel R_{B1} \parallel R_{B2} \right\} \parallel r_{\pi 1} \times D$$

$$R_{of} = \left\{ (R_{E2} \parallel R_f) + r_{e2} + \frac{R_{c1} \parallel r_{o1}}{\beta + 1} \right\} \times D$$

# MULTI-STAGE SERIES SERIES
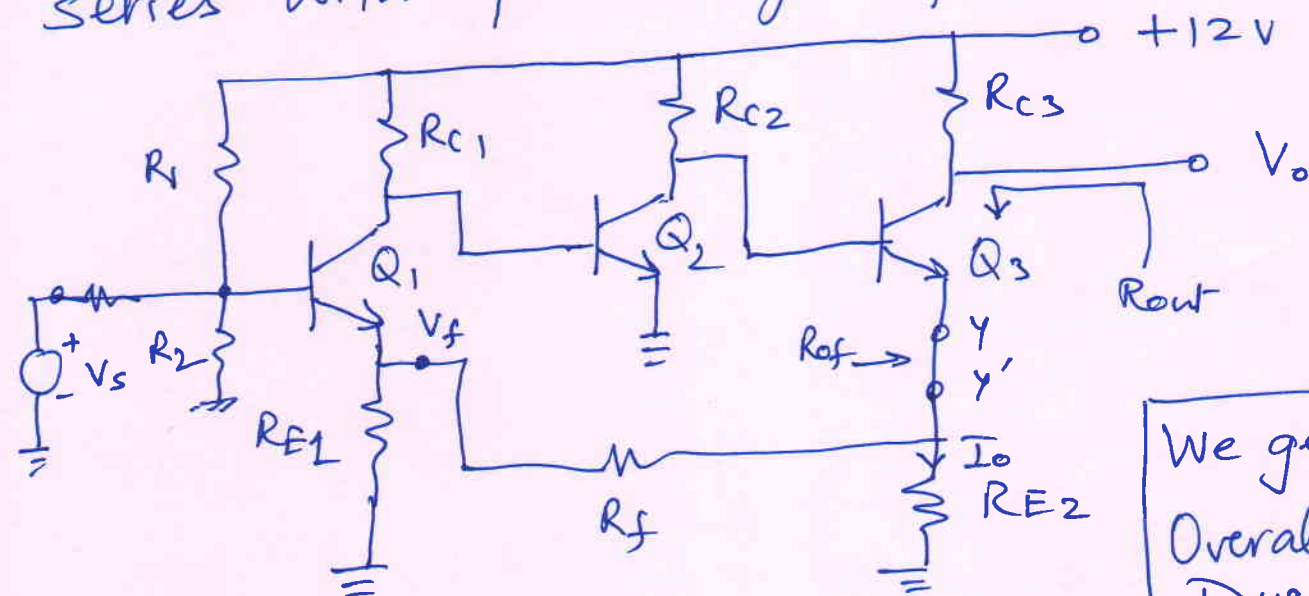
## FEEDBACK.

We can use a 3-stage amplifier (CE) and ~~use~~ tap third stage emitter voltage & inject it at first stage emitter. The output Current  $I_o$  will be sampled and inserted in series with first stage input circuit as  $V_f$



We get large Overall Gain Due to 3 Stages.

$$V_{B1} = V_s$$

$$V_{e1} = \text{in phase with } V_s$$

$$V_{c1} = 180^\circ \text{ out of phase with } V_s$$

$$V_{c2} = 180^\circ \text{ " " " " " } V_{c1} = 360^\circ \text{ with } V_s$$

$$V_{e2} = \text{in phase with } V_{c2} = \text{in phase with } V_s$$

Note  $V_{e1}$  &  $V_{e3}$  are in phase so  $V_f$  strengthens or increases  $V_{e1}$  & opposes more  $V_s$ . This is negative effect.