


SERIES - SERIES F/B Amplifier. ①

Ideal Case:


This topology uses a Voltage-Controlled (V_s) Current Source (I_o) and stabilizes Transconductance.

$A = I_o/V_o$ and β is I_o/V_f or trans-resistance.

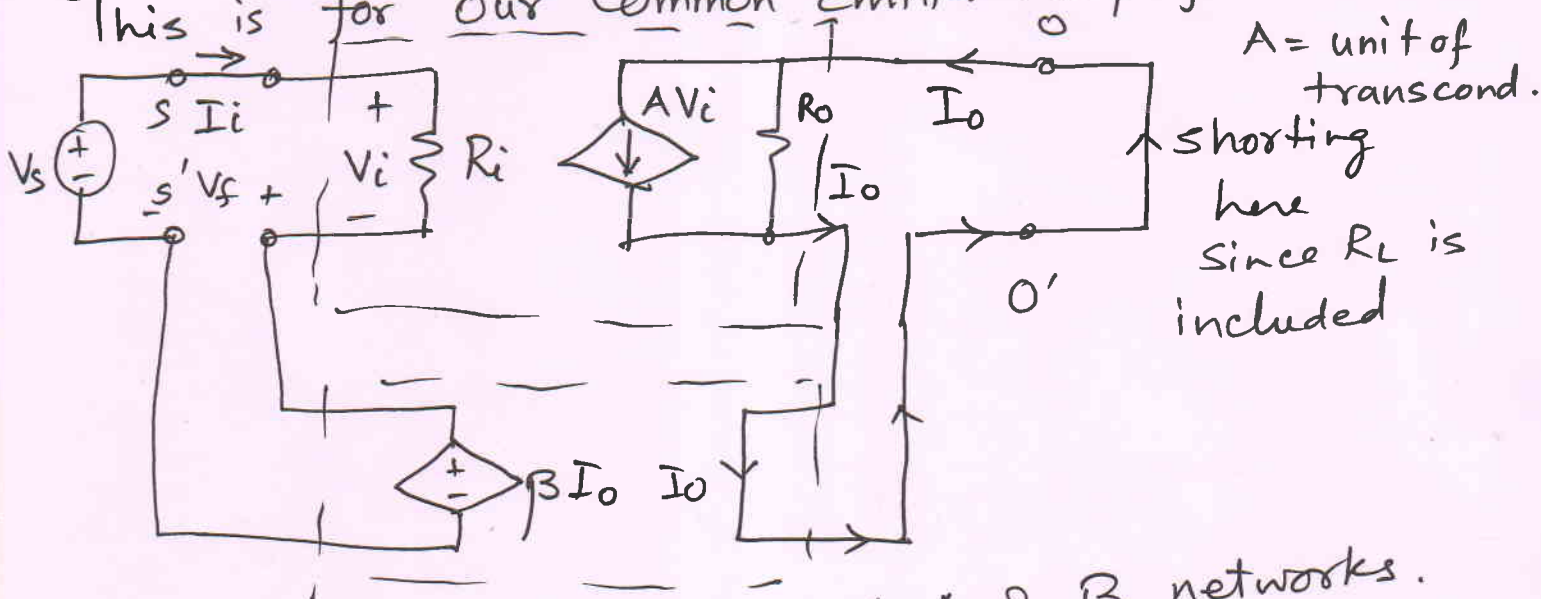This is for our Common Emitter Amplifier.



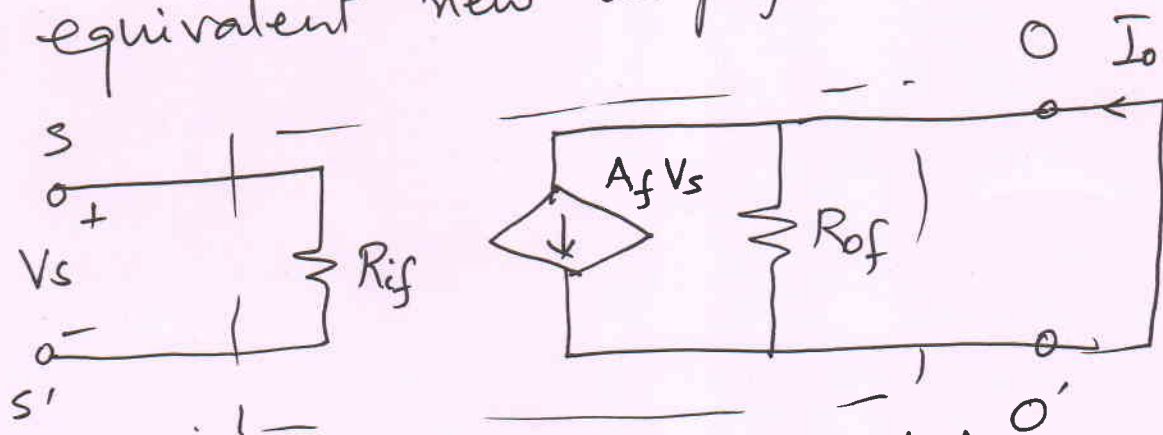Above block shows idealised A & β networks. The output current I_o passes through β network and produces proportional feedback voltage $V_f = \beta I_o$. Above can be reduced to equivalent new amplifier.



Calculate R_{if} and R_{of} and A_f .

$$A_f = \frac{I_o}{V_s} = \frac{A}{1 + A\beta}$$

where A = Transconductance of Original Amplifier with loading of β taken into account but no feedback is applied.


$$R_{if} = \frac{V_s}{I_i} = \frac{V_s}{V_i/R_i} = R_i \frac{V_s}{V_i}$$

$$V_s = V_i + V_f = V_i + \beta A V_i$$


$$\therefore R_{if} = R_i \frac{(V_i + \beta A V_i)}{V_i}$$

$$= R_i (1 + A\beta) = R_i \cdot D$$

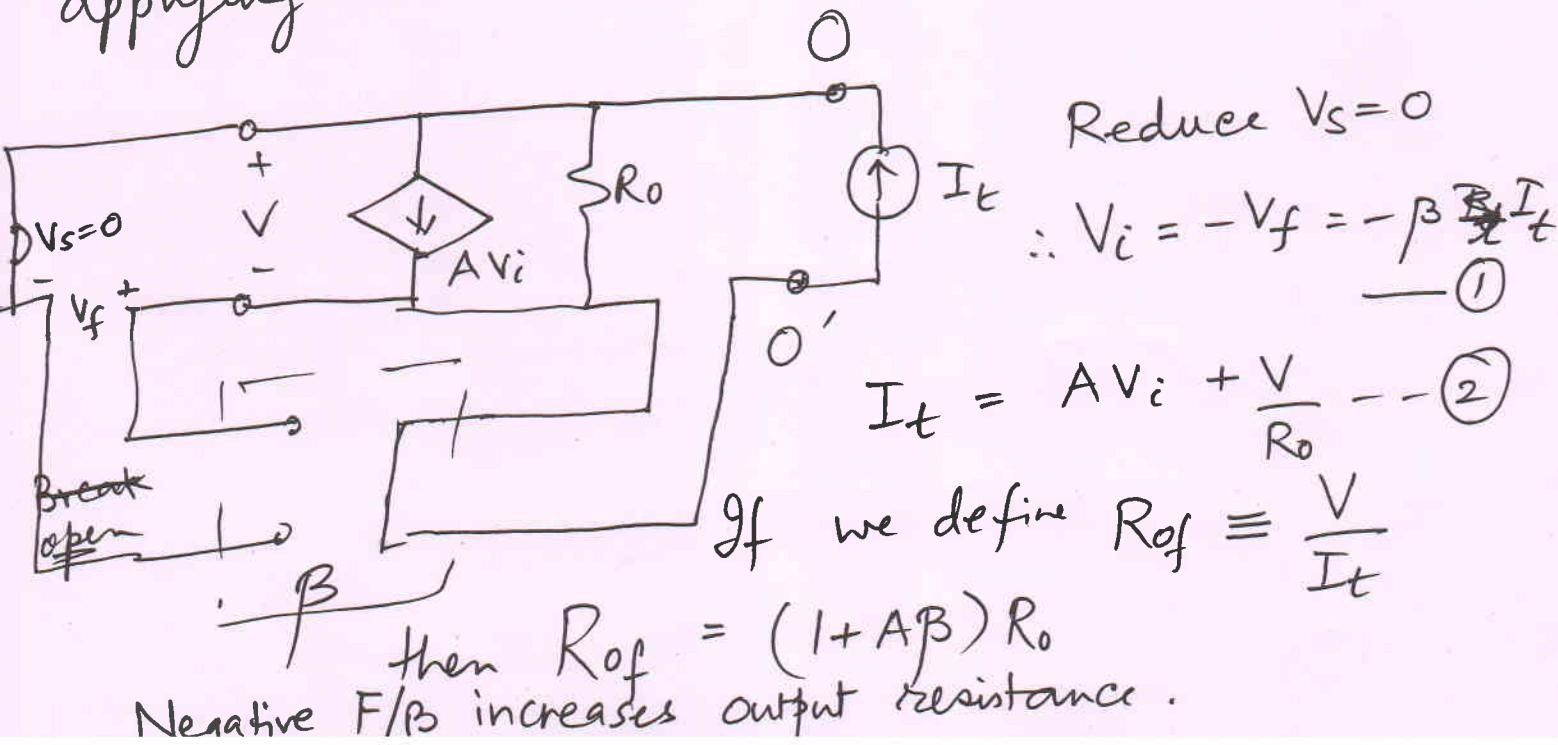
Input resistance R_{if} increases from R_i D times.
Now measure the output resistance by applying a current source I_t from output.



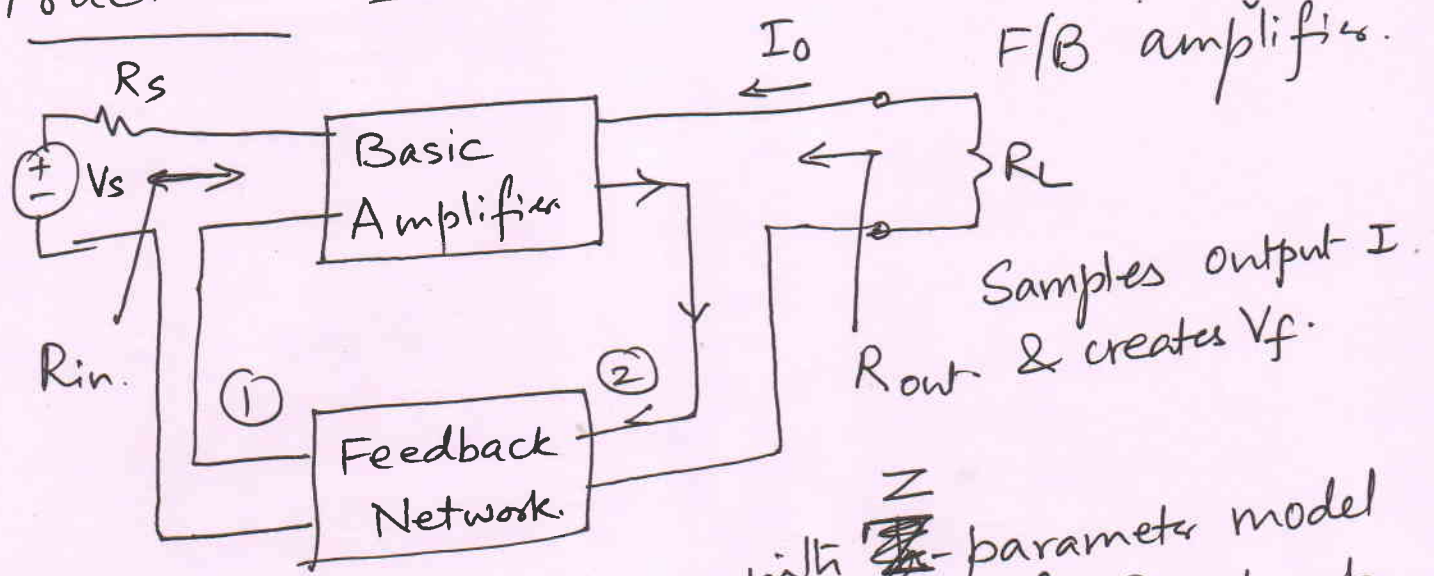Practical Case : See Series-Series Topology. (3)



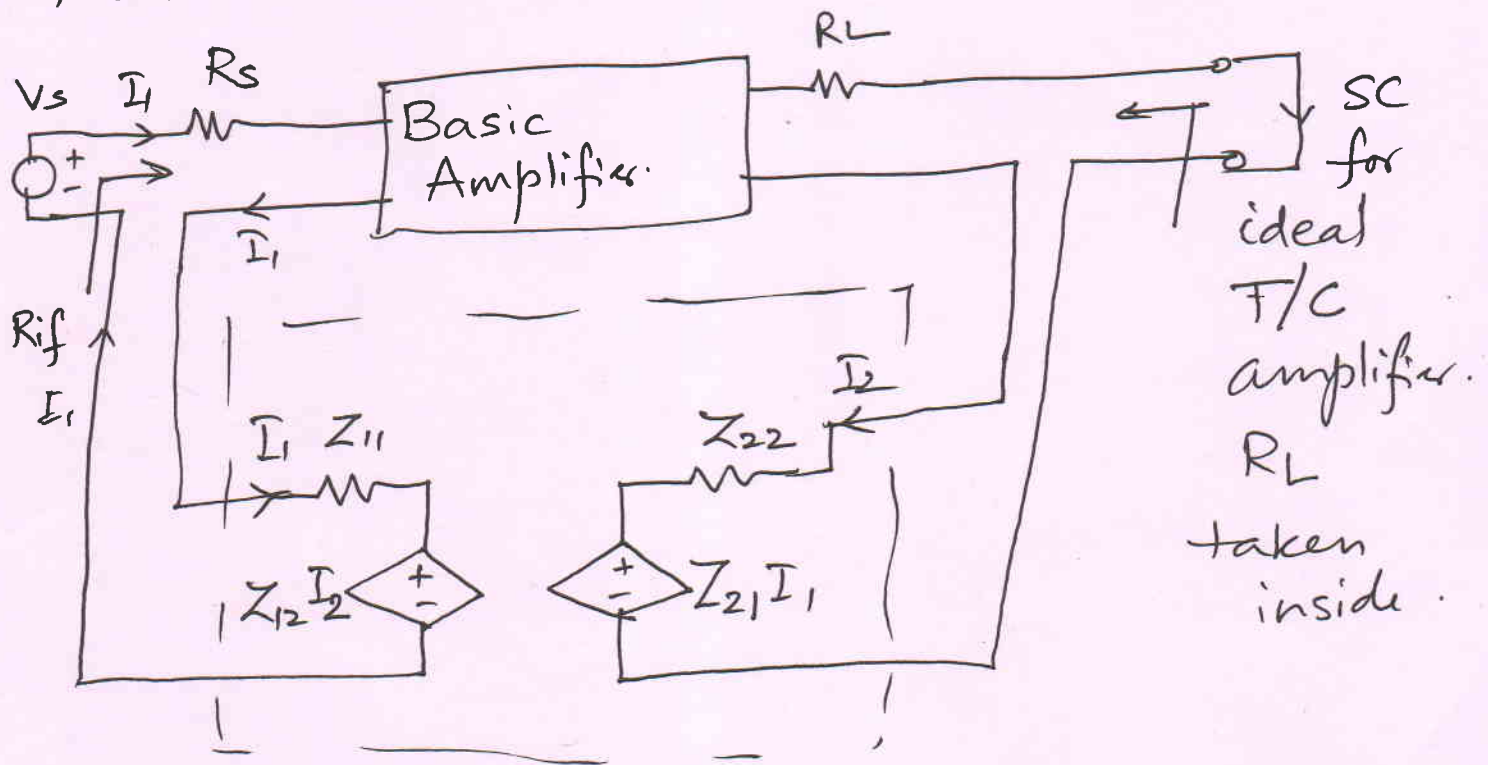Above circuit is shown with ~~Z~~ parameter model for β network.



Z_{11} and Z_{22} have units of resistance.

$$Z_{11} = \text{input resistance} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \text{output open circuited.}$$


$$Z_{22} = \text{Output " } = \left. \frac{V_2}{I_2} \right|_{I_1=0} \quad \text{input open circuited.}$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \text{forward \& } \quad Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \quad \text{Use } I_1 \text{ or } I_2 \text{ as excitation}$$

Appendix B.


Z_{11} and Z_{22} we will lump with original Amplifier just like we will do with R_s & R_L . (4)

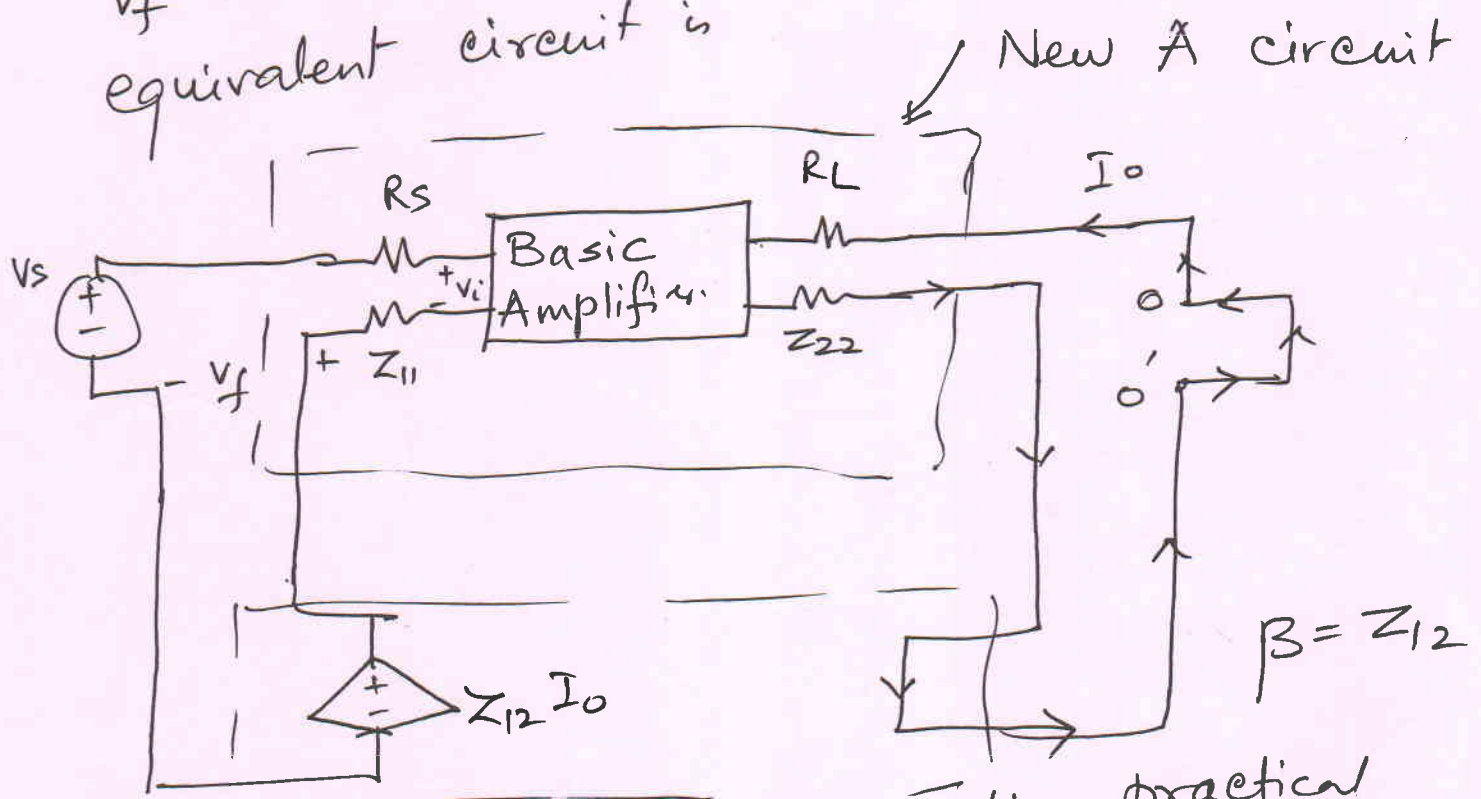Since β network is a passive unit of type attenuator its $Z_{21} \approx 0$ or very small as compared to A of Basic amplifier. So we neglect it and replace it with a SC. $Z_{12} I_o$ is retained as the feedback voltage V_f due to load current I_o . The reduced equivalent circuit is




The above circuit is converting practical circuit into ideal format by modifying A ckt.
Measurement / Calculation of R_{11} , R_{22} & β

A circuit is :

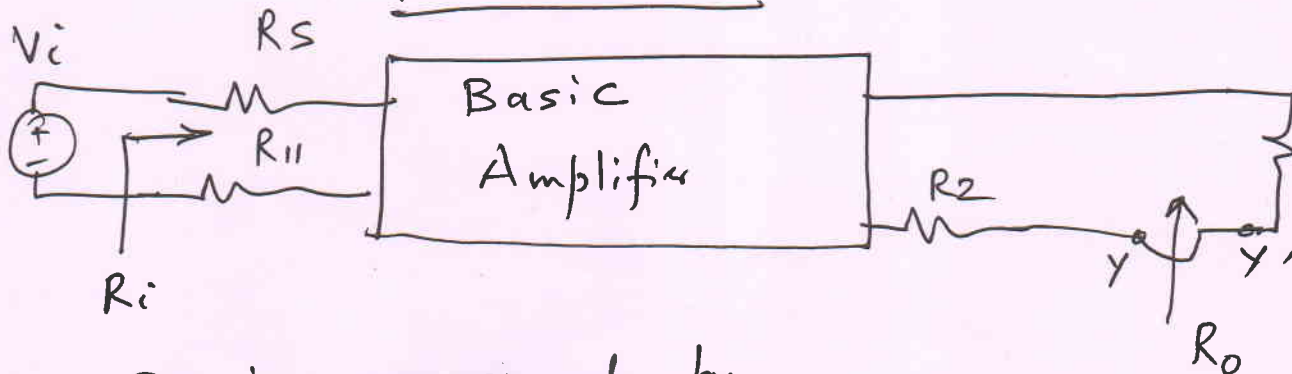


R_{ii} is measured by

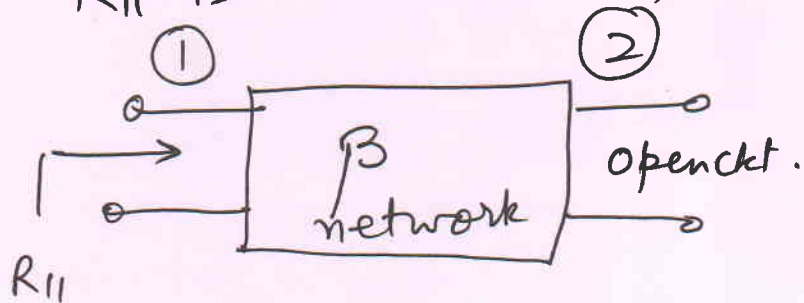


$$\text{Gain } A = I_o / V_i$$

To measure R_o
break Y-Y'
and see inside.

R_{22} is measured by

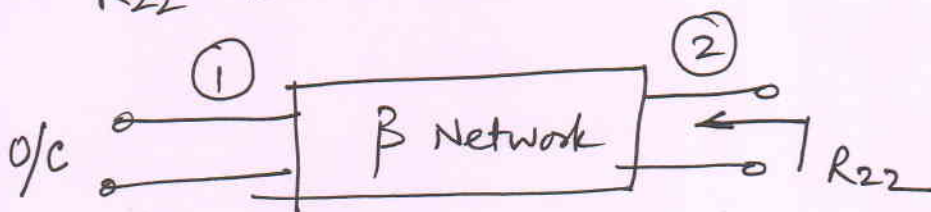

β is obtained by

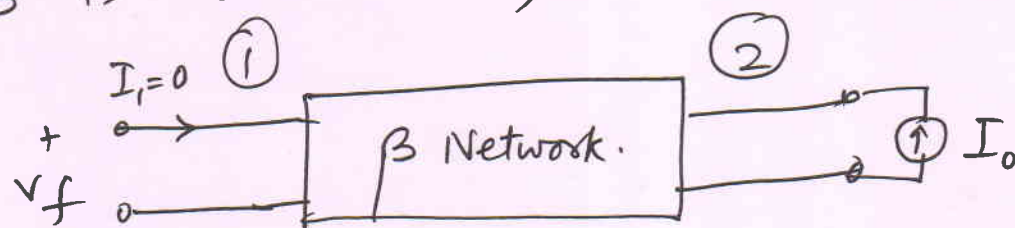

$$\beta = \frac{V_f}{I_o} \quad \text{when } I_i = 0 \quad \text{or input is disconnected.}$$