

24/03/2021

$$f_{im} = f_{RF} + 2f_{IF} \quad (\text{High})$$

$$\text{or } f_{im} = f_{RF} - 2f_{IF} \quad (\text{Low side injection})$$

$$\text{High: } f_{LO} > f_{RF} \Rightarrow f_{LO} = f_{RF} + f_{IF}$$

$$\text{Low: } f_{LO} < f_{RF} \Rightarrow f_{LO} = f_{RF} - f_{IF}$$

$$f_{IF} > \frac{B_{RF}}{2} \rightarrow \text{RF bandwidth}$$

FM radio:

$$88 - 108 \text{ MHz} \quad (f_{RF})$$

$$B_{RF} = 20 \text{ MHz}$$

$$f_{IF} > \frac{20}{2} = 10 \text{ MHz}; \quad f_{IF} = 10.7 \text{ MHz}$$

FM radio

$$RF = 88 - 108 \text{ MHz}$$

$$IF = 10.7 \text{ MHz}$$

$$f_{IF} = \frac{B_{RF}}{2}$$

\sqrt{LO}

$$LO = 98.7 \text{ to } 118.7 \text{ MHz}$$

(High side injection)

or

$$LO = 67.3 \text{ to } 97.3 \text{ MHz}$$

(Low side injection)

$$f_{im} = f_{RF} + 2f_{IF}$$

$$= (88 \text{ to } 108) + 2(10.7)$$

$$= (88 \text{ to } 108) + 21.4$$

$$f_{im} = 109.4 \text{ to } 129.4 \text{ MHz}$$

$$f_{im} = f_{RF} - 2f_{IF}$$

$$= 66.6 \text{ to } 86.6 \text{ MHz}$$

which
not the
in RF band
(88 - 108 MHz)

To avoid image

$$f_{im} = \cancel{f_{RF}} + 2f_{IF}$$

or

→ Lower IF

→ tracking accuracy is lowered


→ Higher IF

→ poor selectivity

or
poor adjacent channel
rejection

X

Hartley architecture for image rejection

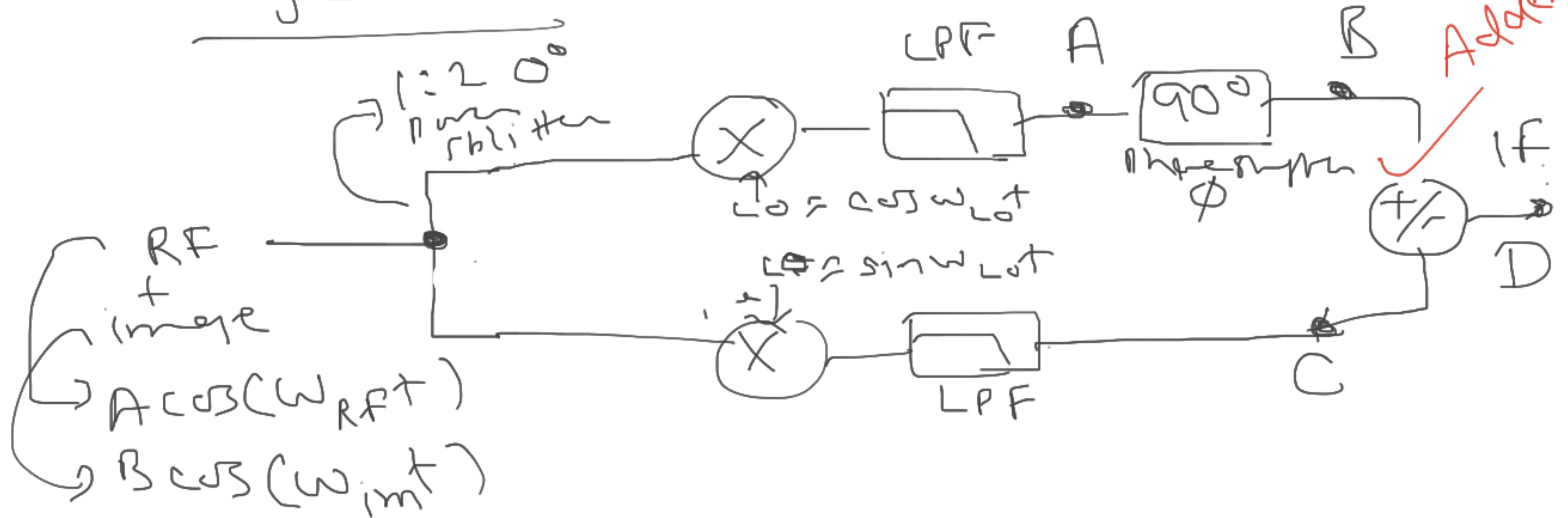

Signal at (A):

$$A \cos(\omega_{RF} t) \cos(\omega_{LO} t) + B \cos(\omega_{im} t) \cos(\omega_{LO} t)$$

$$= \frac{A}{2} \cos(\omega_{RF} - \omega_{LO} t) + \frac{B}{2} \cos(\omega_{im} - \omega_{LO} t)$$

after LPF
 $(\omega_{RF} + \omega_{LO})t$
&
 $(\omega_{im} + \omega_{LO})t$
→ rejected

$$= \frac{A}{2} \cos(\omega_{IF} t) \rightarrow \text{true if}$$

$$+ \frac{B}{2} \cos(\omega_{IF} t) \rightarrow \text{not desired IF}$$

Signal at (B): after 90° phase

$$\frac{A}{2} \cos(\omega_{IF} t + 90^\circ) + \frac{B}{2} \cos(\omega_{IF} t + 90^\circ) \\ = -\frac{A}{2} \sin(\omega_{IF} t) - \frac{B}{2} \sin(\omega_{IF} t)$$

Signal at (C):

$$A \cos(\omega_{RF} t) \sin(\omega_{LO} t) + \\ B \cos(\omega_{IM} t) \sin(\omega_{LO} t) \\ = -\frac{A}{2} \sin(\omega_{IF} t) + \frac{B}{2} \sin(\omega_{IF} t)$$

not true IF \rightarrow

true IF

after LPF to remove IF
 $IF = RF - LO$ or $IF = IM - LO$

$$\underline{\text{Signal at } \textcircled{D} :} = \textcircled{B} + \textcircled{C}$$

$$= -A \sin(\omega_{IF} t)$$

phase
curve


→ true IF, because it is from RF with amplified A

Drawback: → ~~added~~ systems
 (main) → to achieve exactly 90° phase change

Weaver's architecture for image rejection

↳ Ext. of Hartley's architecture

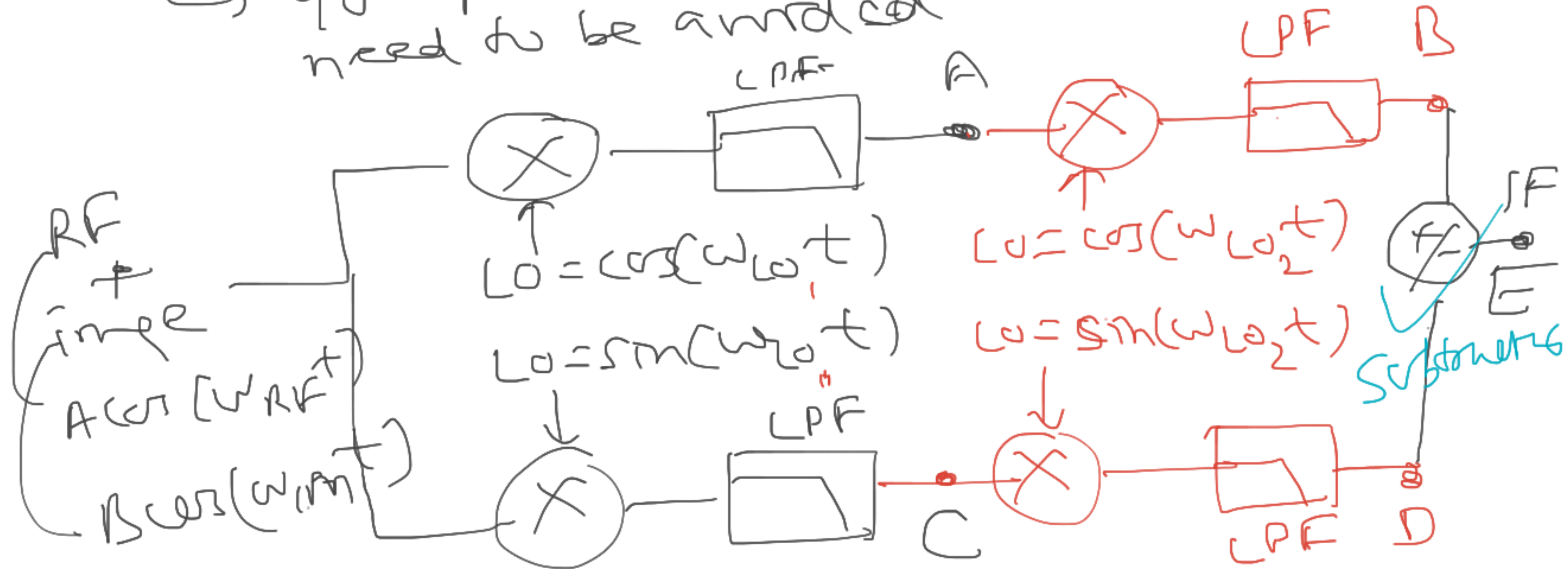↳ 90° phase achievement
need to be avoided



$$\begin{aligned} \textcircled{A}: & \frac{A}{2} \cos(\omega_{IF} t) + \frac{B}{2} \cos(\omega_{IF} t) \\ \textcircled{C}: & -\frac{A}{2} \sin(\omega_{IF} t) + \frac{B}{2} \sin(\omega_{IF} t) \end{aligned} \left. \vphantom{\begin{aligned} \textcircled{A}: \\ \textcircled{C}: \end{aligned}} \right\} \text{same as in Hatter's}$$

$$\begin{aligned} \textcircled{B}: & \frac{A}{2} \cos(\omega_{IF} t) \cos(\omega_{LO_2} t) \\ & + \frac{B}{2} \cos(\omega_{IF} t) \cos(\omega_{LO_2} t) \\ = & \frac{A}{4} \cos(\omega_{IF} - \omega_{LO_2} t) + \\ & \frac{B}{4} \cos(\omega_{IF} - \omega_{LO_2} t) \\ & \text{after LPF} \end{aligned}$$


$$\begin{aligned}
 \textcircled{D}: & -\frac{A}{4} \sin(\omega_{IF} t) \sin(\omega_{LO_2} t) + \\
 & \frac{B}{4} \sin(\omega_{IF} t) \sin(\omega_{LO_2} t) \\
 = & -\frac{A}{4} \cos(\omega_{IF} - \omega_{LO_2} t) + \\
 & \frac{B}{4} \cos(\omega_{IF} - \omega_{LO_2} t) \quad \text{only LPF}
 \end{aligned}$$

$$\begin{aligned}
 \textcircled{E}: & \textcircled{B} - \textcircled{D} \\
 = & \frac{A}{2} \cos(\omega_{IF} t) \rightarrow \text{true IF}
 \end{aligned}$$

Adv: no 90° phase shift required

Maximum Power Transfer \rightarrow Impedance

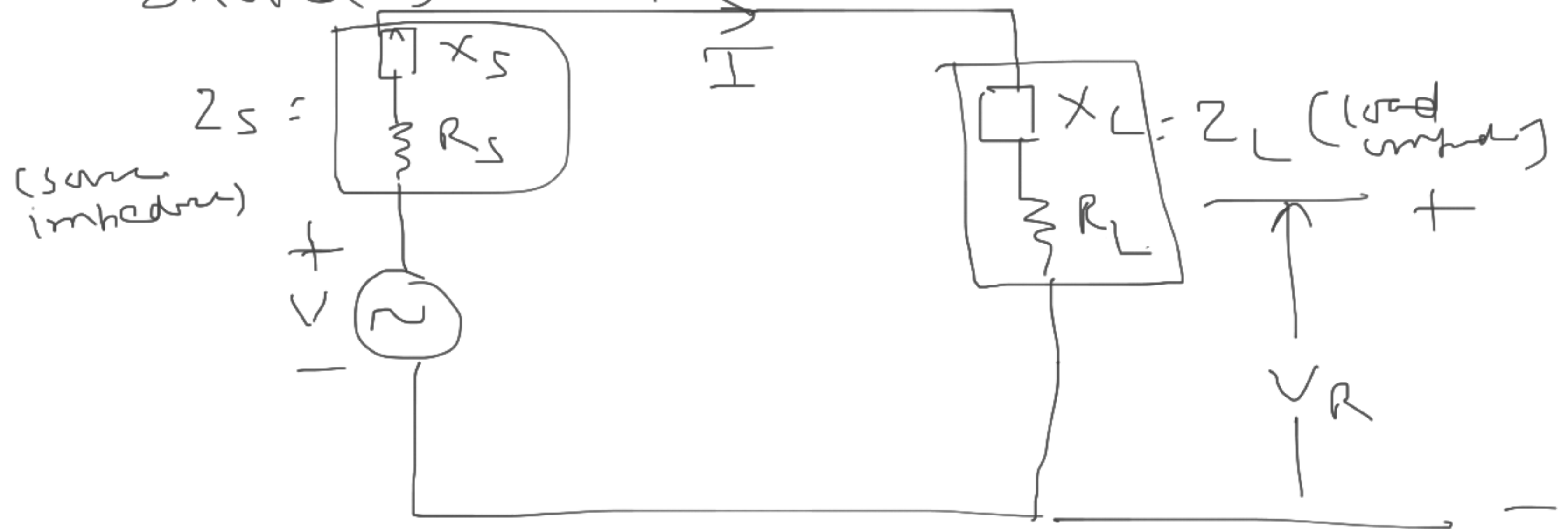(generator).
When a ~~stirny~~ source is required to deliver to a load, the power transfer should be maximum.



Average power delivered to load Z_L is:

$$P_L = V_R \cdot I$$

$$= [I \cdot R_L] \cdot I$$

$$[P = I^2 R]$$

$$= \frac{V}{\sqrt{(R_s + R_L)^2 + (X_s + X_L)^2}} \cdot R_L$$

$$\frac{V}{\sqrt{(R_s + R_L)^2 + (X_s + X_L)^2}}$$

$$P_L = \frac{V^2 R_L}{(R_s + R_L)^2 + (X_s + X_L)^2}$$

Power delivered to load, i.e. P_L should be maximum, i.e.

$$P_L = \frac{V^2 R_L}{(R_s + R_L)^2 + (X_s + X_L)^2}$$

① should be maximum

Looking first at effect of X_L on P_L ,

it will be seen that by making in ①

$X_L = -X_s,$

 — ② A

P_L will be at maximum when by

$$P_L = \frac{V^2 R_L}{(R_s + R_L)^2}$$

— ②

R_L can now be varied to maximize the expression (2), a best (maximum) value of P_L is obtained by equating

$$dP_L/dR_L = 0$$

From (2),
$$\frac{dP_L}{dR_L} = V^2 \left[R_L \cdot \frac{d}{dR_L} (R_S + R_L)^{-2} + (R_S + R_L)^{-2} \cdot \frac{dR_L}{dR_L} \right]$$

$$= V^2 \left[R_L \cdot (-2)(R_S + R_L)^{-3} + (R_S + R_L)^{-2} \cdot 1 \right]$$

$$\frac{dP_L}{dR_L} = V^2 \left[\frac{-2R_L}{(R_S + R_L)^3} + \frac{1}{(R_S + R_L)^2} \right]$$

$$\Rightarrow \frac{dP_L}{dR_L} = v^2 \left[\frac{-2R_L + (R_S + R_L)}{(R_S + R_L)^2} \right]$$

$$\Rightarrow \frac{dP_L}{dR_L} = \frac{v^2 [(R_S + R_L) - 2R_L]}{(R_S + R_L)^2} = 0 \quad \text{for max } P_L$$

from which

$$\boxed{R_S = R_L} \quad (B)$$

Combining (A) & (B),

Condition for max. power transfer

$$R_L + jX_L = R_S - jX_S$$



Conjugate matching of impedance

$$Z_L = Z_S^*$$