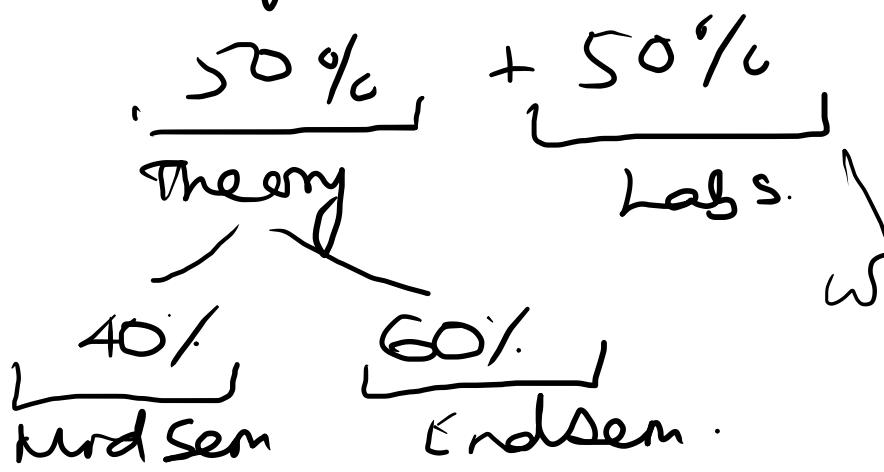



Book : Digital System Design (Using VHDL)
By Charles H. Roth
Lizy Kurian John.

Weightage



When you come back
to the Insti.
(ASAP)

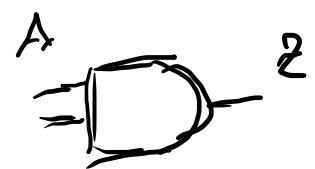
(Course for Registrars) : Assuming BEC + DLD + CO/CA



$$Z = A \cdot B = A \text{ and } B.$$

$$\text{OR} = A \wedge B = \frac{A \vee B}{A + B}$$


BASIC

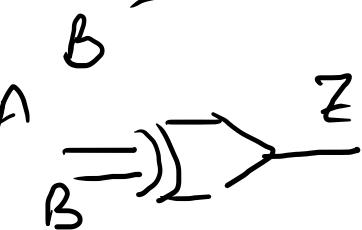

$$Z = A \oplus B = A \text{ XOR } B$$

$$Z = \bar{A} = !A = A!$$

Universal
Gates

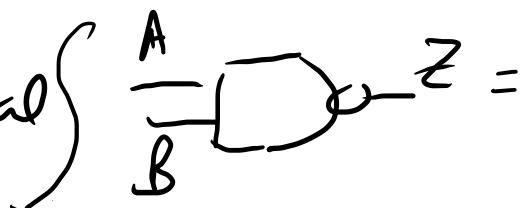


$$Z = A \text{ NAND } B = (A \cdot B)'$$

$$= Z = A \text{ NOR } B = (A + B)'$$




$$Z = \bar{\bar{A}}$$

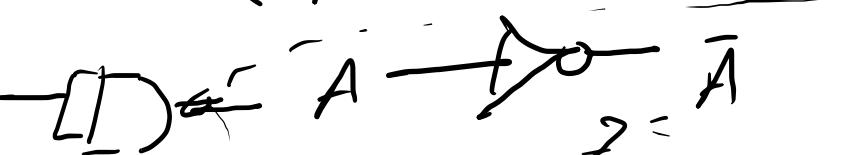MUX, EXOR, DFF, Latches,
memories, Adders, Controllers
 ↓
 MPUs, . . .




Karnaugh Map :-


full Adder

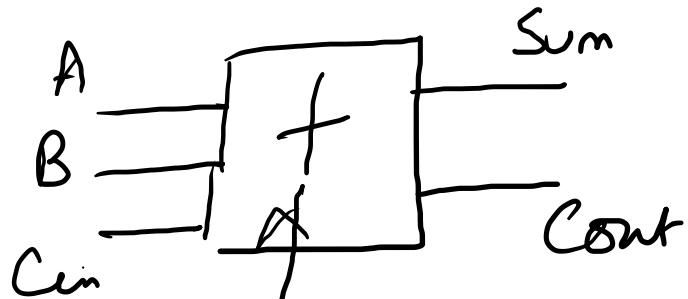
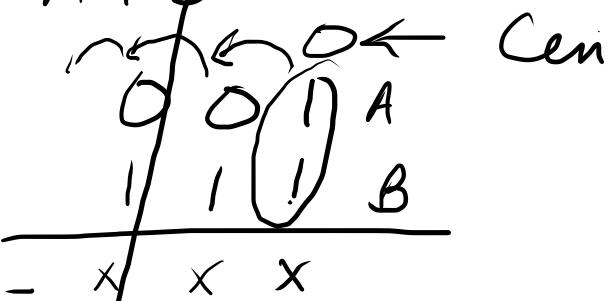
$$A + B + C_{in} = \text{Sum} + \text{Cout}$$



P/S. do not work

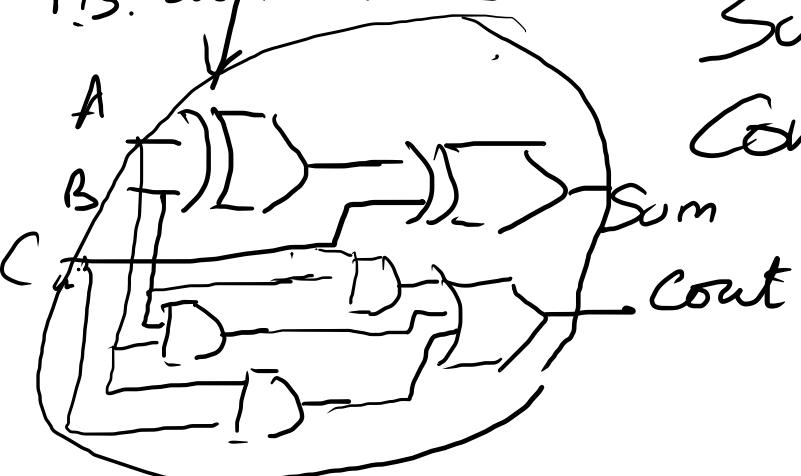

$$\text{Sum} = A'B'C_{in} + A'B'C_{in}' + AB'C_{in}' + ABC_{in}$$

$$= A \oplus B \oplus C$$

$$\text{Cout} = A'B'C_{in} + AB'C_{in} + ABC_{in}' + ABC_{in}$$

$$= AB + AC_{in} + BC_{in}$$

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

A	B	00	01	11	10
Cin	0	0	1		
	1	1	0		


Sum =

A	B	00	01	11	10
Cin	0	/	/	/	/
	1	/	/	/	/

(out -

4-variable K-map:

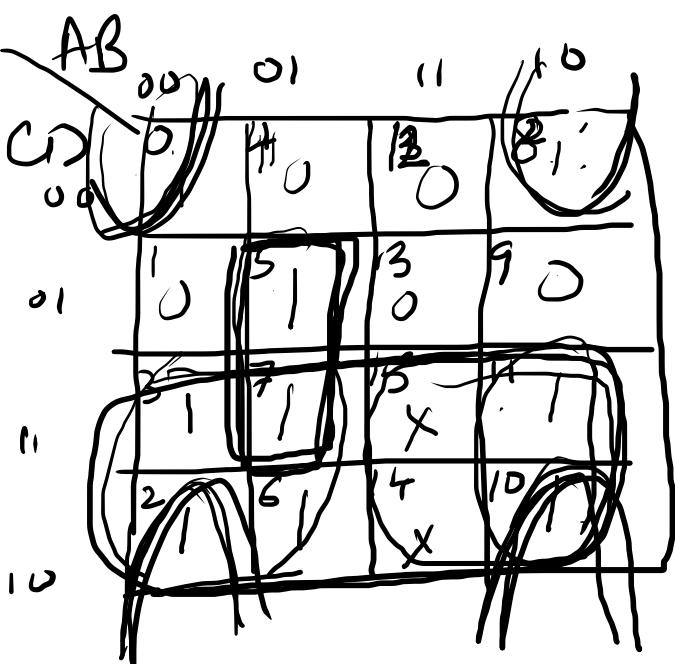
$$f = \sum m(0, 2, 3, 5, 6, 7, 8, 10, 11) + \sum d(14, 15)$$



$$= \underline{C} + \underline{B'D'} + \underbrace{\underline{A'B'D}}_{\text{Product}} \leftarrow \begin{matrix} \text{SOP} \\ \text{Sum of product} \end{matrix}$$
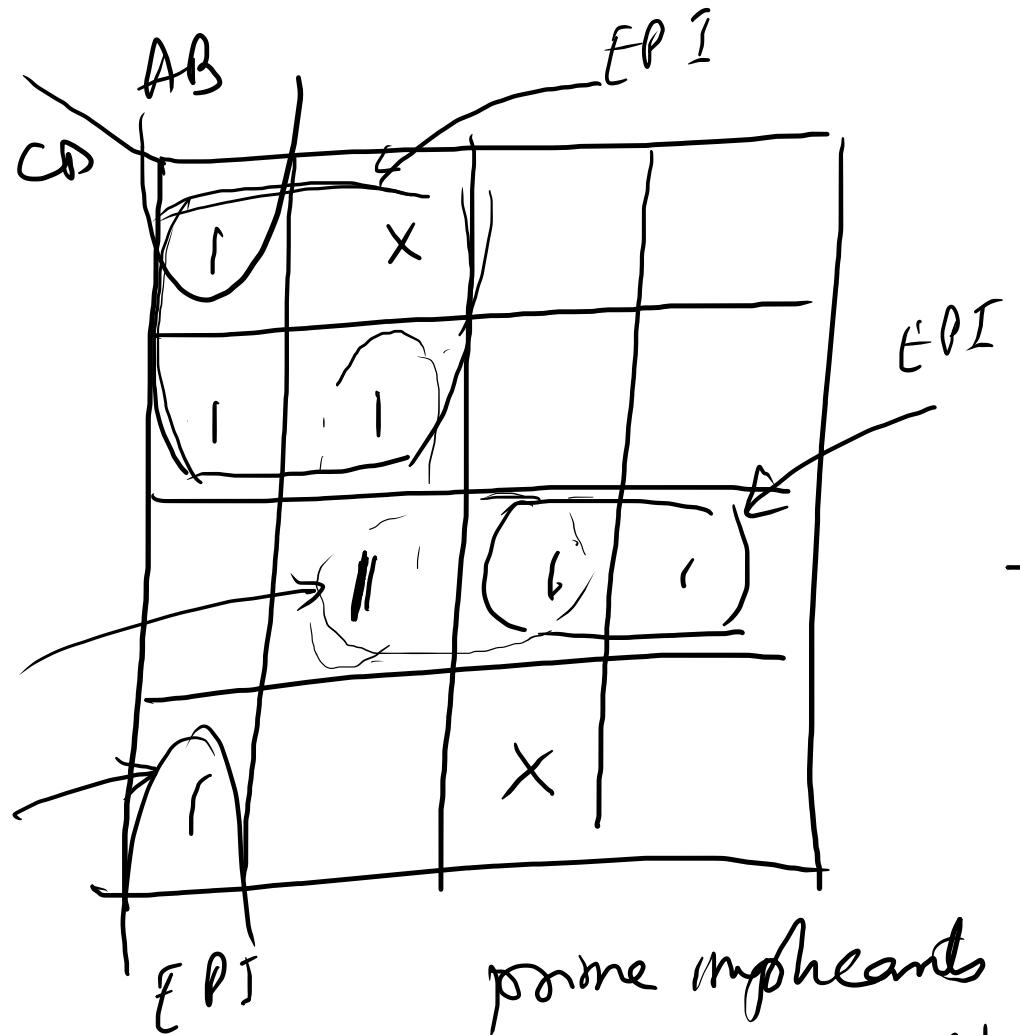
$$\begin{aligned} f' &= \cancel{B'C'D'} + \cancel{B'C'D} + \cancel{AB} && \text{POS} \\ &= \cancel{B'C'D} \cdot (B+C+D) \cdot (A'+B') && \text{Sum} \\ &&& \underbrace{ \cdot (B+C+D) \cdot (A'+B')}_{\text{Product of sums}} \end{aligned}$$





prime implicants :

$\text{EP I} : A'C', ACD, A'B'D'$


$$F = A'C' + ACD + A'B'D' + A'BD \quad \left. \begin{array}{l} \\ \\ \end{array} \right\}$$

$$A'C' + ACD + A'B'D' + BCD \quad \left. \begin{array}{l} \text{or} \\ \end{array} \right\}$$

A sum of one, two, four or eight adjacent 1's on a map represents a prime-implicant if it cannot be combined with another group of 1's to eliminate a variable.


If it is essential if it contains a 1 that is not contained in any other prime implicant.

$(A'C'), (ACD), (A'B'D')$, $A'BD$, BCD

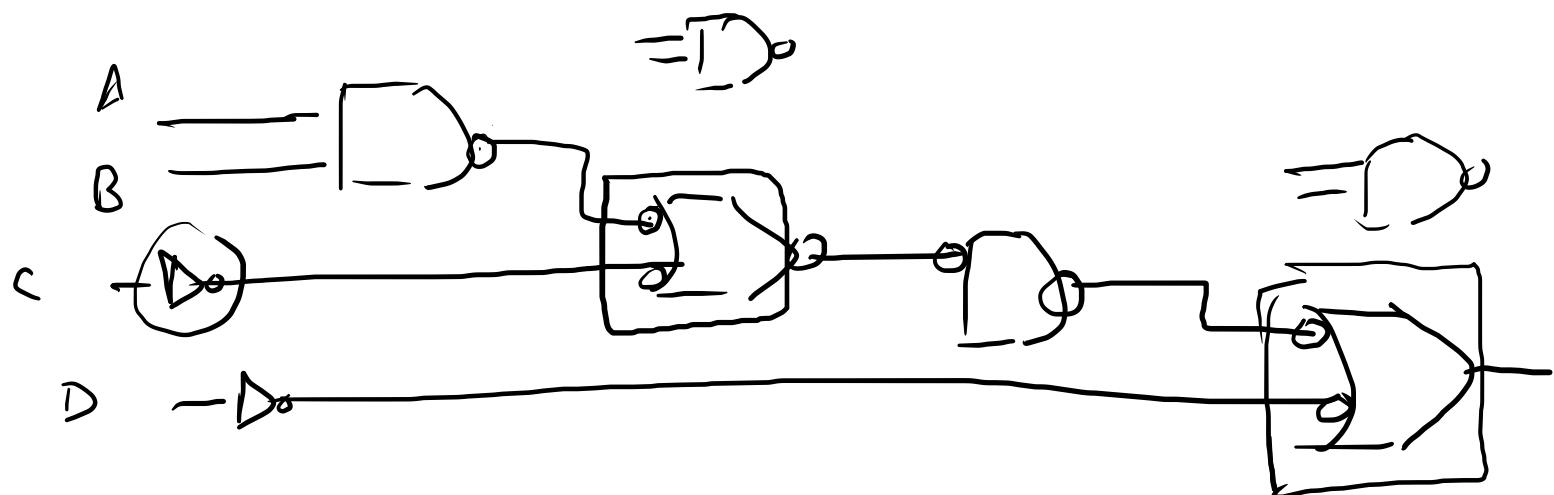




$$(A+B)' = \overbrace{A' \cdot B'}$$

nand gate realization

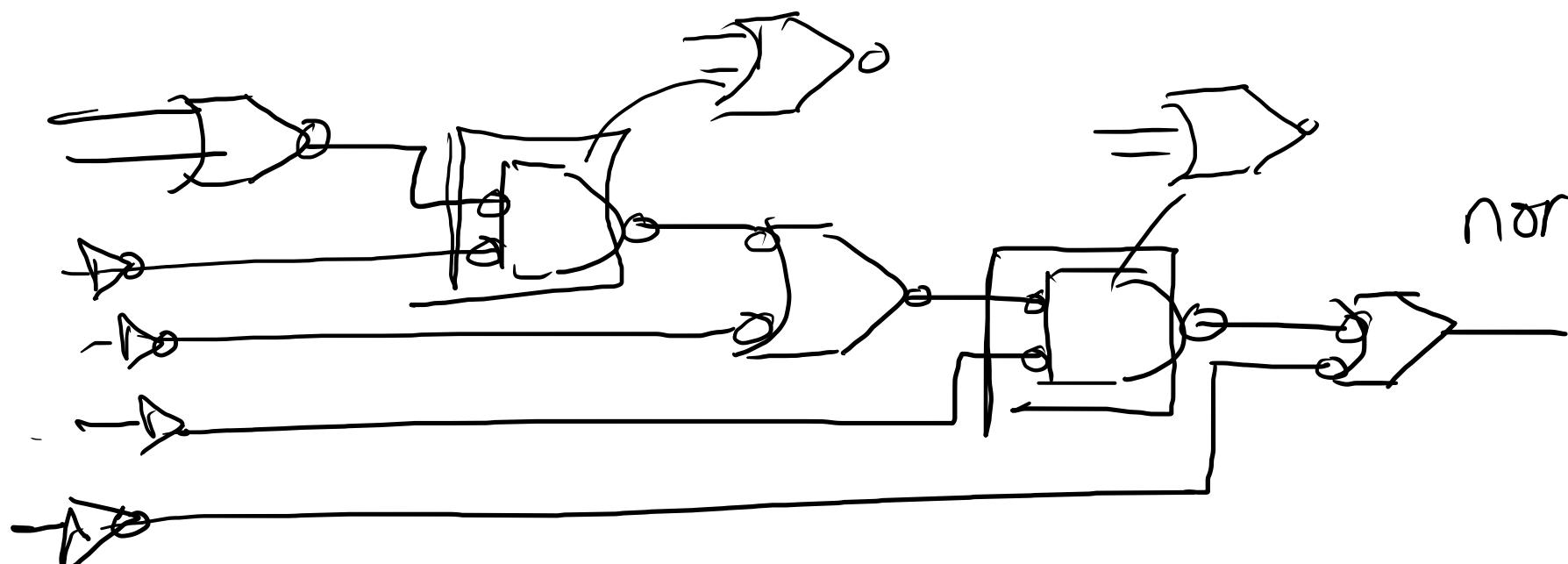


nor gate realization

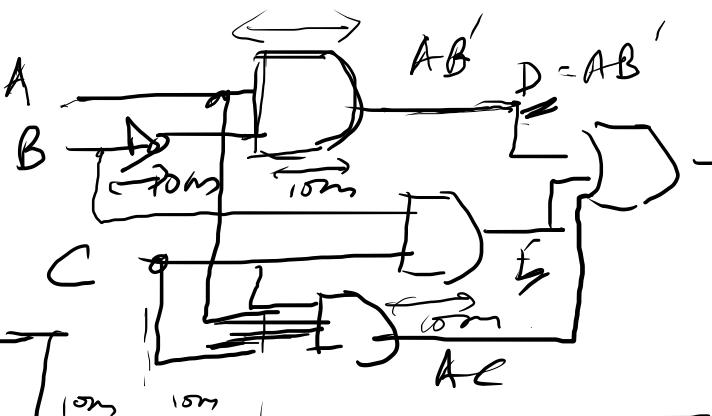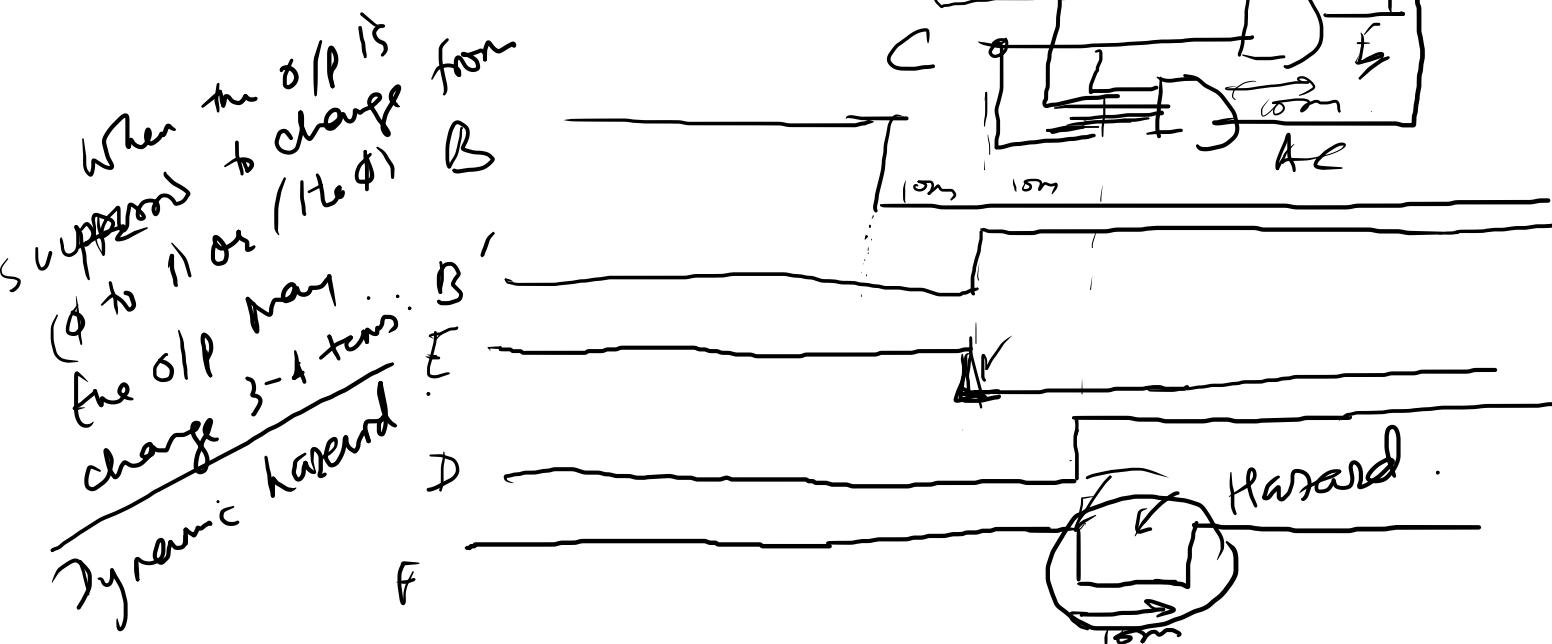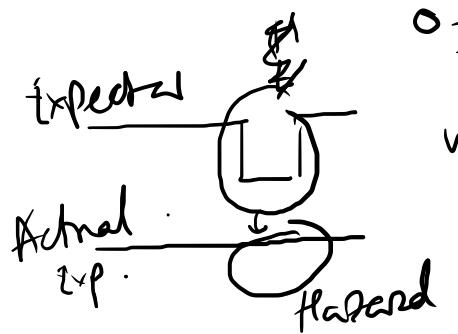Hazards: In response to an input change and for some combination of propagation delays a clk o/p may momentarily go to $U(1)$ when it should stay at 1(0) (State '1') / (State '0')






$$F = AB' + BC$$

Assume
 $A = C = 1$

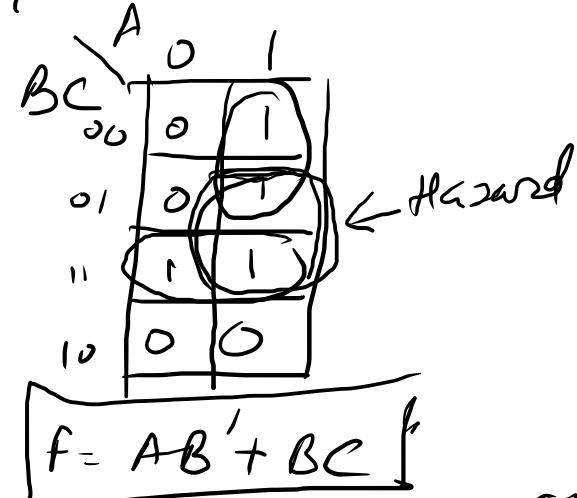

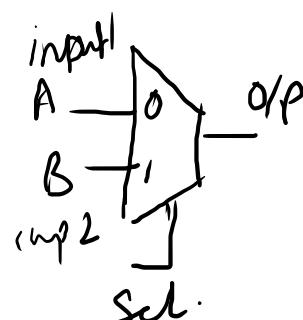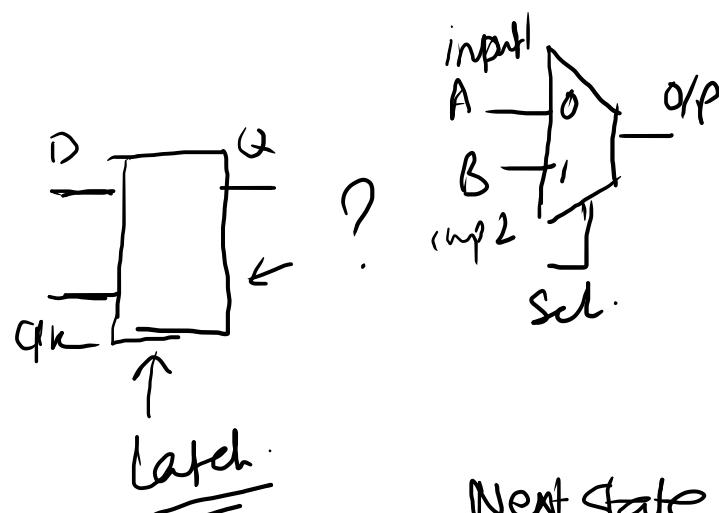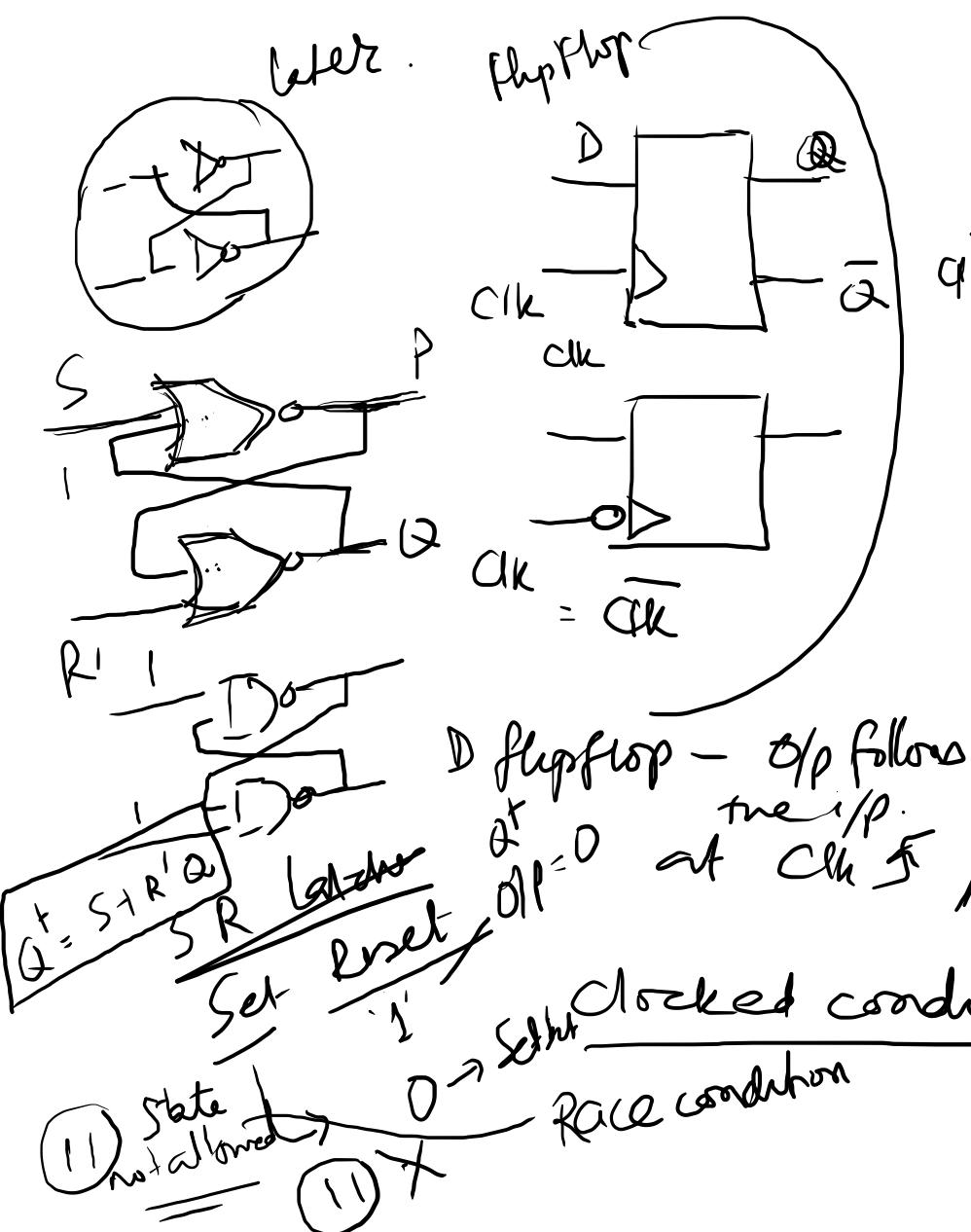
Static '1' hazard occurs in a SOP implementation when 2 minterms differing by only 1 ip variable are not covered by same product term. $f = AB' + BC + \underline{AC}$



JK Next state
 $Q = C.S.$
 $Q^+ = JQ' + K'Q$
 (Next) State equations.

Next State
 $Q^+ = D$

D	Q	Q ⁺
0	0	0
0	1	0
1	0	1
1	1	1

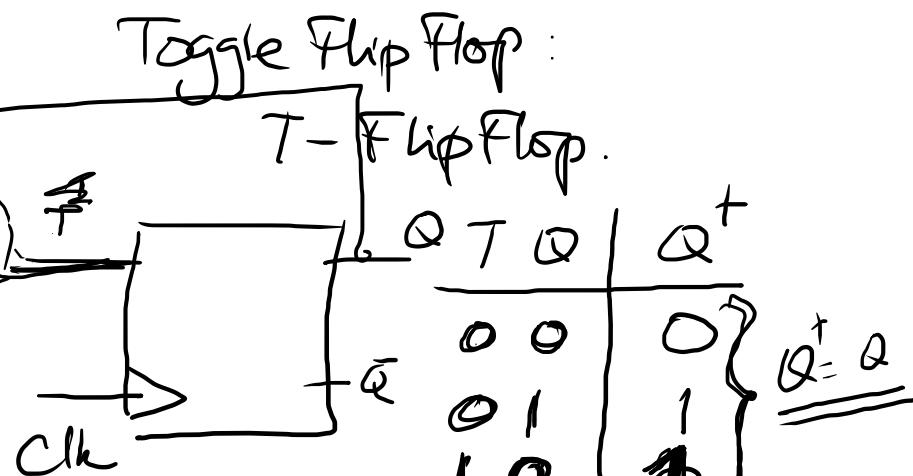

Toggles
 $Q^+ = QT' + Q'T = \underline{Q} \oplus T$

