

Note that there are two wavelength scales on the periphery of the chart. One is labeled *Wavelengths toward Generator* and the other *Wavelengths toward Load*. The first one is used when determining the impedance at a point *nearer the input* than the known impedance. This clockwise rotation is referred to as *moving toward the generator*, the assumption being that a generator is connected to the input. The second scale is used in determining the impedance at a point *nearer the load* than the known impedance. This counterclockwise rotation is referred to as *moving toward the load*.

The following example illustrates the graphical procedure for determining the impedance and admittance transformation due to a length of transmission line as well as other useful properties of the Smith chart.

Example 3-6:

A 5.2 cm length of lossless 100 ohm line is terminated in a load impedance $Z_L = 30 + j50$ ohms.

- Calculate $|\Gamma_L|$, ϕ_L , and the SWR along the line.
- Determine the impedance and admittance at the input and at a point 2.0 cm from the load end. The signal frequency is 750 MHz and $\lambda = \lambda_0$.

Solution:

- Plot the normalized load impedance $\bar{Z} = Z_L/Z_0 = 0.30 + j0.50$ on the Smith chart in Fig. 3-20. This is done by starting from the 0.30 point on the resistance axis and moving up 0.50 reactance units along the constant resistance circle. Next, draw a circle with its center at $\bar{Z} = 1$ (the center of the chart) and a radius equal to the distance between $\bar{Z} = 1$ and \bar{Z}_L . This is shown in the figure and will hereafter be referred to as the SWR circle. It is, in fact, the constant $|\Gamma|$ circle for the given value of load impedance. The \bar{Z}_L point on the Smith chart corresponds to its Γ_L value on the polar chart. Since the angle of the reflection coefficient scale has been retained, the value of ϕ_L (124° in this case) can be obtained from the chart as shown in the figure. The value of $|\Gamma_L|$ is obtained by measuring the radius of the SWR circle on the Reflection Coefficient-Vol. scale located at the bottom of the chart. In this example problem, $|\Gamma_L| = 0.62$.

One reason that the constant $|\Gamma|$ circle is called the *SWR circle* is that its intersection with the right half of the resistance axis (that is, between 1 and ∞) yields the SWR due to \bar{Z}_L . For this case, the SWR is 4.2. Since SWR is so easily obtained, many engineers prefer to calculate $|\Gamma|$ from Eq. (3-53) rather than using the Reflection Coefficient-Vol. scale. The reason that the resistance axis between 1 and ∞ serves as a SWR scale is that it corresponds to positive real values of Γ . As such it represents the magnitude of Γ for all normalized impedances on the SWR circle. Equation (3-101) transforms these values of Γ into $\bar{R} = (1 + |\Gamma|)/(1 - |\Gamma|)$, which is exactly the equation for SWR (Eq. 3-52). The unity SWR circle is simply a point at the center of the chart, while the infinite SWR circle is the periphery of the chart and is equivalent to $|\Gamma| = 1.00$.

- A graphical method of obtaining Γ_{in} when Γ_L and βl are known has been described. For a lossless line, it consists of rotating clockwise $2\beta l$ on the constant $|\Gamma|$ circle. The procedure for obtaining \bar{Z}_{in} from \bar{Z}_L is *exactly the same* except that the impedance coordinates of the Smith chart are used. The steps are as follows:
 - Plot \bar{Z}_L ($0.30 + j0.50$ in this case) and draw its SWR circle (4.20 in this case).
 - Draw a radial line from the center of the chart through \bar{Z}_L to the periphery. Read the value on the *Wavelengths toward Generator* scale (0.078 in this case).

This value in itself has no physical meaning. It is merely the starting point of the clockwise rotation in the next step.

3. Since $\lambda_0 = 40$ cm at 750 MHz and the input is 5.2 cm from the load, rotate clockwise from 0.078 a distance $l/\lambda = 5.2/40 = 0.130$. Draw a radial line from the center of the chart through the 0.208 point on the outer scale as shown in Fig. 3-20. The intersection of the radial line with the SWR circle represents \bar{Z}_{in} since it corresponds to the Γ_{in} point on the polar reflection coefficient chart. In this case, $\bar{Z}_{in} = 2 + j2$ or $Z_{in} = 200 + j200$ ohms.

To obtain the impedance at $d = 2$ cm, start from \bar{Z}_L and rotate clockwise $2/40 = 0.050$ and draw a radial line through the 0.128 point as shown. Its intersection with the SWR circle yields $\bar{Z} = 0.47 + j0.93$ or $Z = 47 + j93$ ohms.

This simple graphical method of determining the impedance transformation due to a length of lossless line is the most useful characteristic of the Smith chart. The procedure for determining the admittance transformation is *exactly the same* since all admittance points are directly opposite their corresponding impedance points on the SWR circle. Thus from the figure, $\bar{Y}_L = 0.88 - j1.47$, $\bar{Y}_{in} = 0.25 - j0.25$, and at $d = 2.0$ cm, $\bar{Y} = 0.43 - j0.87$. Multiplying these values by $Y_0 = 0.01$ mho gives the unnormalized admittance values.

Part *a* of this example problem illustrates how to determine $|\Gamma_L|$, ϕ_L , and SWR when Z_L and Z_0 are known. Since the line is lossless, the SWR and $|\Gamma|$ are the same at all other points on the line. The angle of the reflection coefficient, however, is a function of position and can be read on the periphery of the chart. In this example, $\phi_{in} = 30^\circ$ while at $d = 2$ cm, ϕ is equal to 88° .

Part *b* describes the graphical solution to the impedance/admittance transformation equation for lossless lines.¹⁶ Given \bar{Z}_L , the normalized impedance at any other point on the line is obtained by rotating clockwise on a fixed SWR circle the appropriate distance d/λ . Thus for a given load impedance, the SWR circle represents the locus of all possible impedance and admittance values available on the lossless line. Stated another way, given \bar{Z}_L , it is the locus of all possible values of \bar{Z}_{in} and \bar{Y}_{in} obtainable by varying the line length l . This is an example of how a good graphical procedure can show the effect of a variable (l) on the desired result (Z_{in}). For instance, it is obvious from Fig. 3-20 that if $\bar{Z}_L = 0.30 + j0.50$, varying the line length will never result in $\bar{Z}_{in} = 0.70 + j0.40$ since it is not on the SWR circle containing \bar{Z}_L . If the reader is ambitious, try proving this analytically. To further emphasize the chart's usefulness, consider the ease with which the following problem is solved. Given the impedance values in Ex. 3-6, what value of line length maximizes the reactive portion of the input impedance? With $\bar{Z}_L = 0.30 + j0.50$ plotted in Fig. 3-20, the SWR circle represents all possible values of \bar{Z}_{in} that can be obtained by varying l . A brief look at the chart shows that the reactive portion is maximized at the point where the SWR circle is tangent to the reactance lines. A positive reactive maximum occurs when $\bar{Z}_{in} \approx 2.3 + j2.0$. A radial line through this point intersects the *Wavelengths toward Generator* scale at 0.216. Therefore, the 100 ohm line must be $(0.216 - 0.078)$ or 0.138λ long.

¹⁶For a lossy line, a second SWR circle is required. It is obtained by multiplying $|\Gamma_L|$ by $e^{-2\alpha d}$ and converting the resulting $|\Gamma|$ to SWR. The intersection of the radial line with the circle defined by the new SWR value yields \bar{Z} at d units from the load.